

Phy 402G
Date


Electric charge

- Two kinds $+$ & $-$
- quantized $1.6 \times 10^{-19} C$ (often ignore this)
- conserved
- opposites attract, same sign repell

Electric force:


- Given by Coulomb's law

$$F = k \frac{q_1 q_2}{r^2}$$

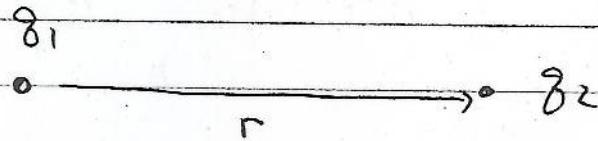

- Electric force is strong

Two electrons:

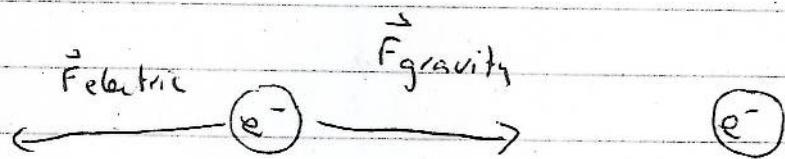


$$\frac{|\vec{F}_e|}{|\vec{F}_{\text{gravity}}|} \approx 10^{42}$$

Electric Field


- magnitude $\frac{\text{Force}}{q_0}$ where q_0 is (small) test charge.

- direction: Direction a \oplus test charge would go

Ex 1

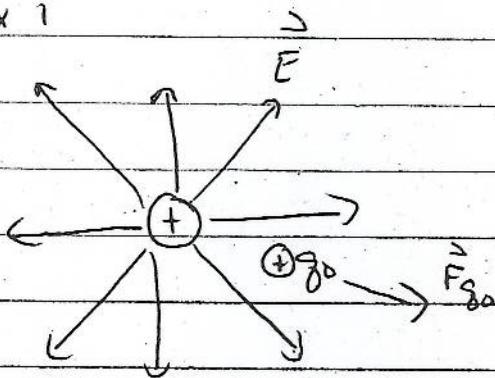



Ex 2

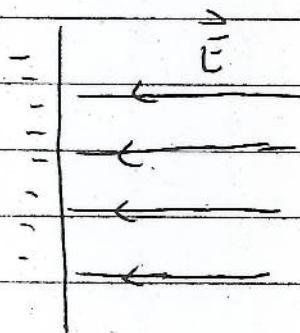Current (C/s or Amperes)

magnitude: ratio of flow of charge

$$I = \frac{dQ}{dt}$$

direction:

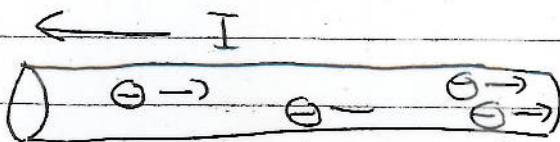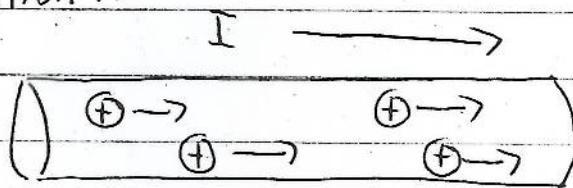

Drift speed in wire


$$\frac{4 \text{ "}}{1000 \text{ / sec}}$$

Signal speed:

$$\frac{12 \text{ billion inches}}{\text{sec}}$$

Voltage (Potential difference)
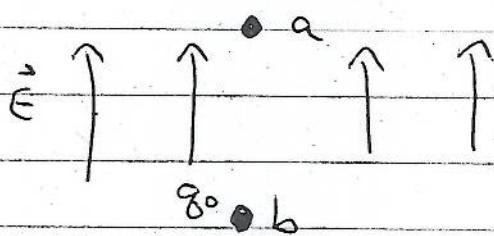
$$\Delta V = \frac{\text{work}}{\text{charge}}$$




- 1) Take some g_0 at b.
- 2) Move it to a
- 3) Measure work to do this
- 4) $V_b - V_a = \frac{\text{work}}{g_0} \rightarrow \text{Indep of } g_0$

Voltage is a relative quantity, describes the space


Potential energy describing position in space

When you go with a field line:

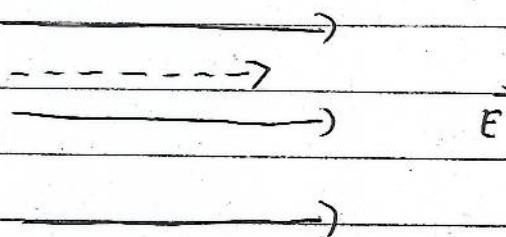

Voltage decreases


Against a field line

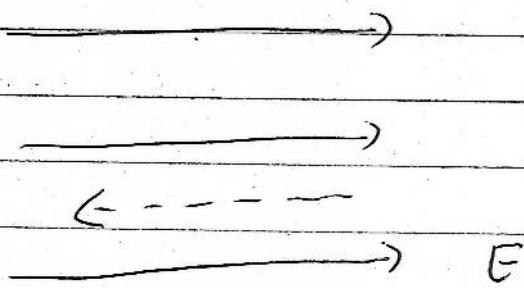

Voltage increases

+ charge "wants" to go from higher to lower voltage
- lower to higher

Resistance (ohms or Ω)

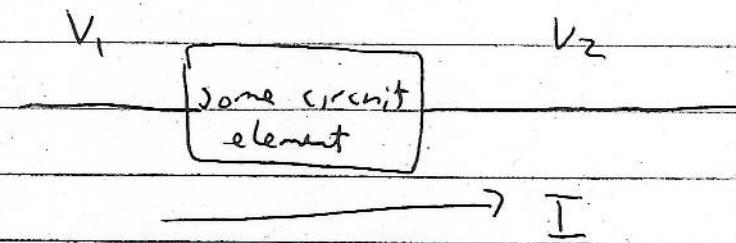

$$R = \frac{dV}{dI}$$


Often:

$$V = IR \quad \text{Ohm's Law}$$


↑
constant

Ohm's Law is

- useful
- Not fundamental

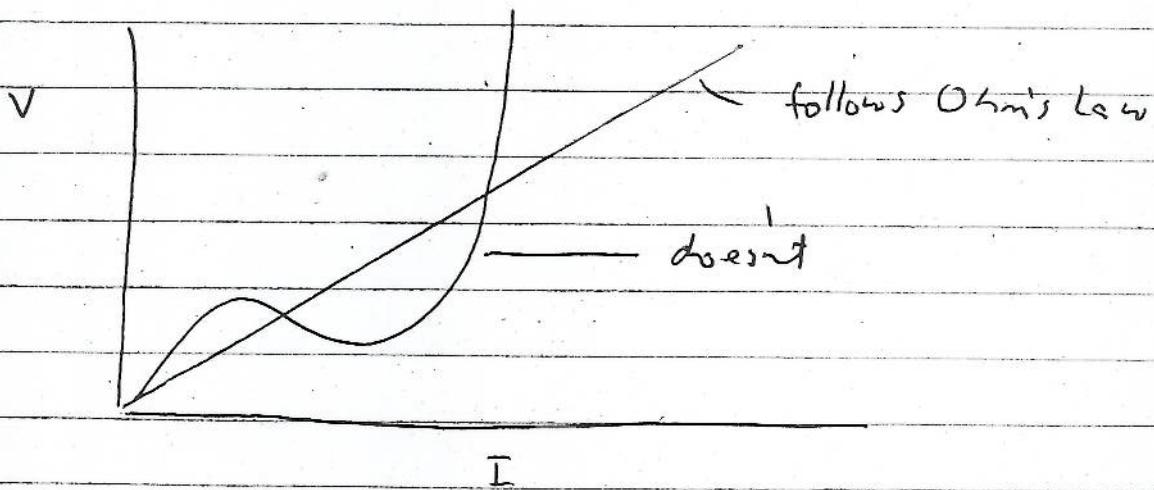

Typical resistor

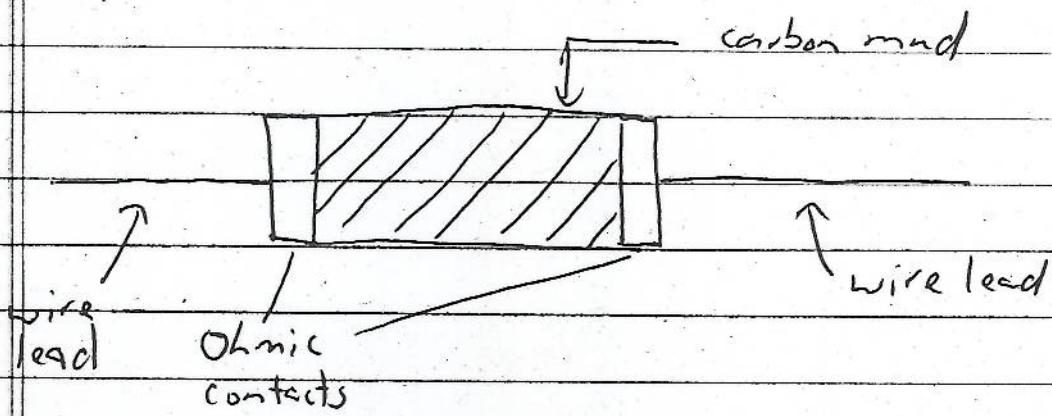

Symbol:




Resistivity

Consider water pipe

H_2O \rightarrow $\rightarrow H_2O$
in out
Harder to push water through This vs this

H_2O \rightarrow $\rightarrow H_2O$
in out



Wire

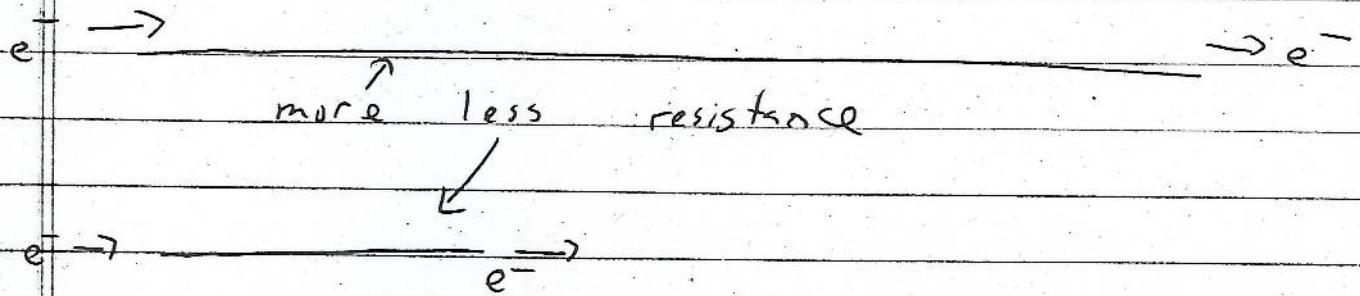

R & L

\uparrow
length of wire

Again, water analogy

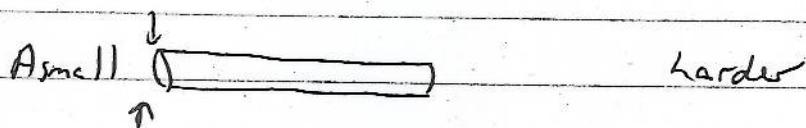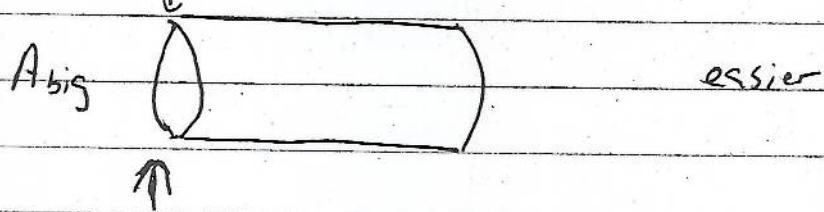

$$R \alpha \frac{1}{A} \leftarrow \frac{\text{cross sectional area}}{a_{\text{req}}}$$

$$R = \rho \frac{L}{A}$$

↑ resistance ↑ some constant:
 ↓ resistivity ← area ← length

ρ : bulk property

low ρ : conductor

high ρ : insulator

Conductors - charges move around easily

- metals

- humans

- salt solutions

- plasmas

Insulators - charges stuck to atoms/molecules

- plastic

- rubber

- glass

- quartz


(See resistor code in book.)

What good are resistors?

- Dissipate energy (heat, light)


- Drop voltage

To get $\Delta V \rightarrow$ need I

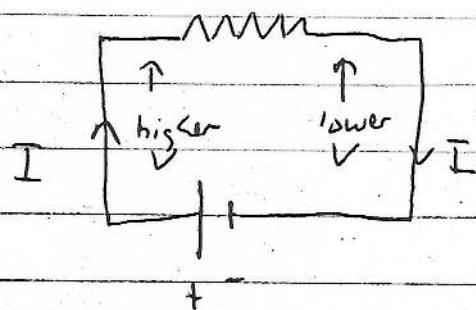


current goes from high V to low V

Resistors in series

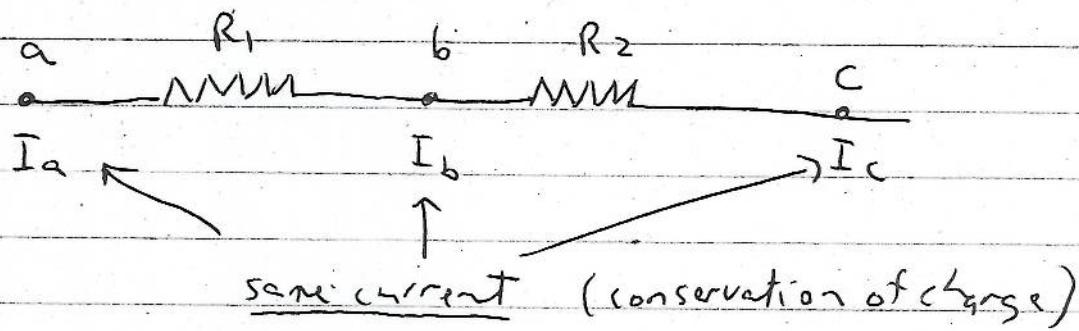

ΔV_R , not necessarily ΔV_{R2}

Resistors in parallel

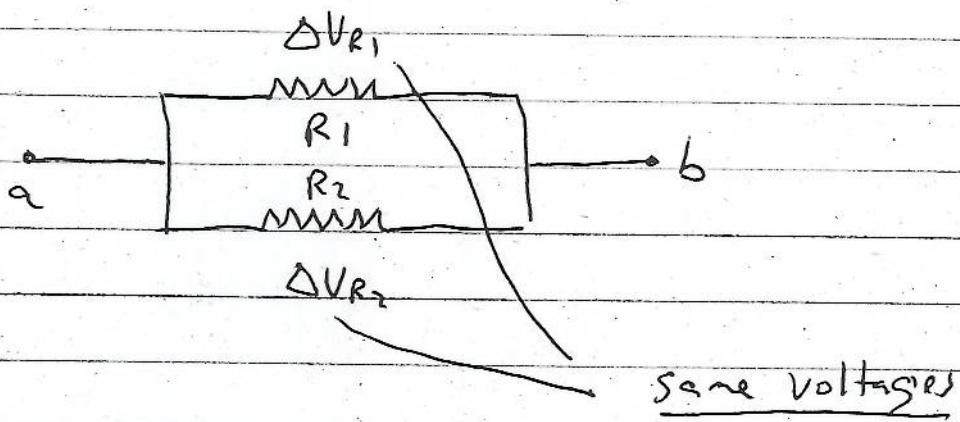


→ conservation of energy

Potential difference b/wn a & b is

path independent.

I_{R_1} not necessarily I_{R_2}

Series

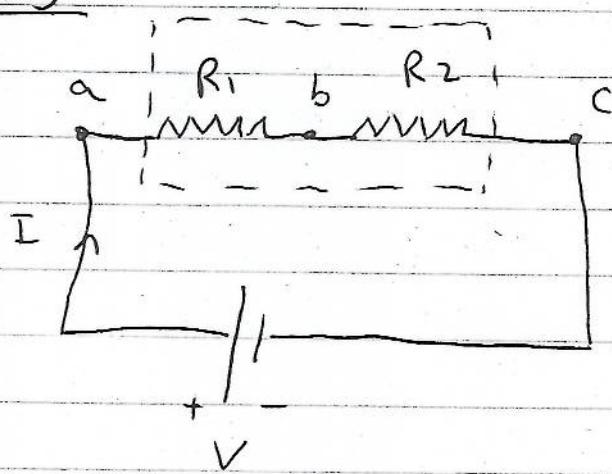

$$\left. \begin{aligned} V_a - V_b &= I R_1 \\ V_b - V_c &= I R_2 \end{aligned} \right\} V_a - V_c = I(R_1 + R_2)$$

Replace $| - - - |$ with Reg


General

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \dots$$

series


Exercise:

Analog computer $\div 2$

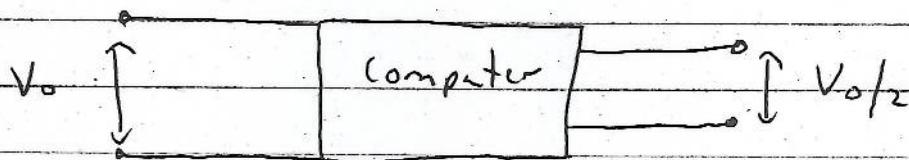

Input # in
form of voltage
 V_o

Output answer:
 $V_o/2$

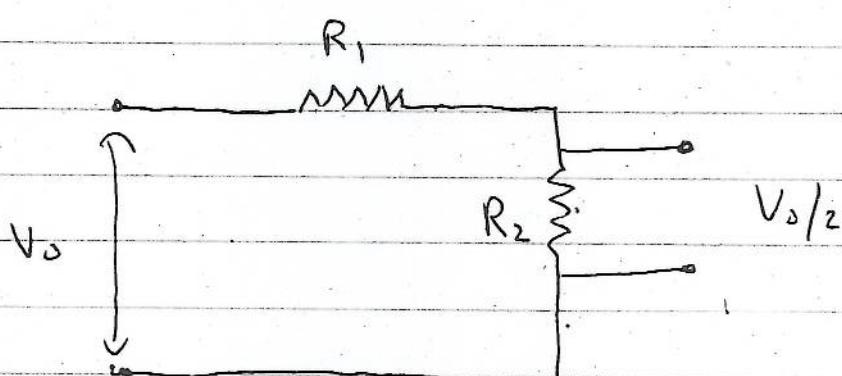


If $R_1 = R_2 = R$

$$V_{R_1} = V_{R_2} = V_o/2$$

$$\begin{array}{c} T \\ | \\ IR \\ | \\ T \\ | \\ IR \end{array}$$

Computer to \div by 4

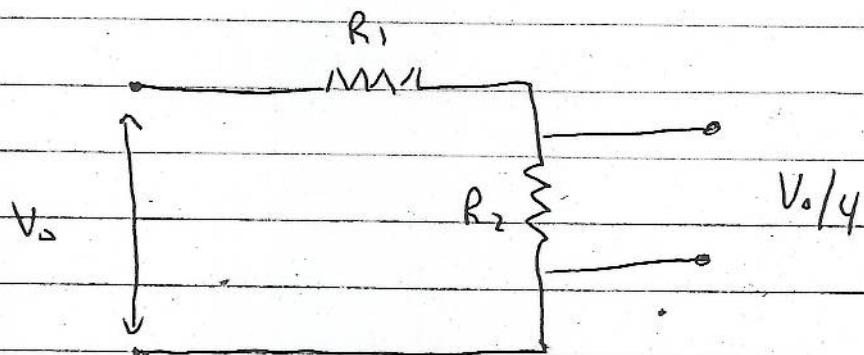


$$V_o = IR_1 + IR_2$$

$$\text{Want } IR_2 = V_o/4$$

$$IR_1 = \frac{3}{4} V_o$$

$$\frac{R_2}{R_1} = \frac{1}{3}$$

Resistors in Parallel

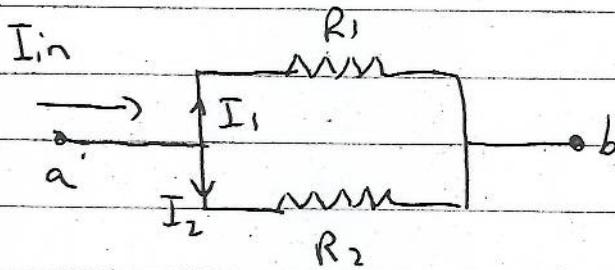

- I_{in} splits into $I_1 \& I_2$
- More goes to path of less resistance

$$I_{in} = I_1 + I_2 = \frac{V_{ab}}{R_1} + \frac{V_{ab}}{R_2} = V_{ab} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

Replace w/ R_{eq}

$$I_{in} = \frac{V_{ab}}{R_{eq}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

General

$$\boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots}$$

resistors in parallel

Note :


Series



$$R_{\text{eq}} = R_1 + R_2$$

R_{eq} bigger than R_1 & R_2


Parallel

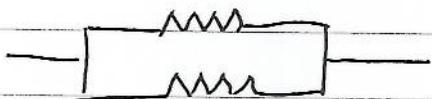


$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

R_{eq} less than both R_1 & R_2
"extra path"

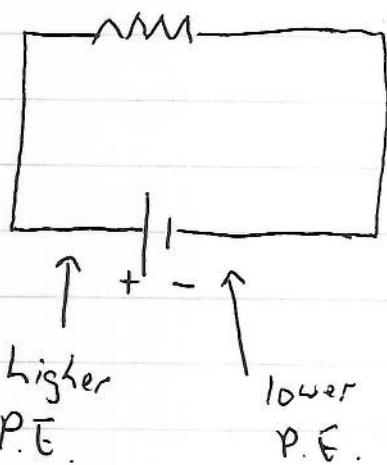Battery - increases P.E. of charges in the circuit



Consider

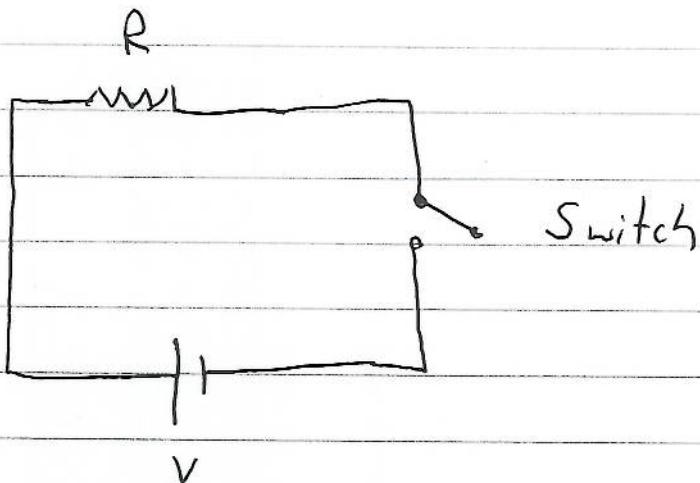

1) Close switch


→ something complicated happens

2) Wait a while

→ circuit attains steady state

$$I = \text{const.}$$


Ideal Battery

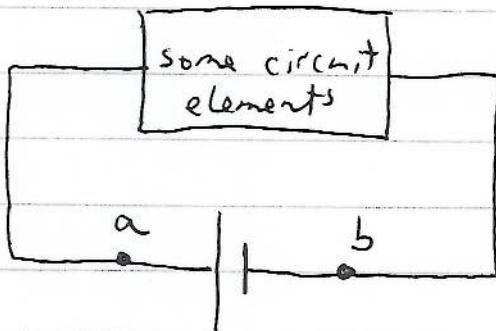

No matter what you do $V_a - V_b = \text{const.}$

Ideal battery is not a constant current source.
It is a constant voltage source.

Real battery (Expt 1)

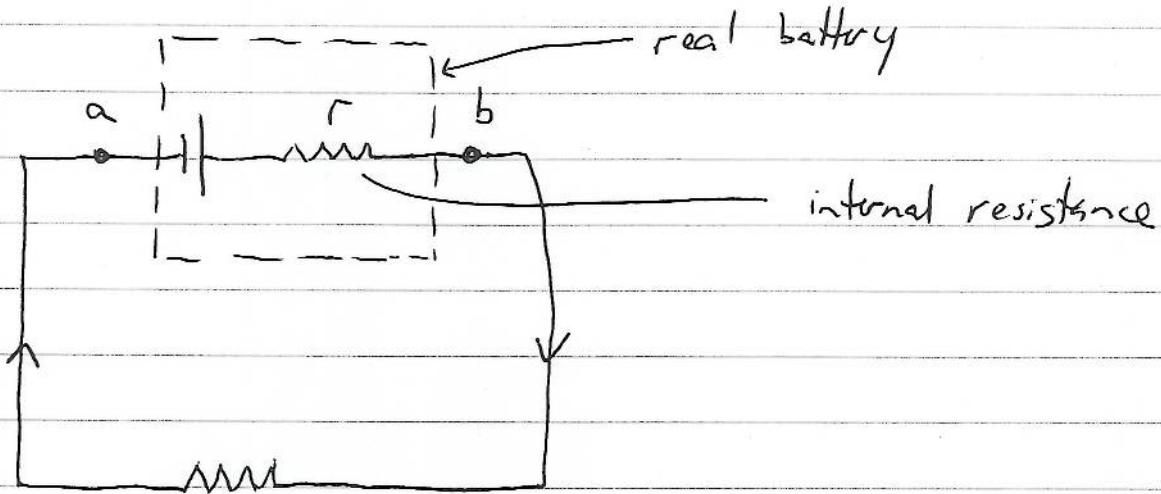

Define

\mathcal{E} : open circuit voltage

→ terminal voltage of battery when $I=0$

$$V_{ab} = \mathcal{E} - Ir$$

potential
across battery

terminal
voltage when
 $I=0$

Voltage drop due
to internal resistance
of battery

r will be measured in Lab #1

Power:

$$\text{Energy} = \text{charge} \times \text{Voltage}$$


$$\text{Power} = \frac{\text{energy}}{\text{time}} = \frac{\text{charge}}{\text{time}} \times \text{Voltage}$$

$$P = 1 \text{ V}$$

$$V = IR$$

$$P = I^2 R = \frac{V^2}{R}$$

The incandescent light bulb


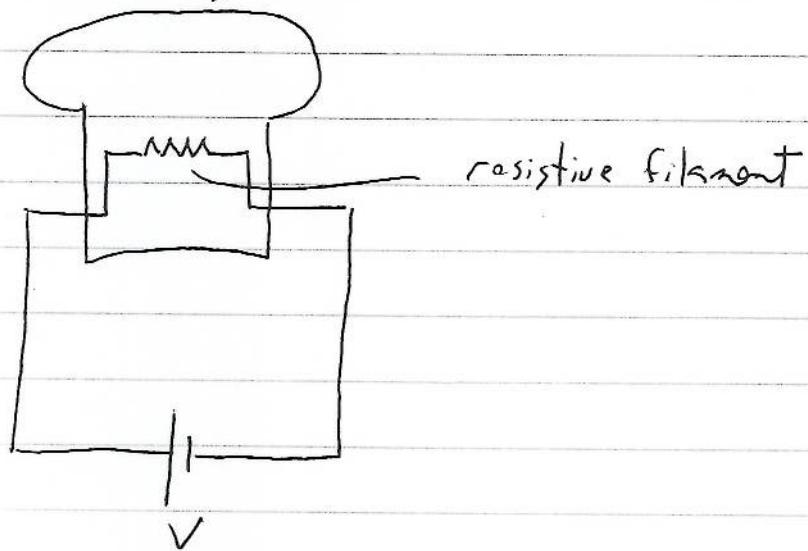


- $P = I^2 R = \frac{V^2}{R}$
- filament heats up
- filament glows

more current \rightarrow more light

Case 1

Compare for identical resistors

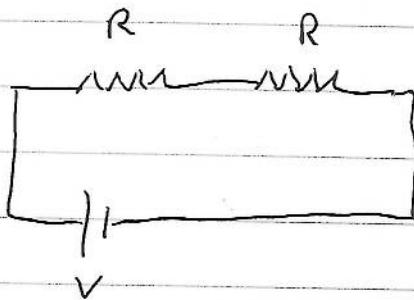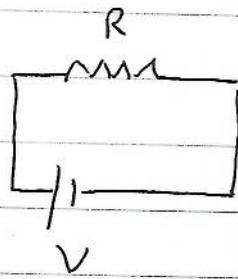



What are the relative brightnesses if each resistor is a lightbulb

$$P = \frac{V^2}{R}$$

$$\frac{(V/2)^2}{R} \quad \left\{ \quad \frac{(V/2)^2}{R}$$


Power down by 4

Case 2

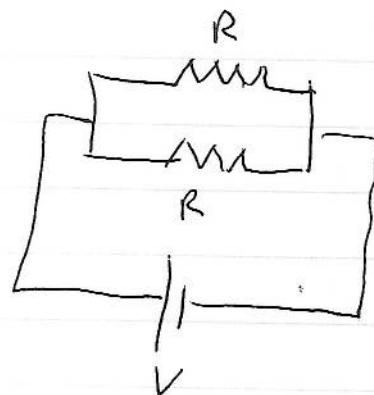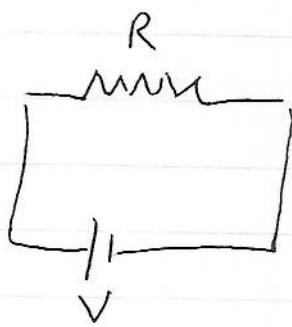


Same V, same power, same brightnesses

Case 3

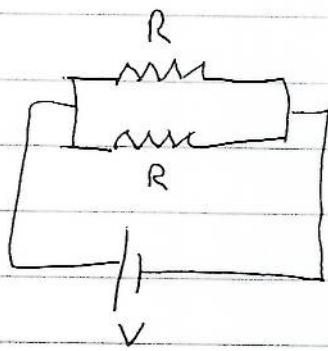


VS

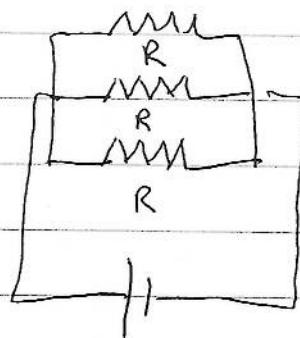


All the same brightnesses

Case 4


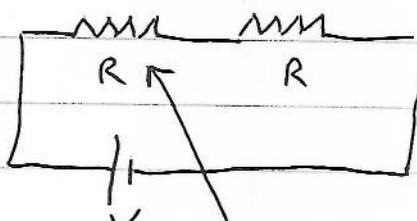


VS

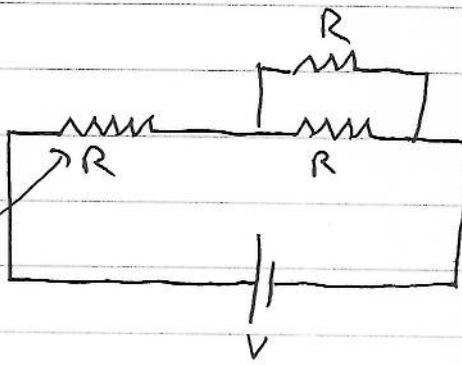


This gets brighter or dimmer?
(brighter)

So far, we can deal with

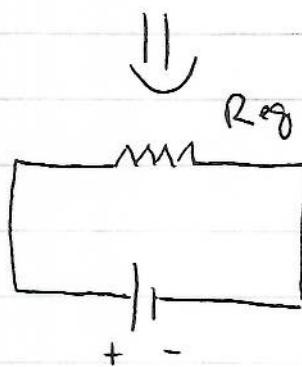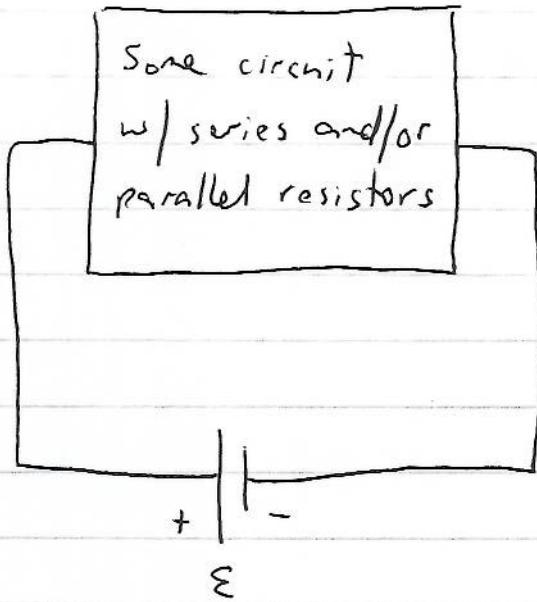


$$R_{eq} = R_1 + R_2$$

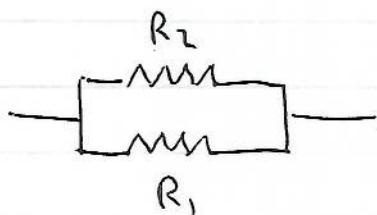


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

But what if?

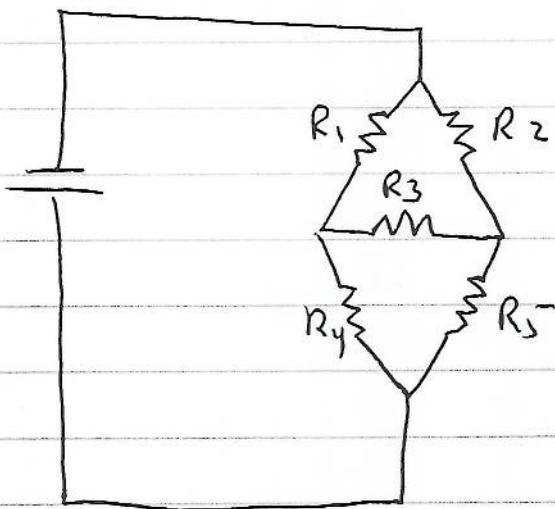

or

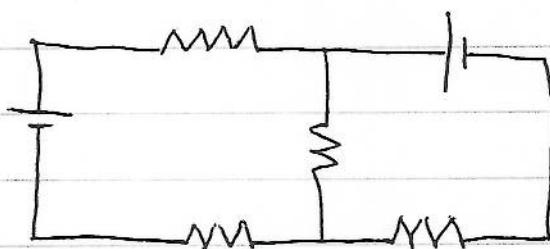


Nothing's in series, nothing's in parallel

New tools: Kirchhoff's Laws

Kirchhoff's Current Law (Junction Rule, node rule)

Sum of currents entering any junction = sum of those leaving. (charge conservation)

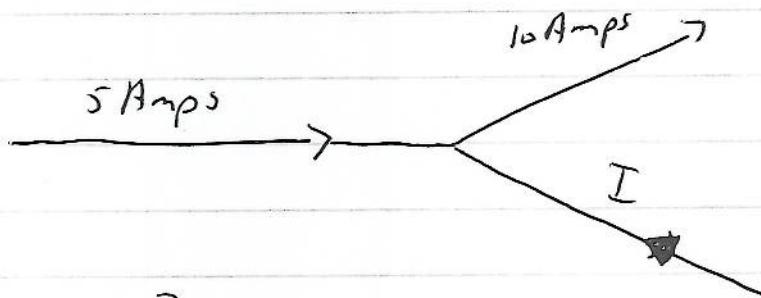
Junction or node - Any point in circuit where current can split.



What is I ?

Kirchhoff's Voltage Law (Loop Rule)

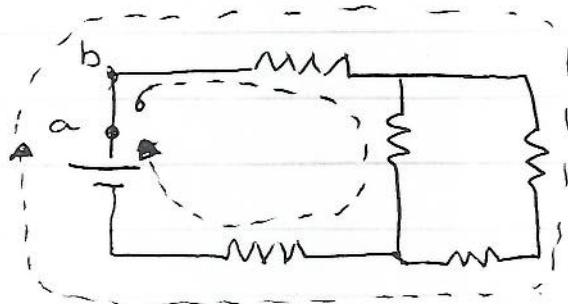The algebraic sum of the changes in potential across all of the elements around any closed loop is zero. (energy conservation)




$$V_a = V_b$$

Stuff to know:

If you go around loop and


- 1) Cross a resistor with the current

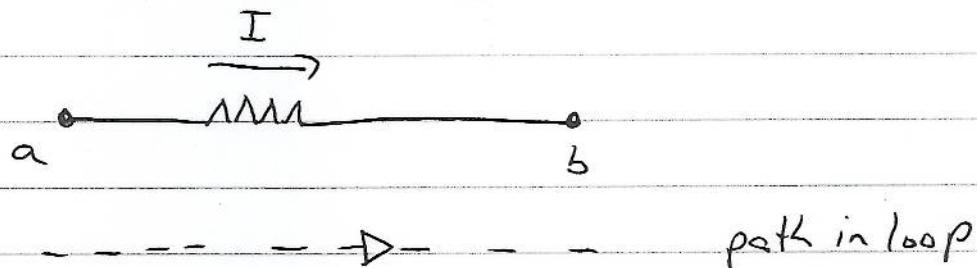

Voltage (potential) drops

$$V_b - V_a = -IR$$

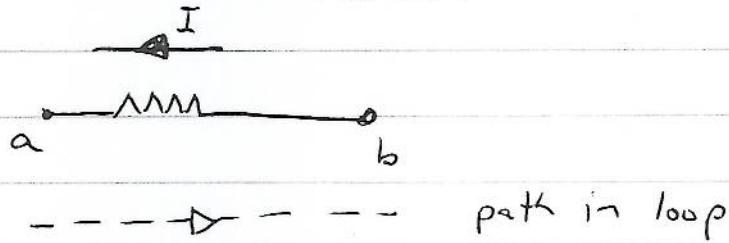
- 2) Cross a resistor against the current



Voltage increases

$$V_b - V_a = +IR$$

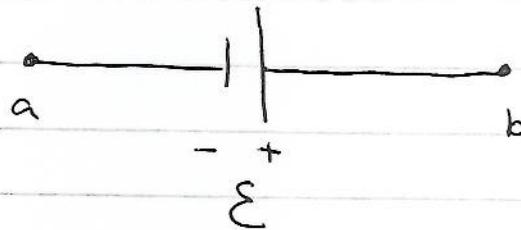- 3) Cross a source of emf in the direction of the emf,
i.e. from - to +




----- \Rightarrow ----- path in loop

Voltage increases

$$V_b - V_a = + \mathcal{E}$$

(For ideal emf, current direction does not matter)

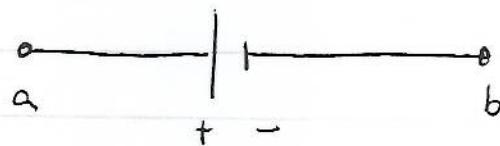- 4) Cross a source of emf opposite to direction of emf,
i.e. from + to -



----- \Rightarrow ----- path in loop

Voltage decreases

$$V_b - V_a = - \mathcal{E}$$

General approach to circuit analysis

1) Draw diagram, labeling R's & emfs

2) Simplify circuit where possible

series } resistors \rightarrow Reg
parallel }

3) Apply junction rule

- Label currents $I_1, I_2, I_3 \dots$

- Draw arrows for directions. If you don't know direction of a current, assume one. If final sign of current is +, you guessed correctly. If -, no problem.

4) Apply loop rule.


- Stick with assumed signs of currents

- keep applying loop rule until you have as many independent equations as unknowns.

5) Solve simultaneous equations.


Example 1:

26

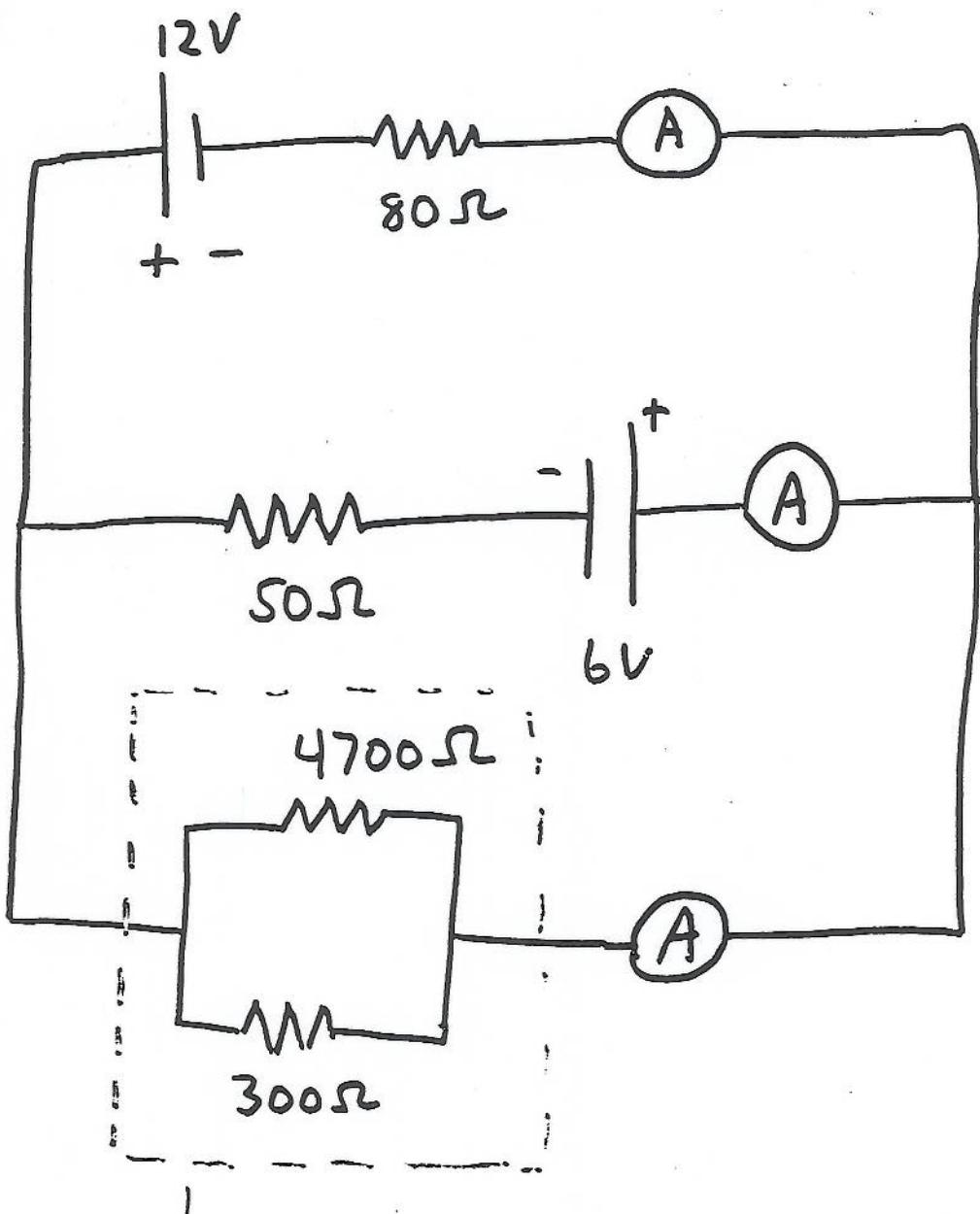

$$\frac{1}{R_{eq}} = \frac{1}{4700\Omega} + \frac{1}{300\Omega}$$

$$R_{eq} = 282\Omega$$

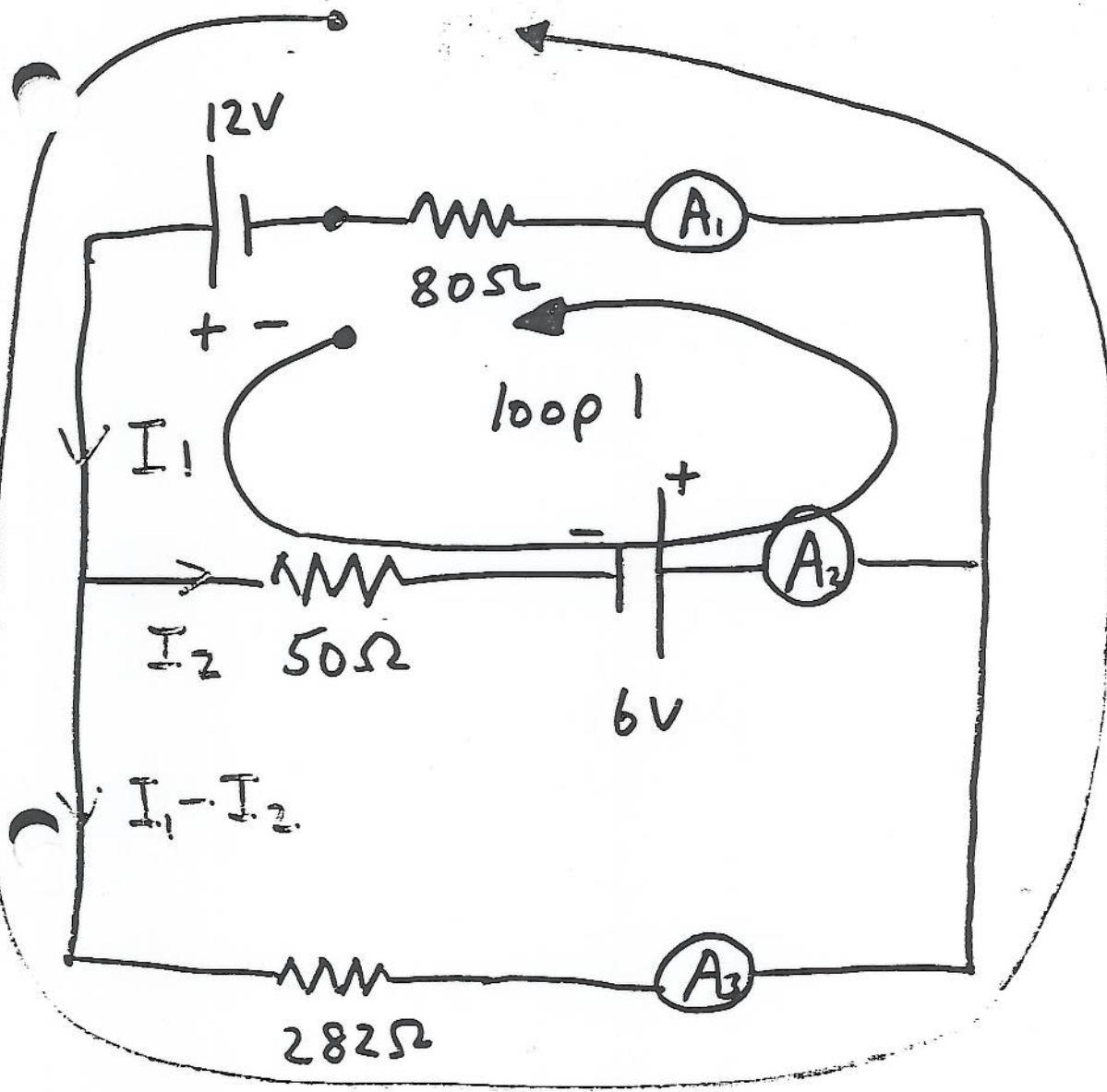

Loop 1

$$12V - I_2 \cdot 50\Omega + 6V - I_1 \cdot 80\Omega = 0$$

$$18V - I_2 \cdot 50\Omega - I_1 \cdot 80\Omega = 0$$

$$\Rightarrow I_2 = \frac{1}{50\Omega} (18V - I_1 \cdot 80\Omega)$$

Loop 2

$$12V - (I_1 - I_2)282\Omega - I_1 80\Omega = 0$$

$$12V + I_2 282\Omega - I_1 362\Omega = 0$$

$$12V + \frac{1}{50\Omega} (18V - I_1 80\Omega) 282\Omega - I_1 362\Omega = 0$$

$$113.52V - I_1 813.2\Omega = 0$$


$$I_1 = 0.1396$$

$$I_2 = \frac{1}{50\Omega} (18V - I_1 80\Omega) = 0.1366$$

$$I_1 - I_2 = 0.003 \text{ Amps}$$

Ex-2: Without power dissipation must R_3
be able to tolerate?

29

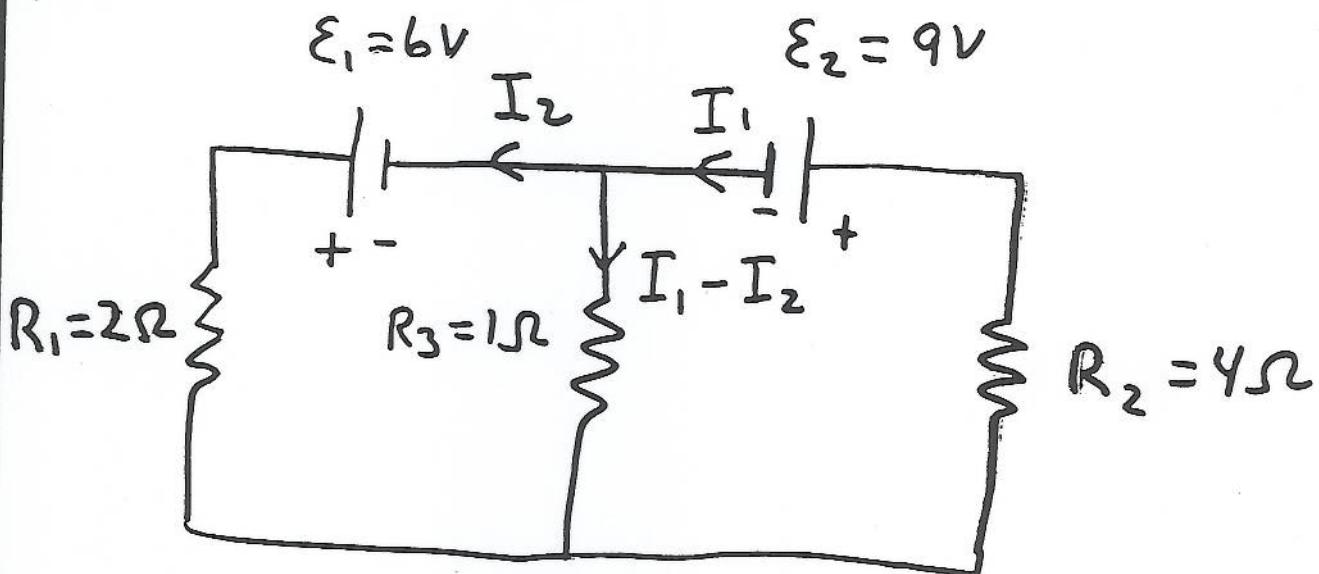

\mathcal{E}_2 is the biggest emf.

Deliberately pick I_1 in the "wrong" direction.

Loop 1

$$-9V + 6V - I_2 2\Omega - I_1 4\Omega = 0$$

$$I_1 = \frac{1}{4\Omega} (-3V - I_2 2\Omega)$$

29

Loop 2

30

$$6V - I_2 2\Omega + (I_1 - I_2) 1\Omega = 0$$

$$6V - I_2 3\Omega + I_1 1\Omega = 0$$

$$6V - I_2 3\Omega + \frac{1\Omega}{4\Omega} (-3V - I_2 2\Omega) = 0$$

$$I_2 (3.5\Omega) = 5.25$$

$$I_2 = 1.5 \text{ Amps}$$

$$I_1 = -1.5 \text{ Amps}$$



minus sign says we assumed
"wrong" direction for current


$$I \text{ in } R_3 = I_1 - I_2 = -3 \text{ Amps}$$

$$P_3 = I^2 R_3 = 9 \text{ Amps}^2 1\Omega = 9W$$

Thevenin's Theorem (Expt 2)

Phil-
skip Trevenin

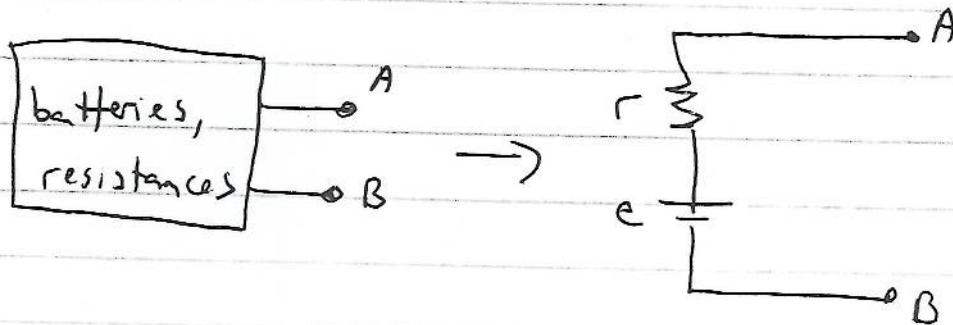Any branch of batteries & resistances w/ two terminals
 → ideal battery (e) in series w/ one
 resistance r



$$V_{AB} = e - Ir$$

1) e is V_{AB} when $I=0$ (open circuit voltage)


2) We now know e (just a constant voltage)

In principle, can connect a wire to A & B (short them out). $V_{AB}=0$

$$r = \frac{e}{I_{\text{short circuit}}}$$

Shorting A \nparallel B can be dangerous

In practice

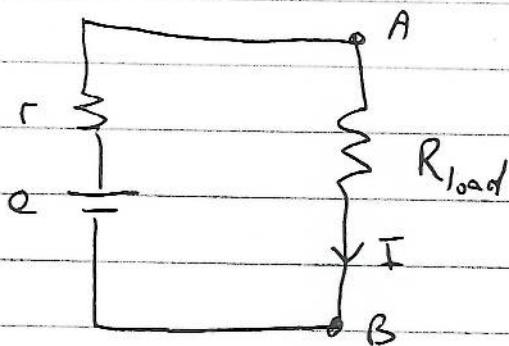



1) Measure e for open circuit
(or R_{load} very large)

2) measure V_{AB} and I for some finite R_{load}

$$r = \frac{e - V_{AB}}{I}$$

Example:


Use Thévenin's Thm to find $I_{3\Omega}$

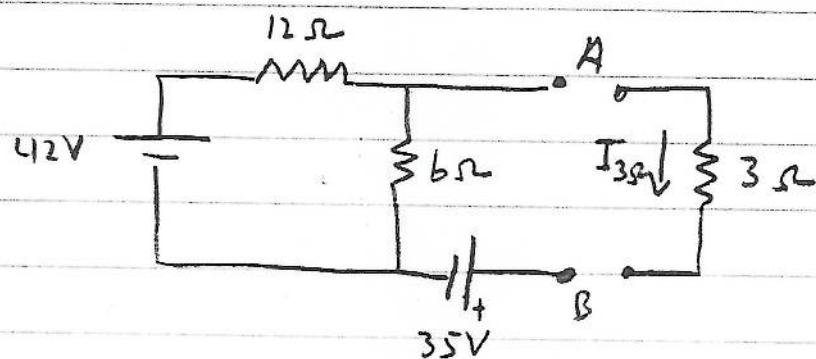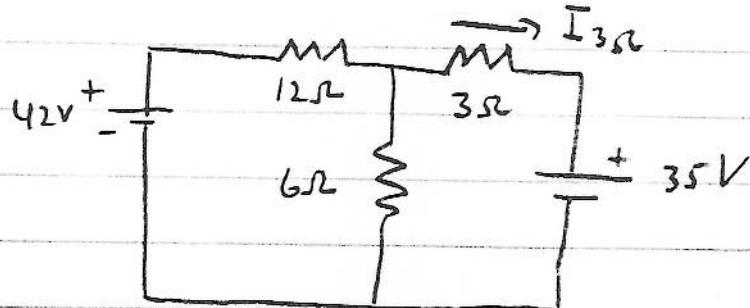

$$V_{Th} = \frac{42V}{12\Omega + 6\Omega} \cdot 6\Omega = 14V$$

$$V_{oc} = 14V - 35V = -21V$$

Short circuit

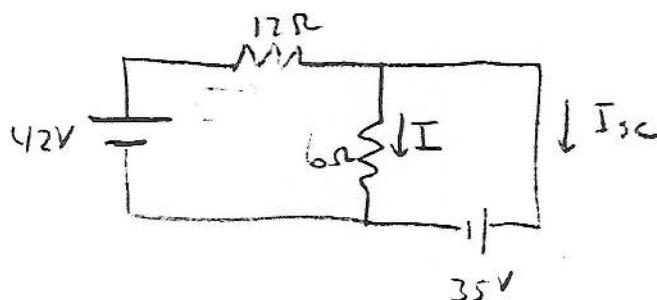

$$42V - (I + I_{sc})12\Omega - 12\Omega = 0$$

$$42V - 12I - 12I_{sc} = 0 \quad \textcircled{*}$$

$$42V - (I + I_{sc})12\Omega - 35 = 0$$


$$7V - 12I - 12I_{sc} = 0 \quad \textcircled{**}$$

$$35V - 6I = 0$$

$$I = \frac{35}{6}$$

$$I_{sc} = \frac{7V - 12 \frac{35}{6}}{12} = \frac{7V - 70V}{12} = \frac{-63}{12} = -\frac{21}{4} A$$
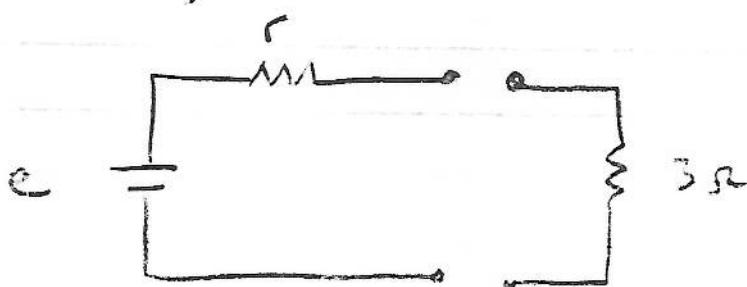
$$r = \frac{V_{oc}}{I_{sc}} = \frac{-21}{-21/4} = 4\Omega$$




$$e = I(r + 3\Omega)$$

$$-21V = I \cdot 7\Omega$$

$$I = -3 \text{ Amps}$$

AC Circuits

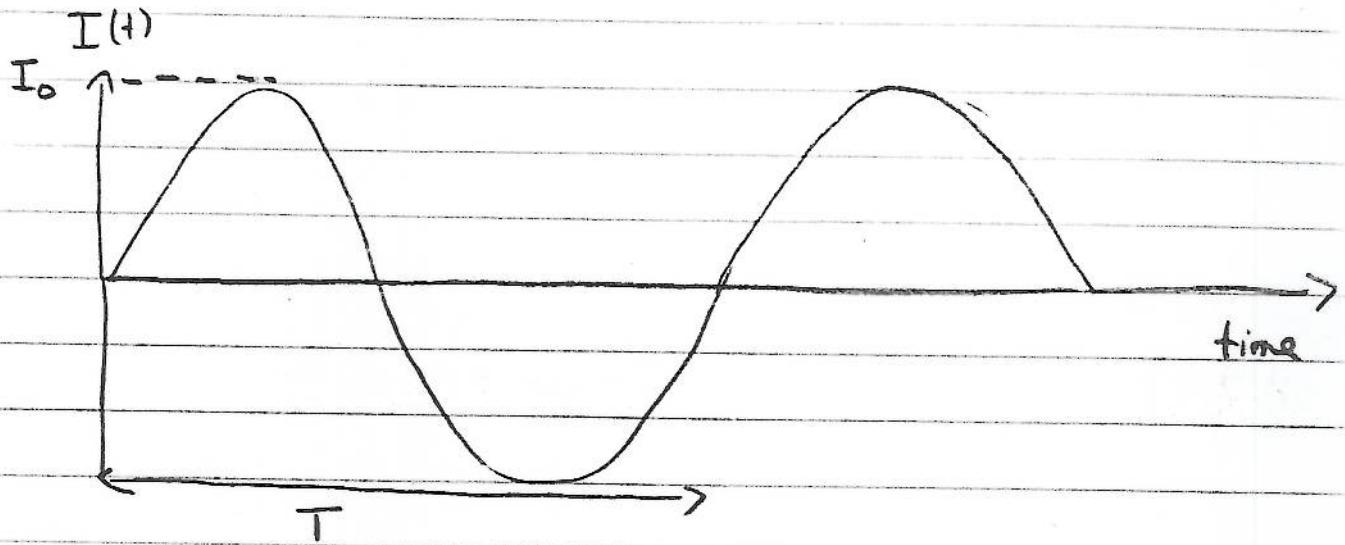

$$I(t) = I_0 \sin \omega t$$

T : period

f : frequency $f = \frac{1}{T}$ ← Hz, 1/sec

w : angular frequency $\omega = 2\pi f$

\uparrow
radians
 sec

I₀ : amplitude

2I₀ : peak-to-peak amplitude

Average of a sine wave:

$$\int_0^T \sin \omega t = 0$$

useless.

Instead, use root-mean-square


- 1) square it
- 2) average it
- 3) take the square root

$$V_{rms} = \left[\frac{1}{T} \int_0^T V^2(t) dt \right]^{1/2}$$

[always +]

$$V(t) = V_0 \sin \omega t$$
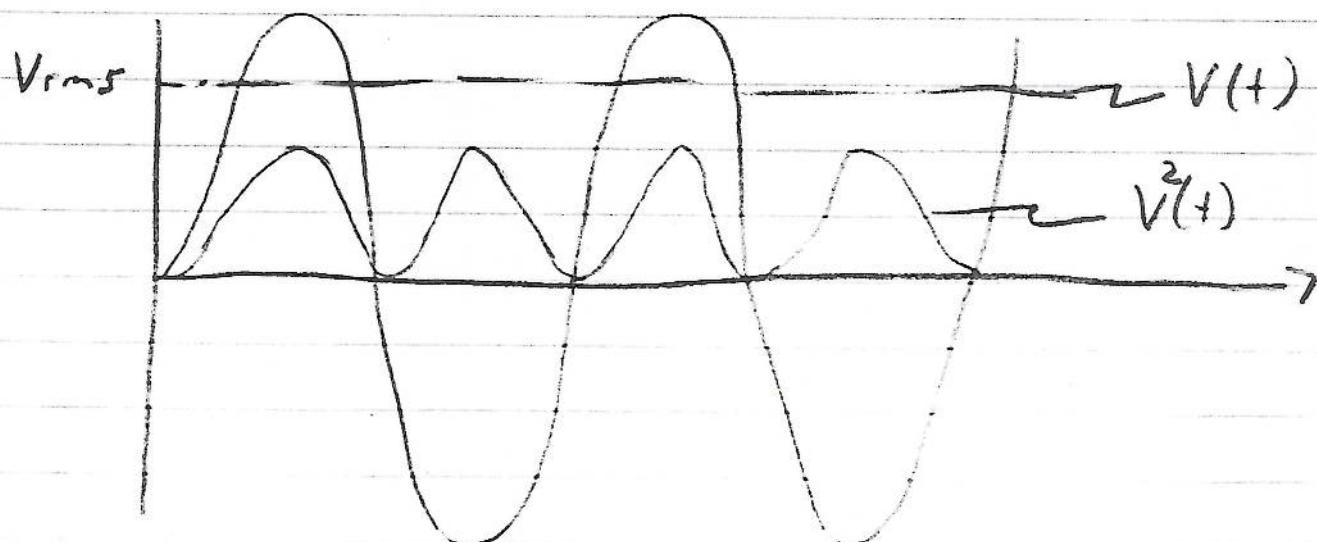
$$V_{rms} = \left[\frac{1}{T} \int_0^T V_0^2 \sin^2 \omega t dt \right]^{1/2} = \frac{V_0}{\sqrt{2}} = 0.707 V_0$$




Cool thing about rms:


→ Can solve AC circuits without carrying around time dependences

X

Phase (same frequency)

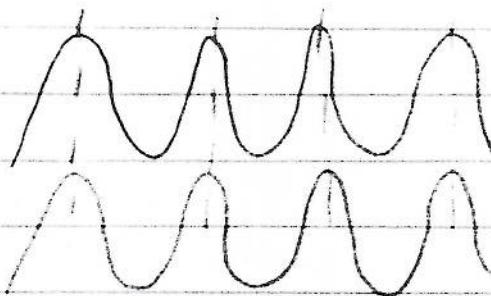

in phase

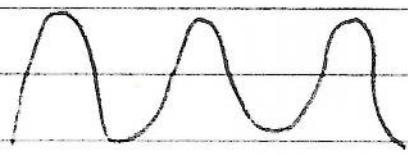

180° out of phase




$$v(t) = V_0 \sin(2\pi ft + \varphi)$$

in phase


$$V_0 \cos \omega t = V_0 \sin(\omega t + \pi/2)$$

eable AC Power

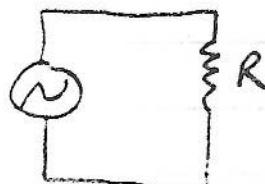

$$i(t) = \frac{v(t)}{R} = \frac{V_0 \cos \omega t}{R} = I_0 \sin \omega t$$

$I \& V$ are in phase

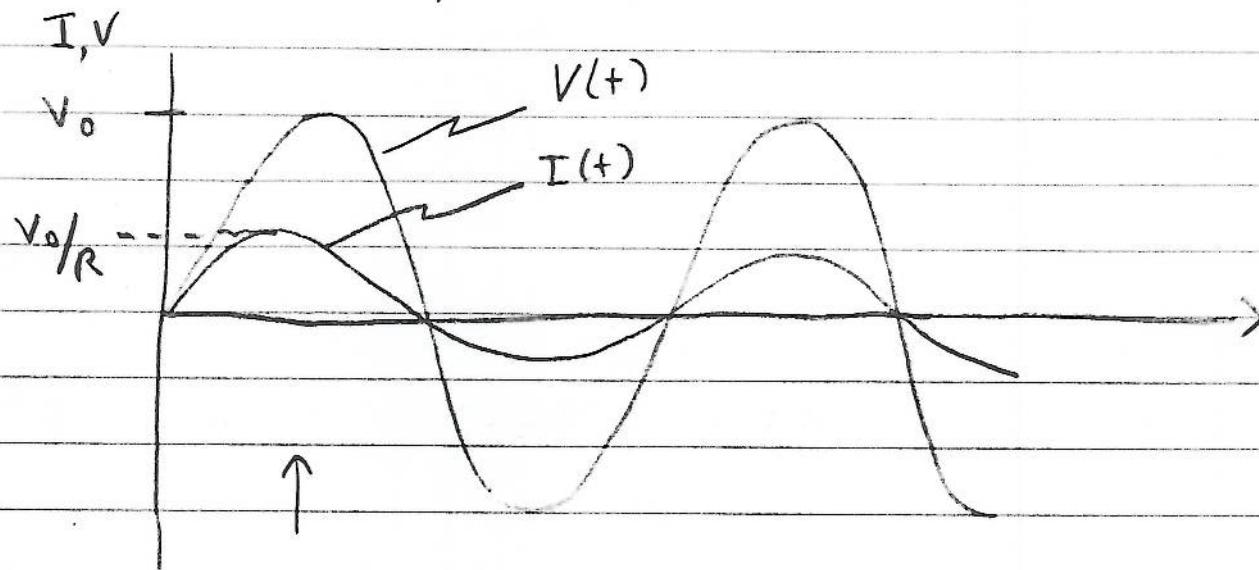

Peak at the
same time

$$P(t) = [i(t)]^2 R = I_0^2 R \sin^2 \omega t$$

$$P_{\text{ave}} = \frac{I_0^2 R}{2} = \frac{V_0^2}{2R}$$

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$$

$$P_{\text{ave}} = \frac{V_{\text{rms}}^2}{R} \quad \text{just like } \frac{V^2}{R} \quad \text{but } P \rightarrow P_{\text{ave}} \\ V \rightarrow V_{\text{rms}}$$