

R_{12} is always less than R_1 . Why?

$$\tau' = \frac{R_2}{R_1 + R_2} \tau_{in}$$

$$\tau' < \tau.$$

Semiconductor Physics



Types of matter


gas - atoms interact only via hard collisions

liquid - weak interaction

plasma - ionized gas


solid - rigid lattice

crystal

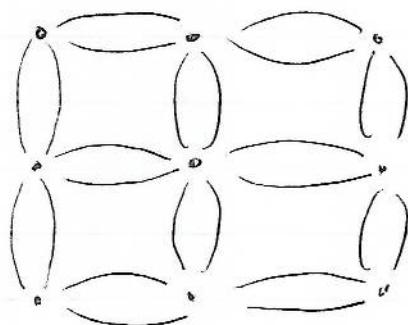




amorphous - not regular pattern

Potential energy of electron in crystal

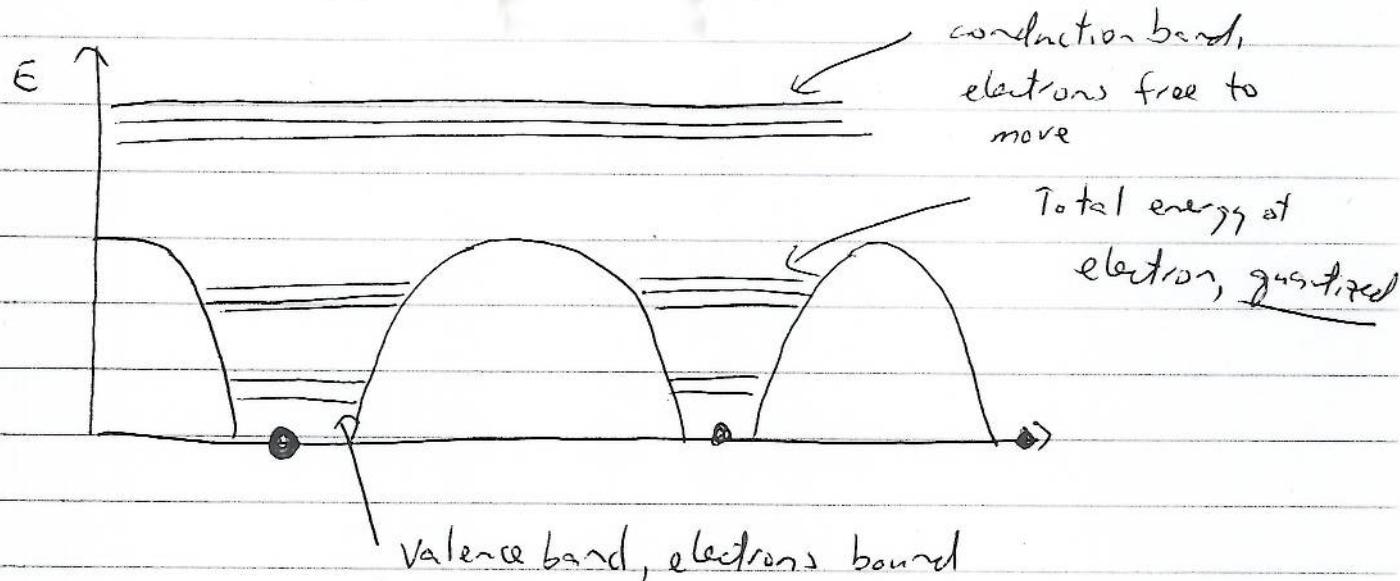

Quantization:

Consider a string with both ends fixed

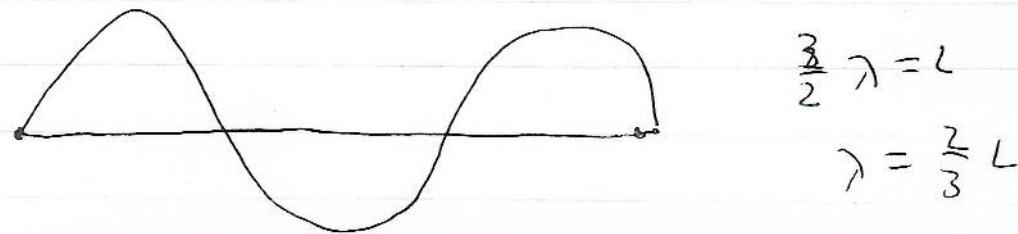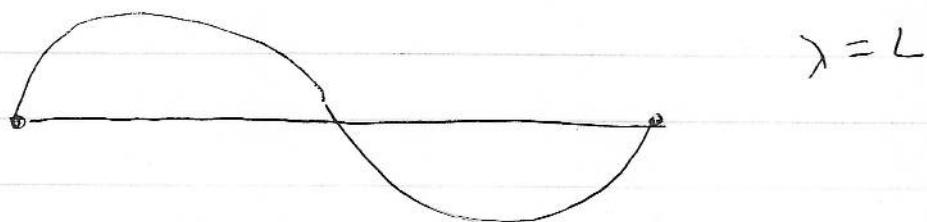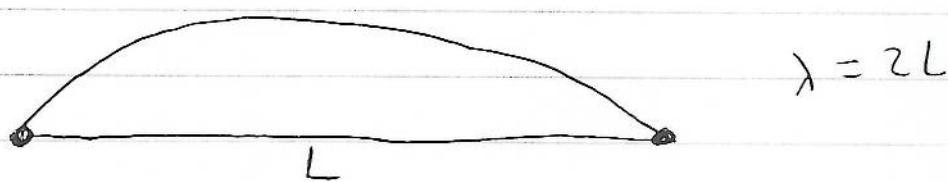

Never have $\lambda = 3.1415 L$.

Electrons are fermions


fermions: spin $1/2, 3/2, 5/2$

No two can occupy the same state

bosons: spin $0, 1, 2, 3$

Can occupy the same state

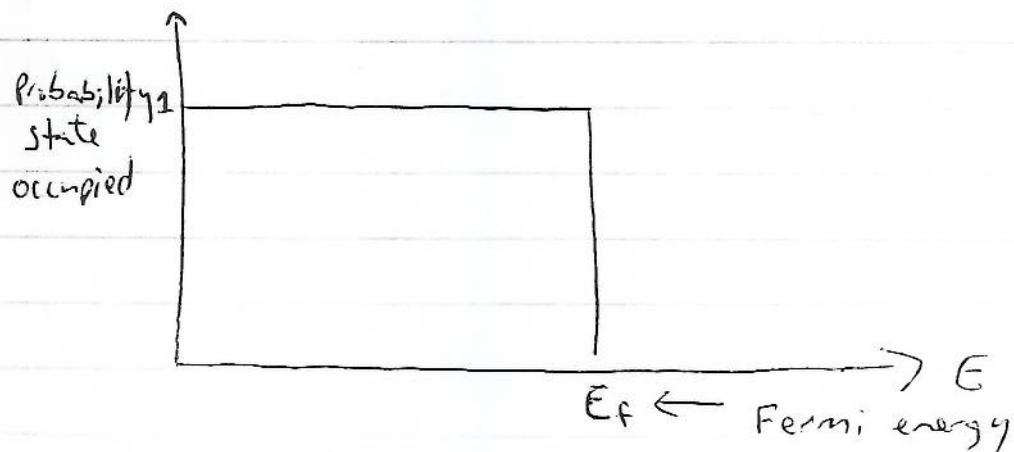④ At low T , electrons fill lowest states first



At $T \neq 0$, electrons not all packed in lowest levels



Careful treatment

Probability a state occupied:

$$F(E) = \frac{1}{e^{(E-E_f)/kT} + 1}$$


k : Boltzmann's constant

at room temp $kT \approx \frac{1}{40}$ eV

Number of electrons in a range $[E, E+dE]$

$$\oplus \quad N(E)dE = \rho(E) dE F(E)$$

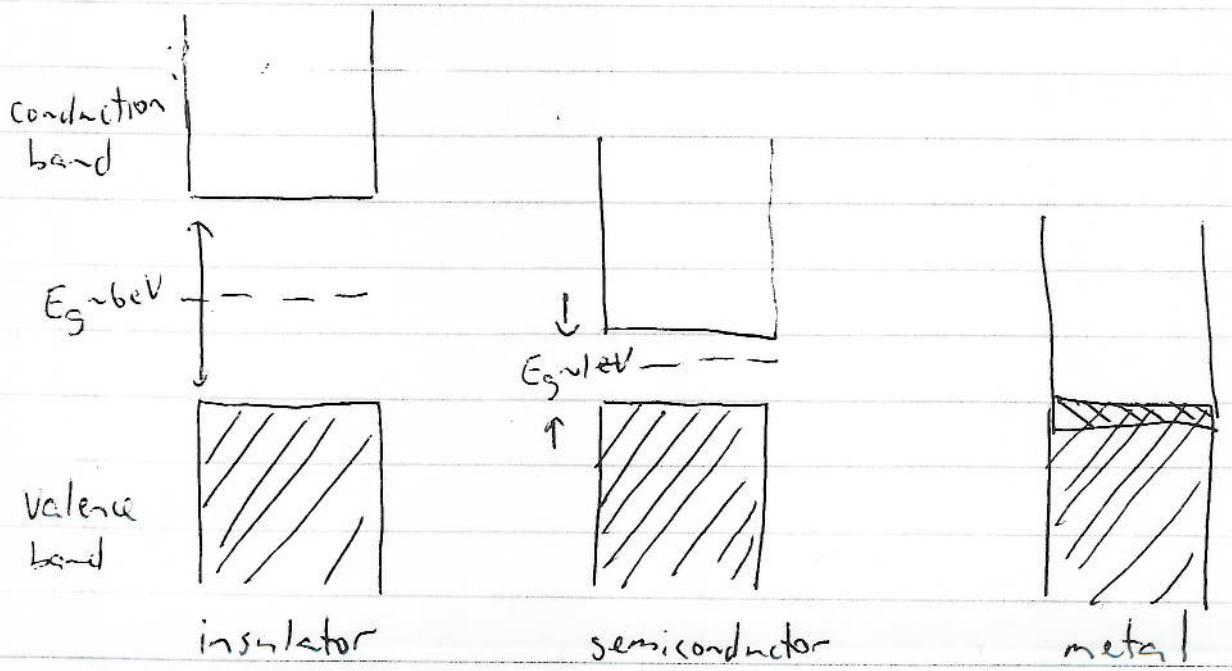↑
 number of states per unit energy
 ↑
 Probability they are occupied




~~(X)~~


93

Define $E = 0$ at top of valence band

$$\rho(E) \propto (E - E_{gap})^{1/2}$$


Semiconductor at finite T

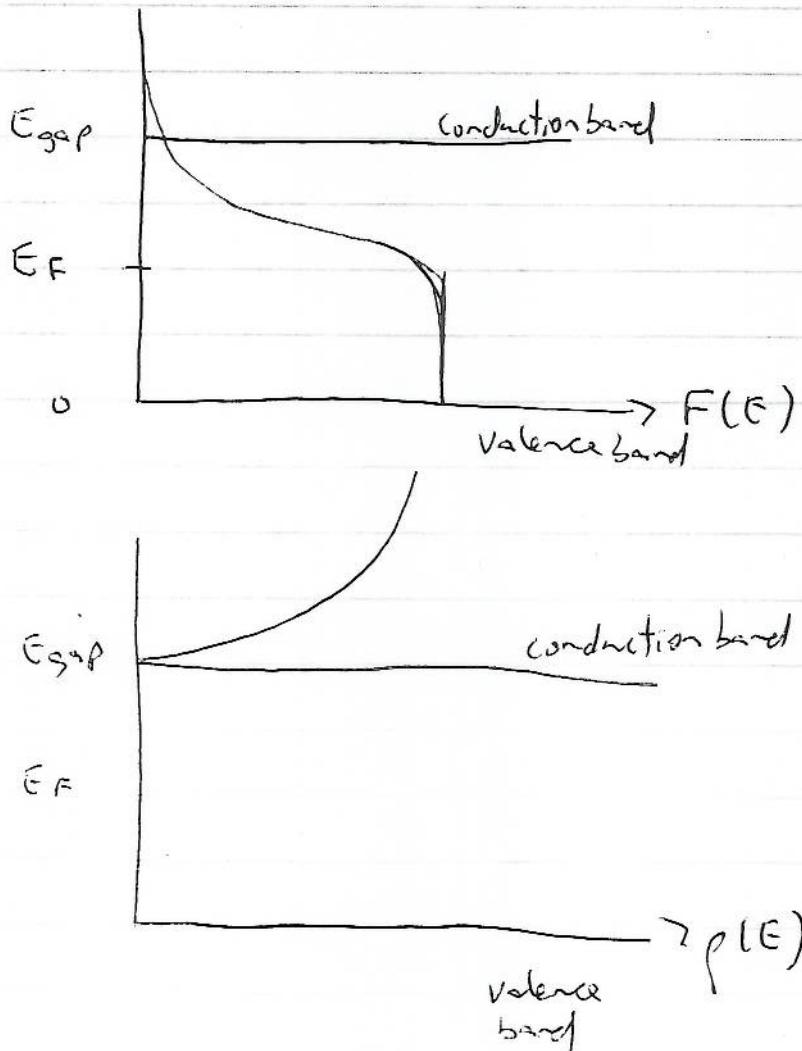

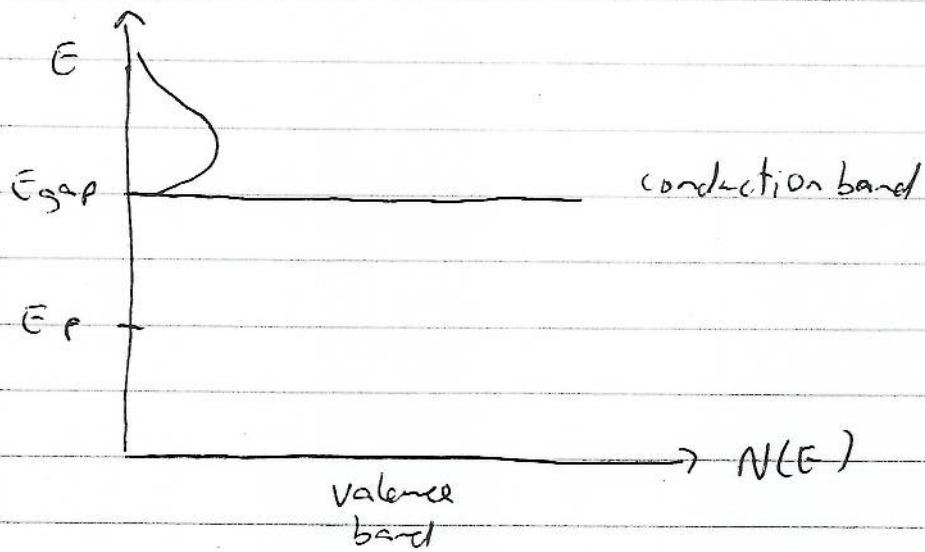


Doping

Insert carriers into lattice

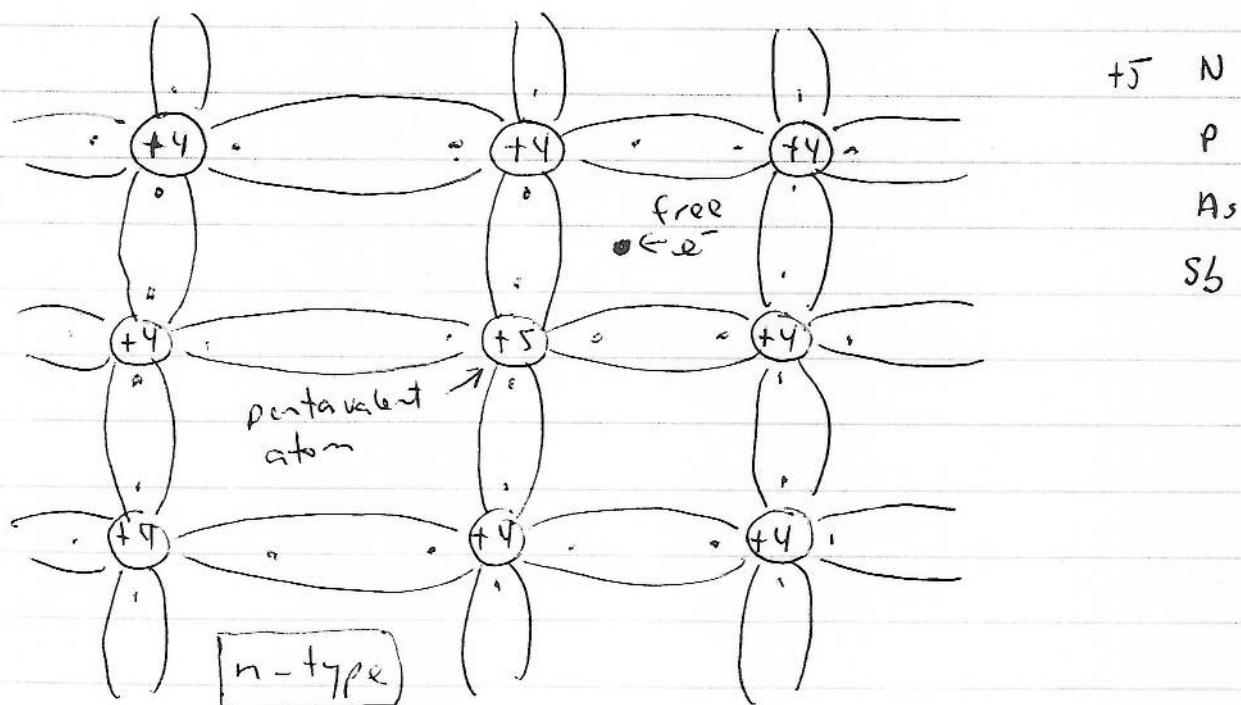


- carriers

n-type

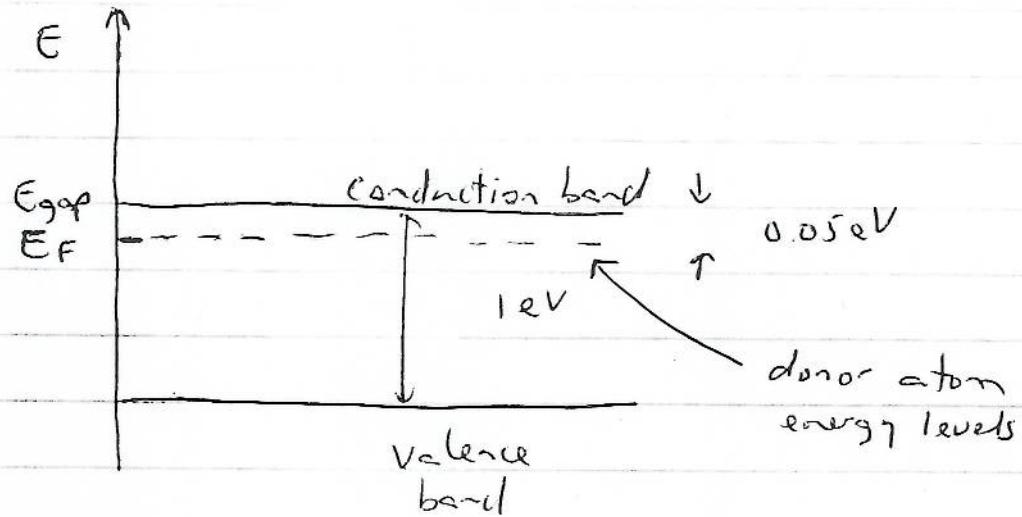


P-type

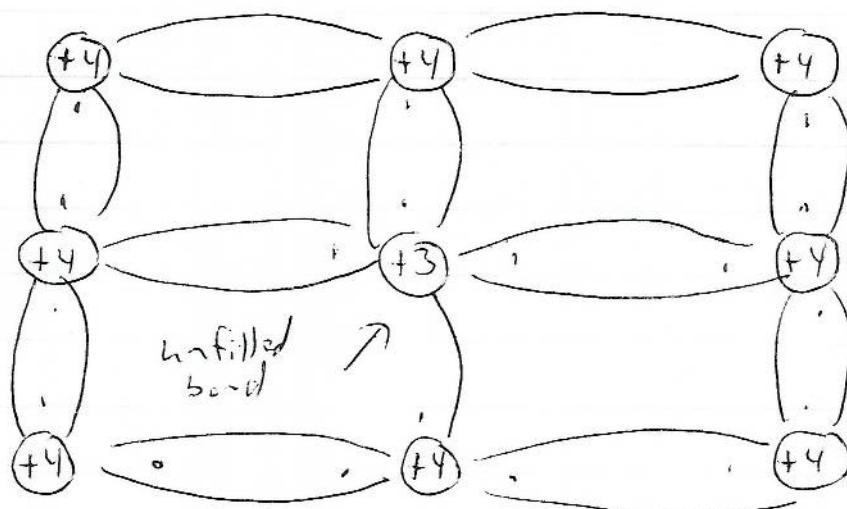

+ carriers (holes)


P-type

96

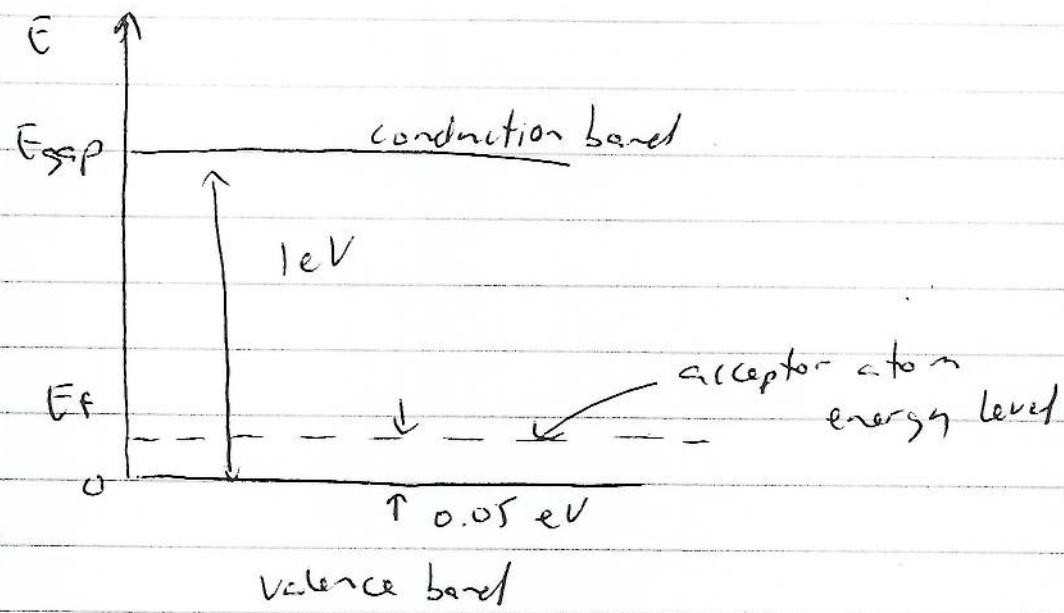

P-N Junctions

Consider an open bottle of perfume

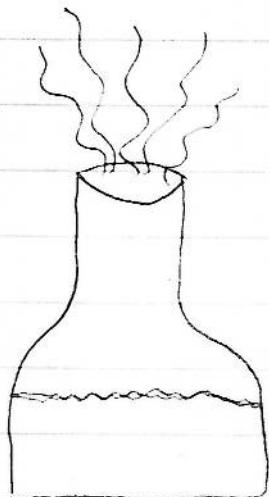

Diffuses from high density to low density

~~97~~


97

N-type




total charge = 0, but \ominus can move

P-type

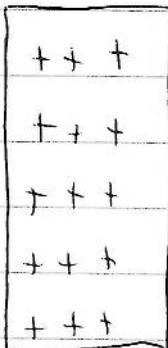

total charge = 0, but \oplus can move

Put them together

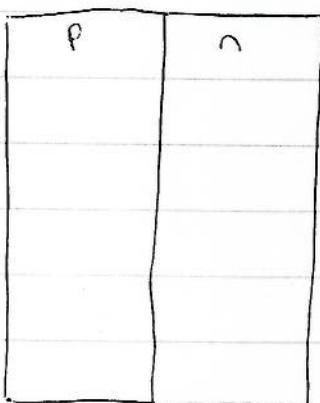


$\leftarrow \ominus$

$\oplus \rightarrow$


$\leftarrow F$

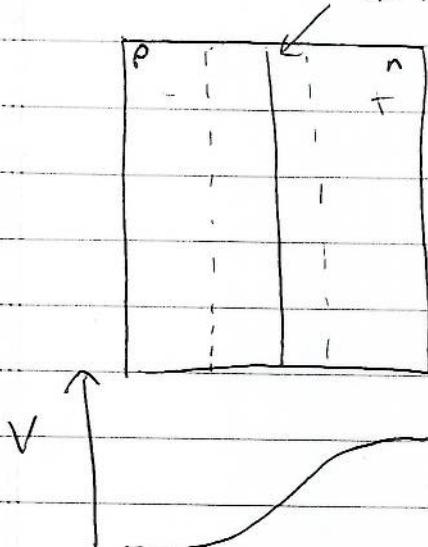depletion region
no free carriers, but charge





⊕ Particle easily flows \leftarrow , but not \rightarrow

Open circuit

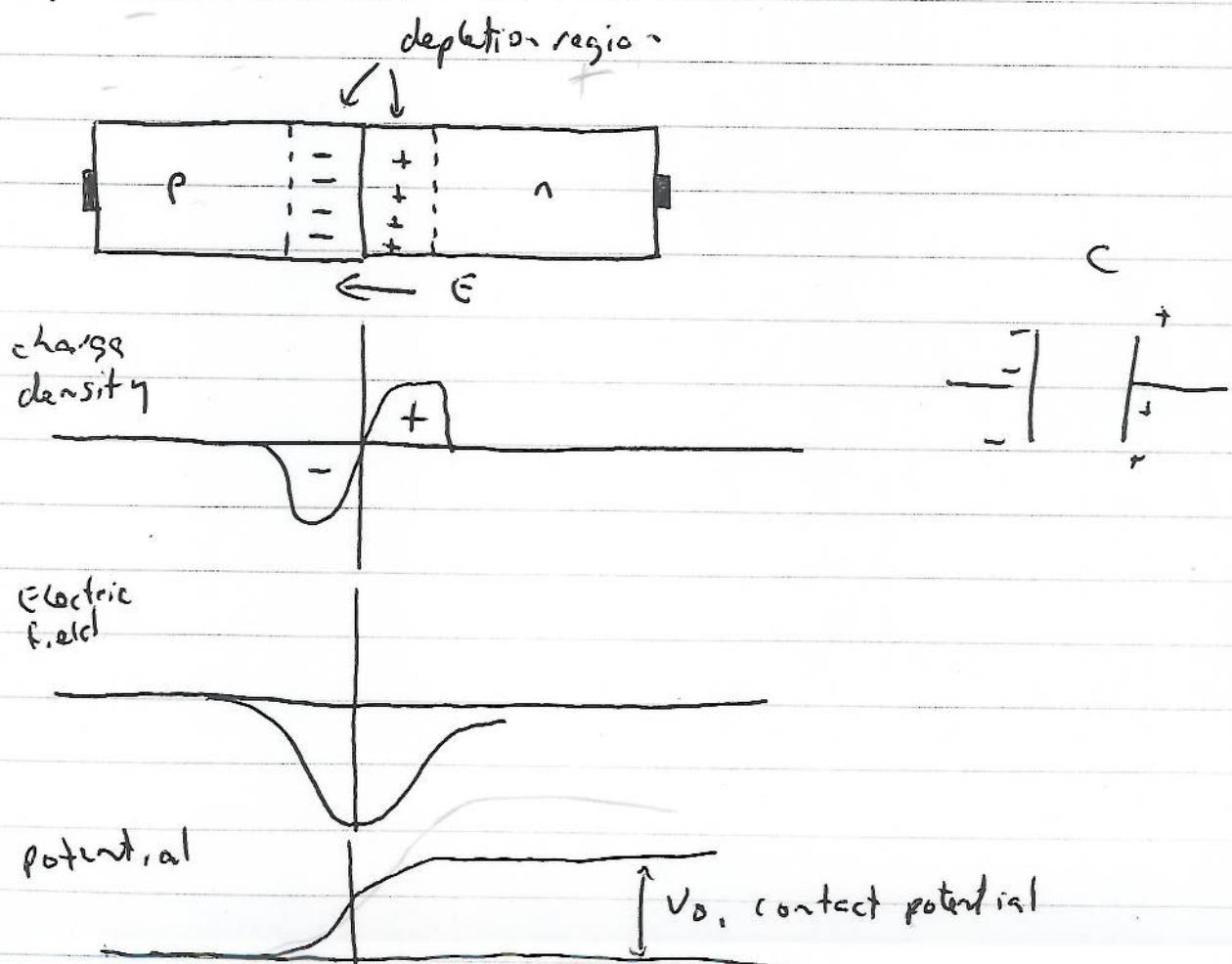

Diode acts as one-way valve for current



Reverse bias

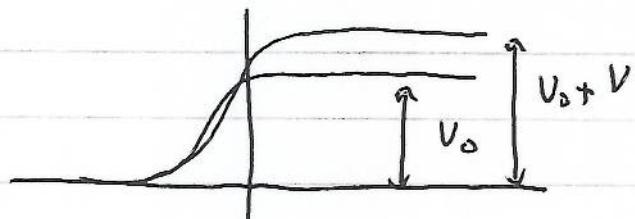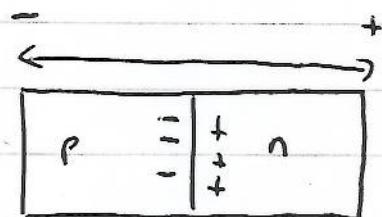

- Bigger depletion region
- P side + charges can move - see large potential barrier
- " "
- " "

Need kinetic energy $> e(V_d + V)$ to conduct
Temperature dependent.

Forward bias

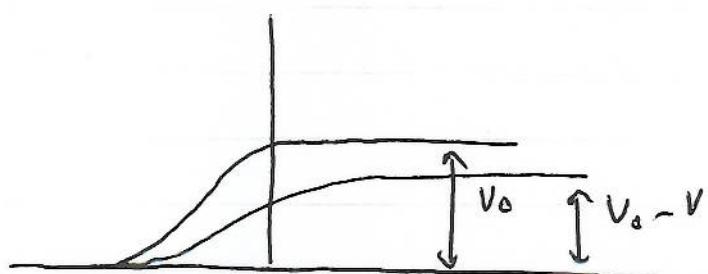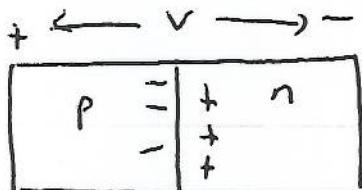


- Potential barrier decreased
- Depletion region decreased
- When $V > V_0 \rightarrow$ conduction


$V_0 \sim 0.5V$ for Si . Depends on T

$$I = \frac{V - V_{\text{turnon}}}{R} \quad R: \text{external resistance}$$


Recall Ohms law

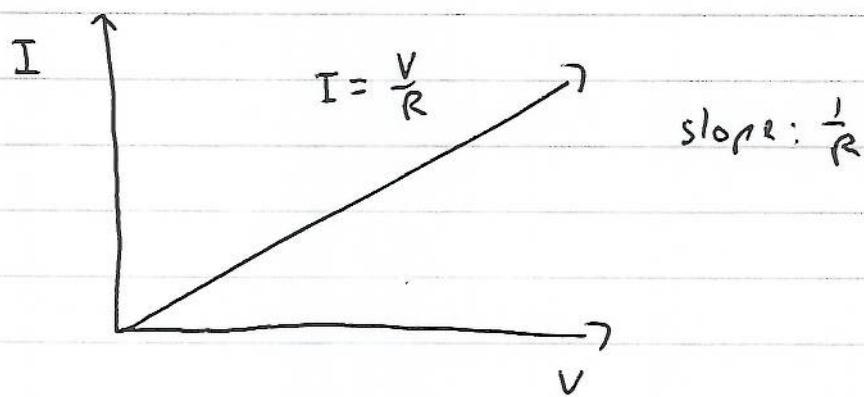

Now we have

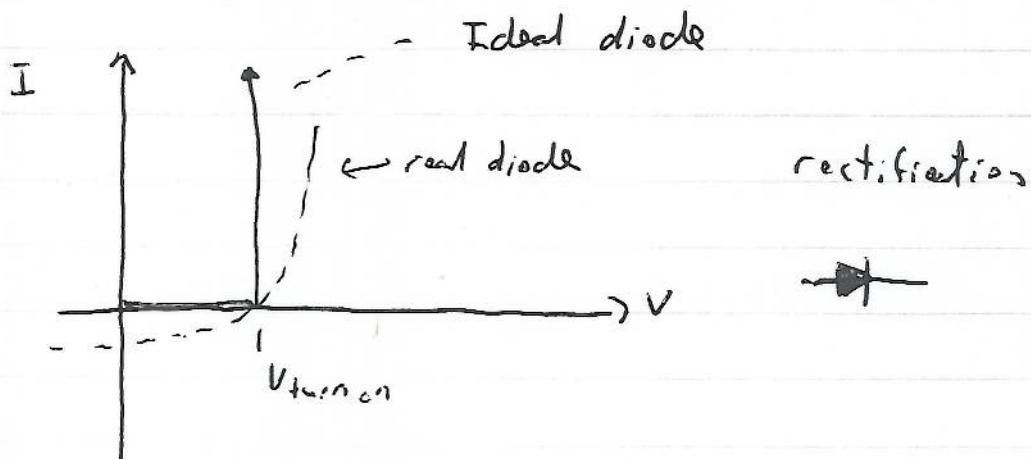

Energy level picture

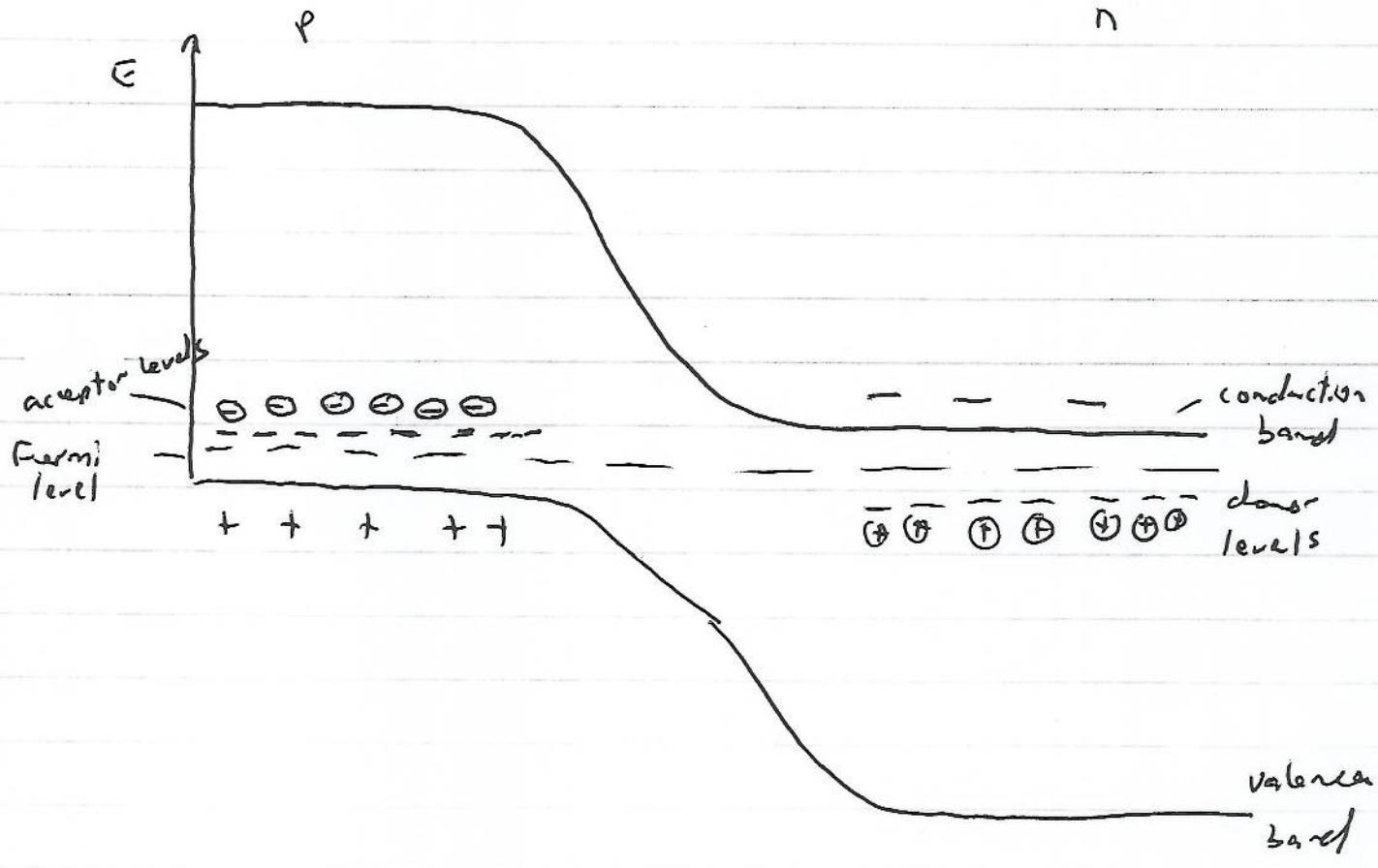

$p + \gamma/\alpha$

n type



Electrons in C.B can't move \leftarrow

Holes in V.B can't move \rightarrow

Zener diode (avalanche, reference, breakdown diode)

Reverse bias:


Recall

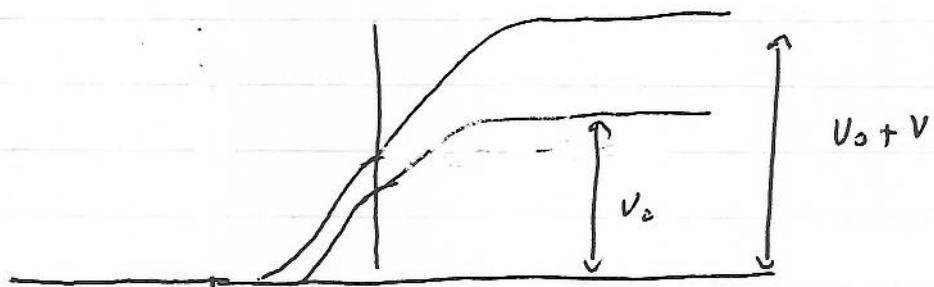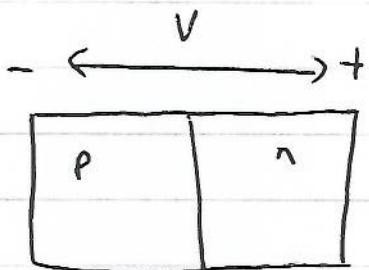

E


$$E = -\nabla V$$

bigger

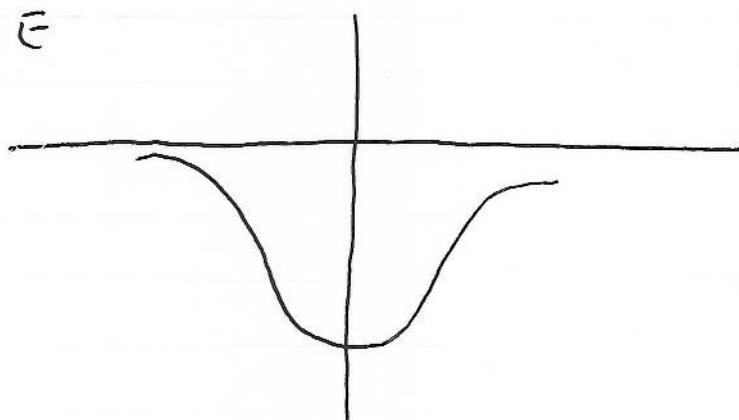


e^- 's pulled out of covalent bonds (ionized)

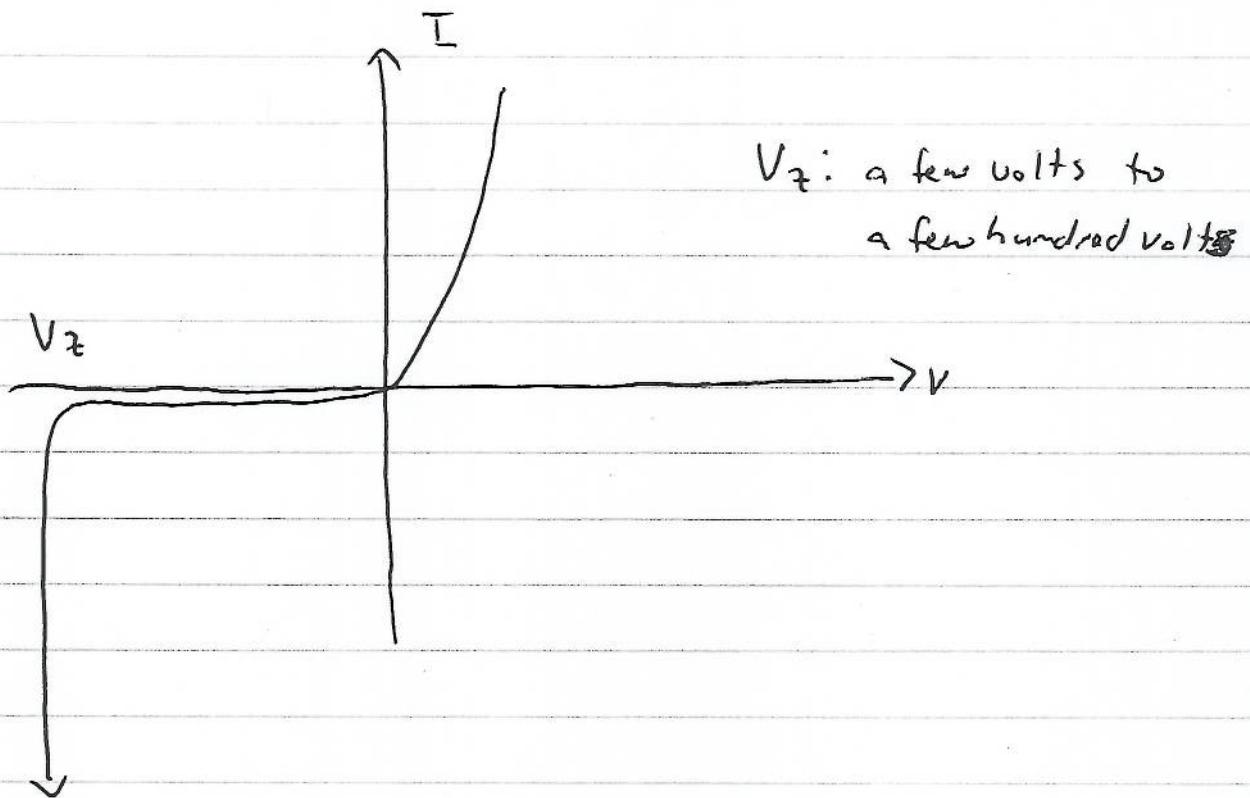\rightarrow These electrons ionize others \rightarrow avalanche




Zener diode Voltage Regulator

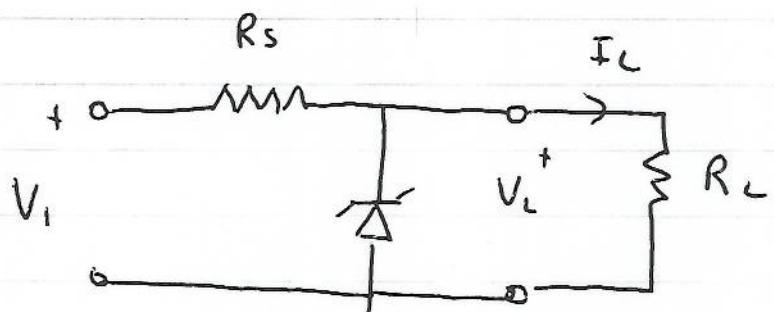



Zener keeps V_L from exceeding V_Z

Tunnel diode

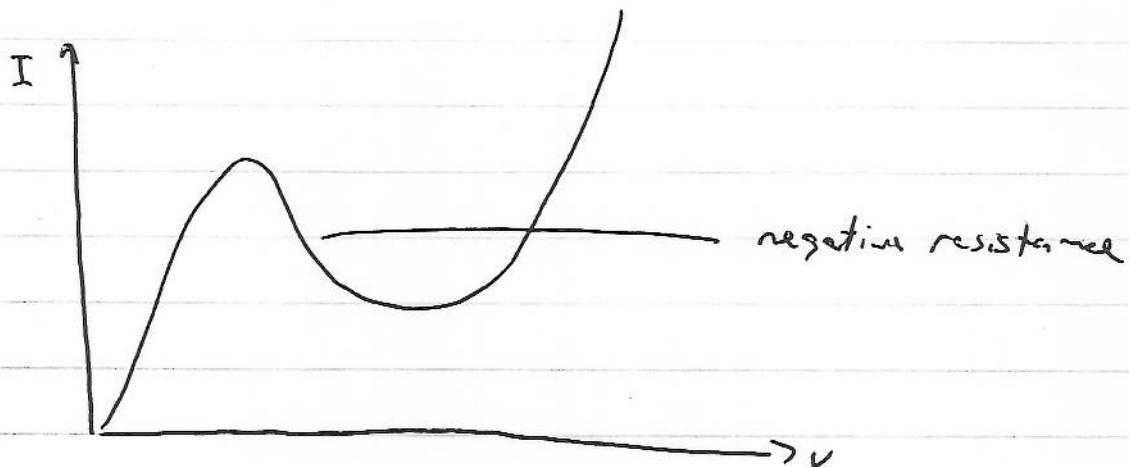

The Photovoltaic diode

reverse bias

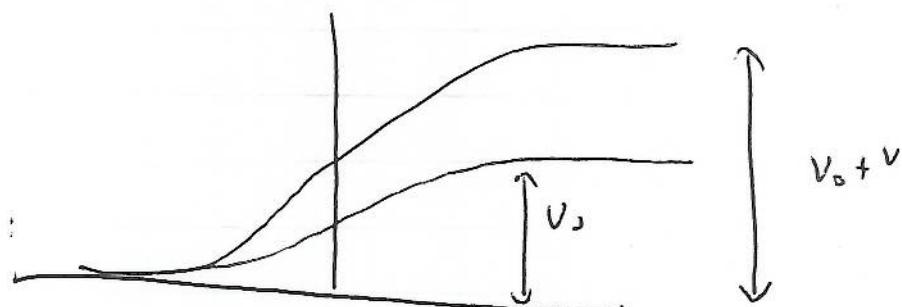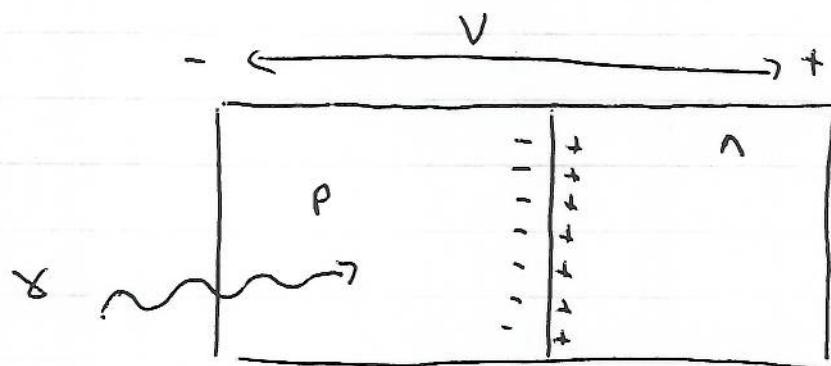


Photon creates e^- -hole pair
swept by field in depletion region

Fabrication Techniques

Method I

Ion implanted

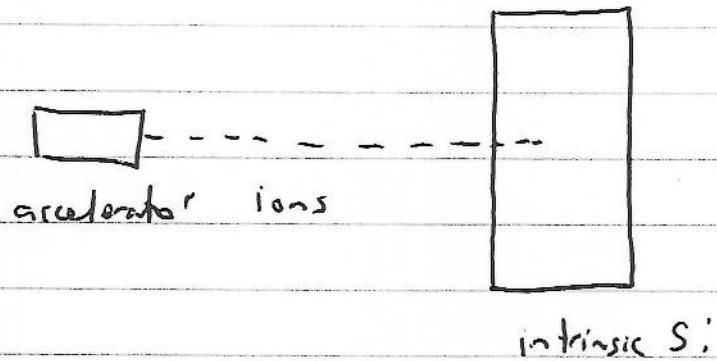


Beam energy gives depth of penetration

Must be annealed

Method II

Liquid diffusion technique

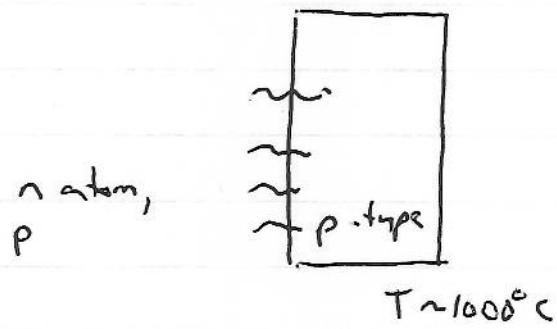


diffuse n-atom in

Junction depths controlled by

- concentrations
- diffusion time


Particle detectors

Recall diode junction

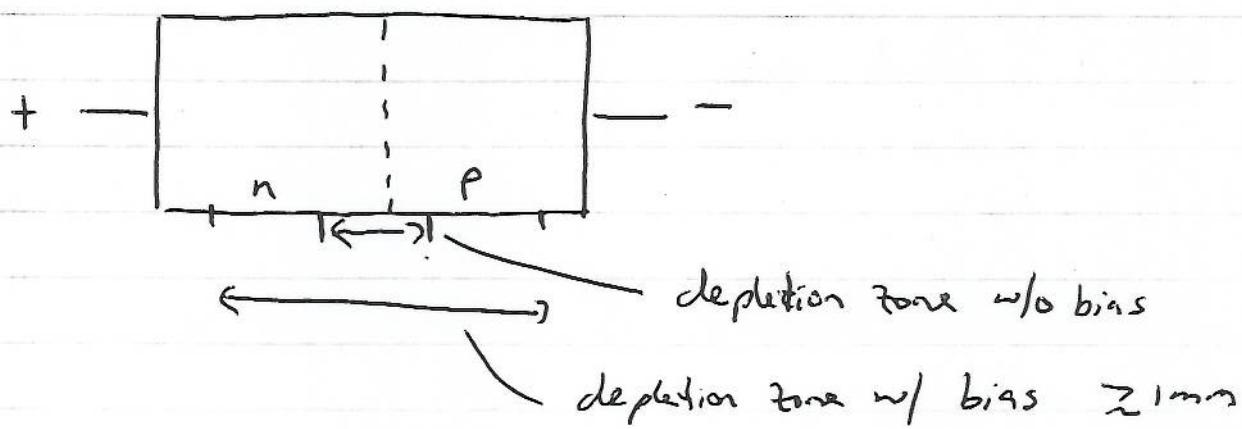

Reverse bias increases depletion layer

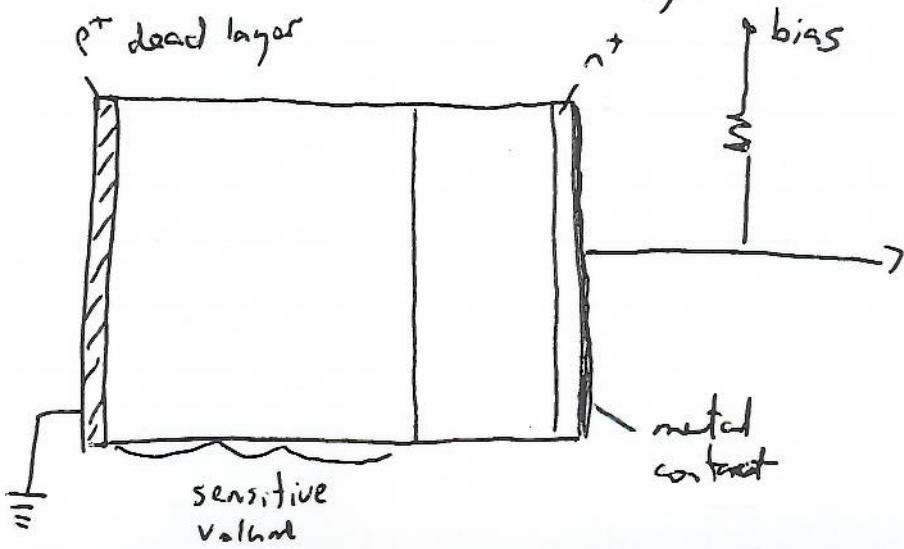Charged particle entering depletion layer ionizes
 \rightarrow signal size \propto to energy



GERMANIUM DETECTOR OPERATIONAL CHARACTERISTICS

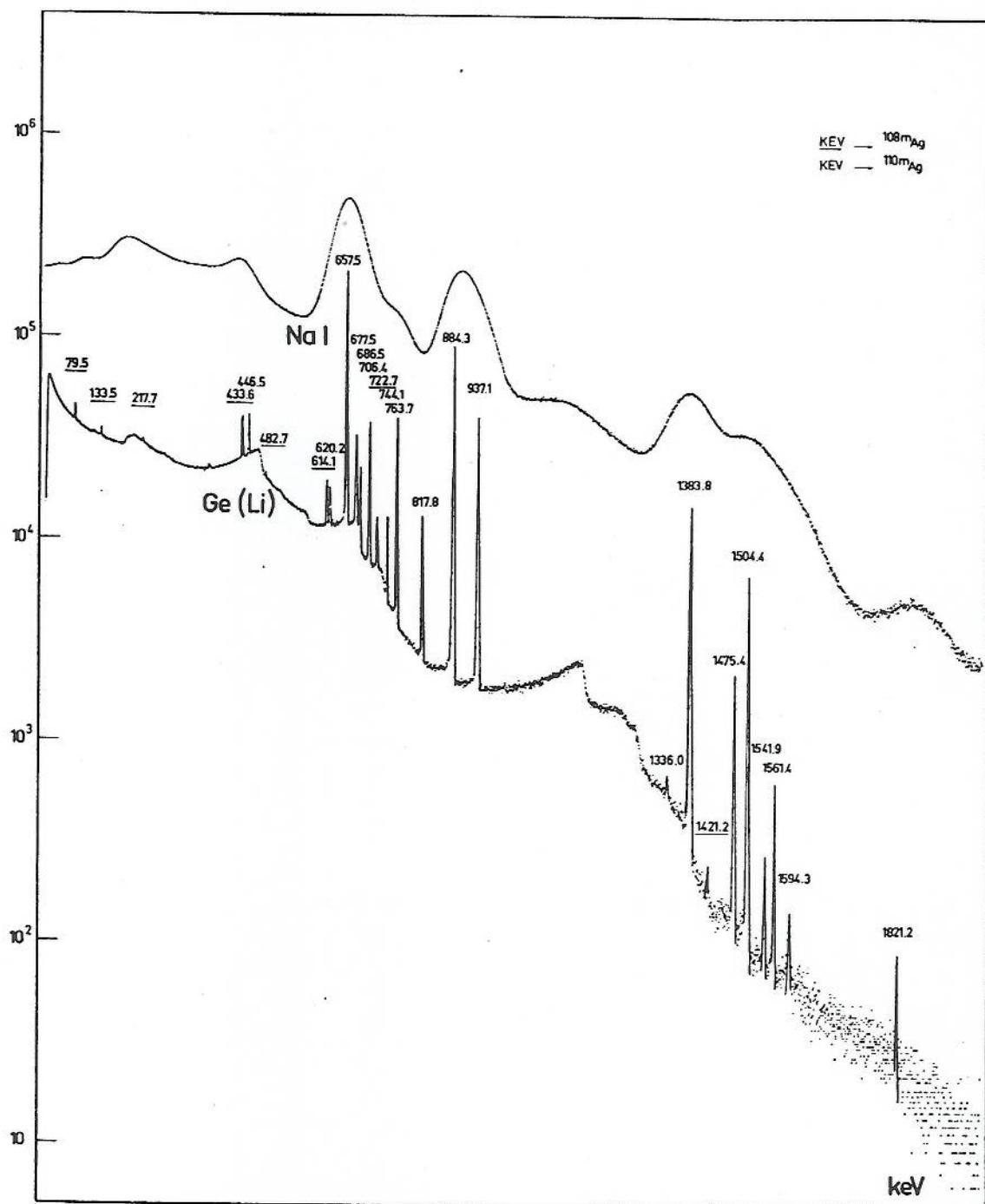


Figure 12-6 Comparative pulse height spectra recorded using a sodium iodide scintillator and a Ge(Li) detector. The source was gamma radiation from the decay of ^{108m}Ag and ^{110m}Ag . Energies of peaks are labeled in keV. (From Philippot.⁹)

Diode Applications


Rectifiers:

- (1) Most power is delivered as AC
- (2) Many devices need D.C.

Why (1)?

Reason 1:

Power production

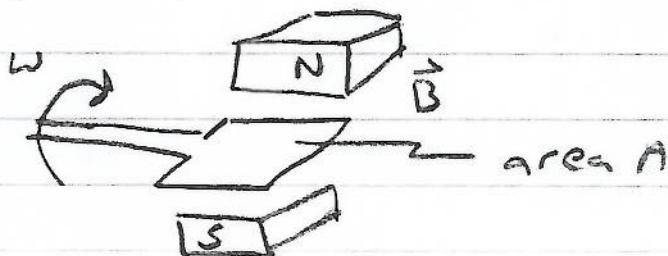


Rotate loop in B field

Faraday says


$$\mathcal{E} = - \frac{d\Phi}{dt}$$

$$\Phi = BA \cos \omega t$$
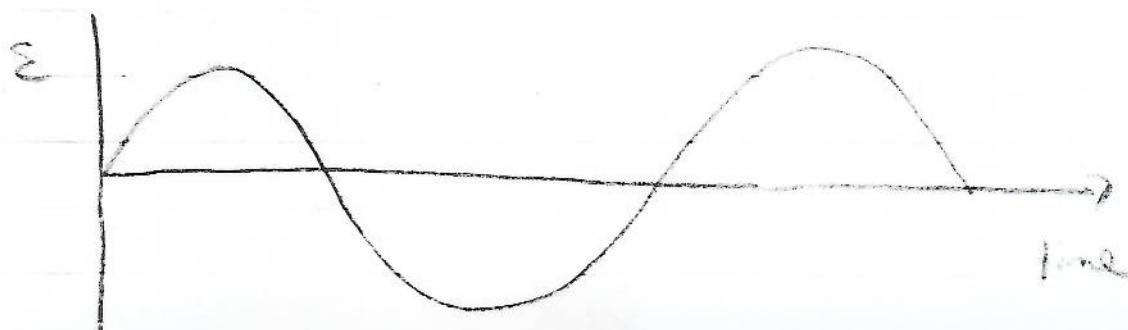
$$\mathcal{E} = B A \omega \sin \omega t$$



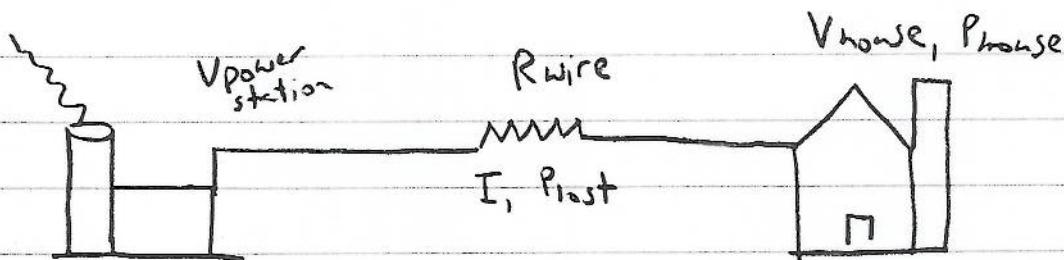Why not rectify (ie make it DC) at the power plant?



$$P_{lost} = I^2 R_{wire}$$

$$\begin{aligned} P_{house} &= I V_{house} \\ &= I V_{power} - I^2 R_{wire} \end{aligned}$$


For fixed R_{wire} , want high voltage, low current

Want to transmit at high voltage



Transformers

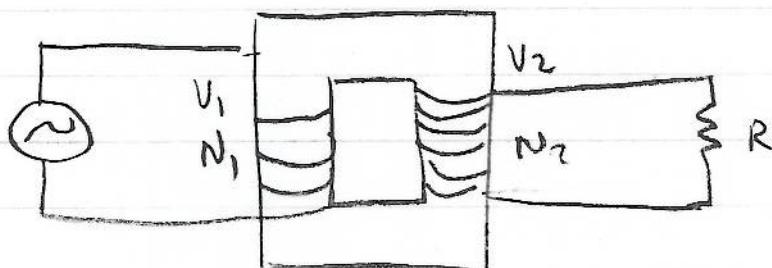Increase or decrease A.C. voltage as needed



Primary
(input)

Secondary
(output)



schematic

$$V_1 = -N_1 \frac{d\Phi}{dt}$$

$$V_2 = -N_2 \frac{d\Phi}{dt}$$



$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$N_2 > N_1$, step up

$N_2 < N_1$, step down transformer



Rectifiers

- half wave

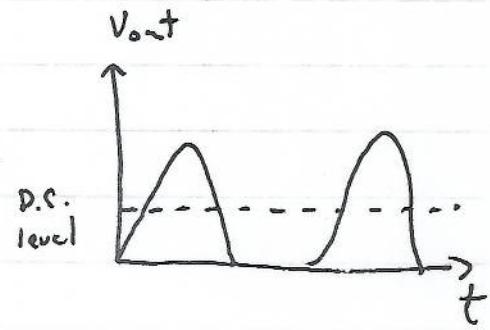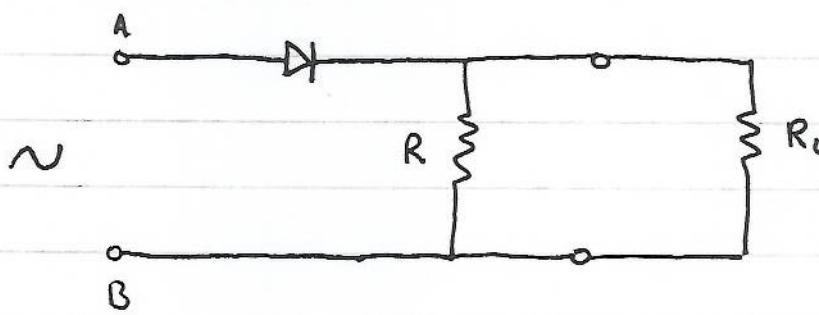


$$\text{Half wave: } V(t) = V_0 \left(\frac{1}{\pi} + \frac{1}{2} \cos \omega t + \frac{2}{3\pi} \cos 3\omega t + \dots \right)$$

w/ low pass filter

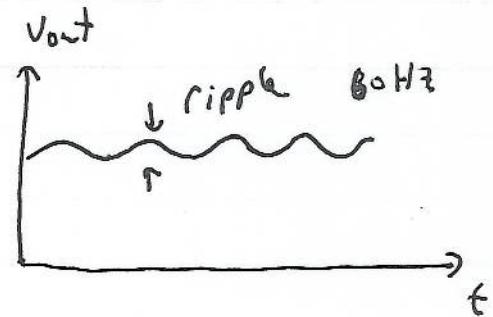
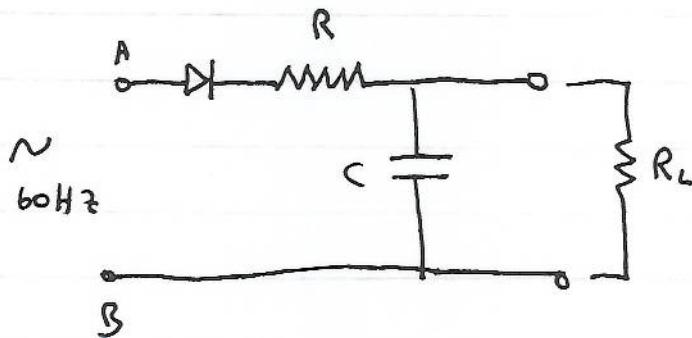


Not efficient

Full wave rectification

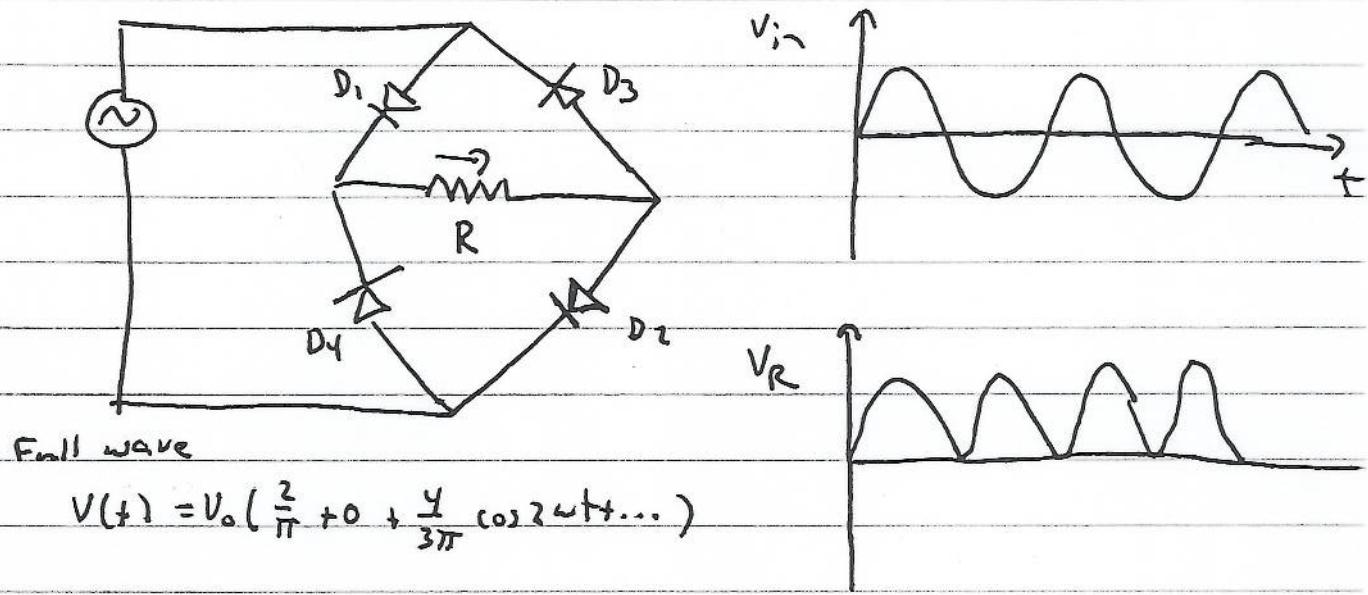



w/ low pass filter

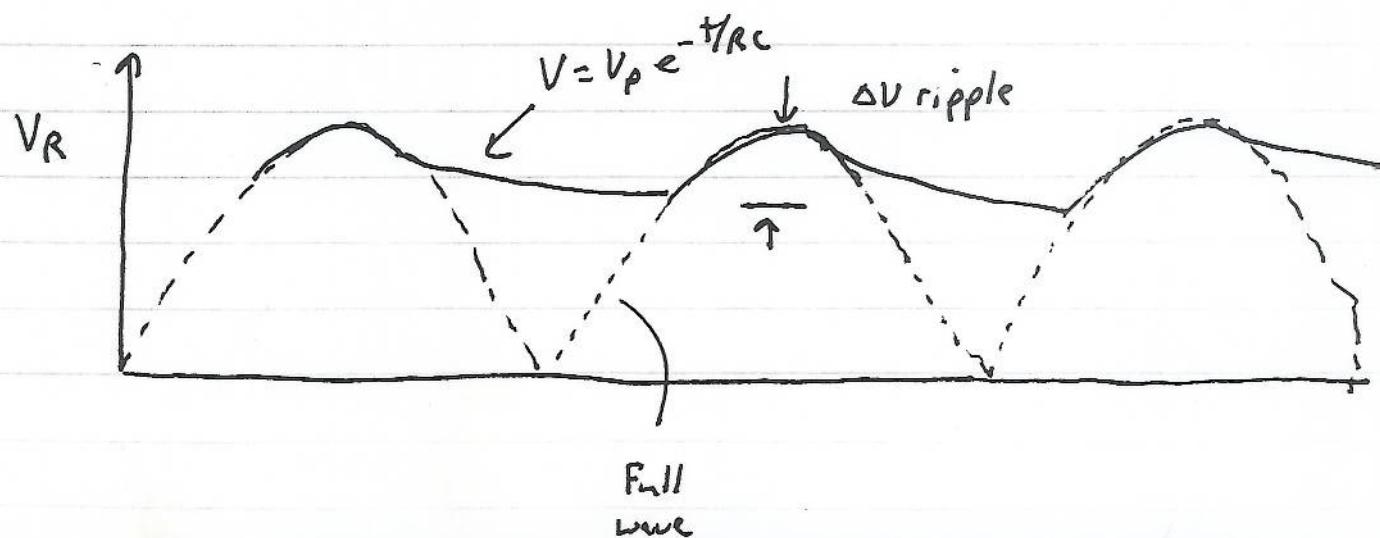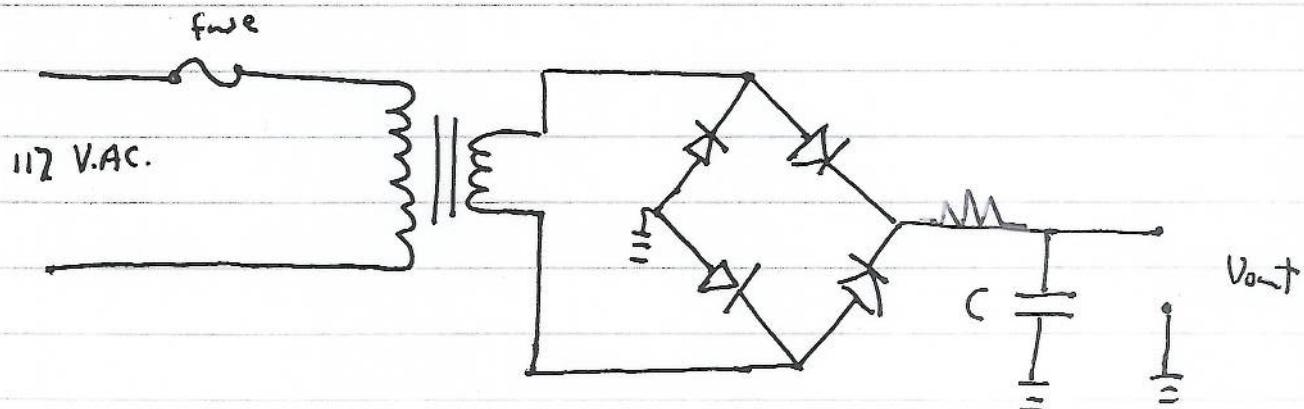

Let's say we want $\Delta V = 2V$ for 1Amp

$$C \approx \frac{I t_0}{\Delta V} = \frac{1 \times \frac{1}{120\text{sec}}}{2V} = 4166 \mu\text{F}$$

doJ Peak detector - r.f. signals

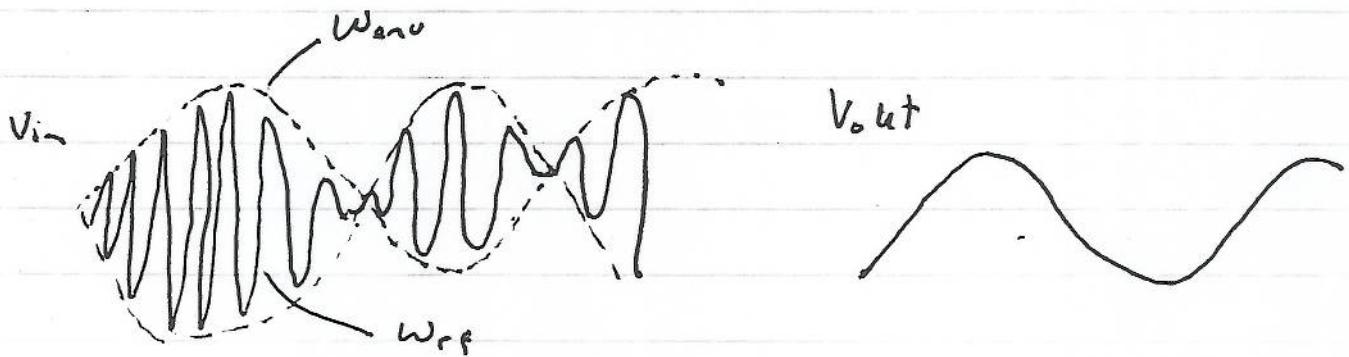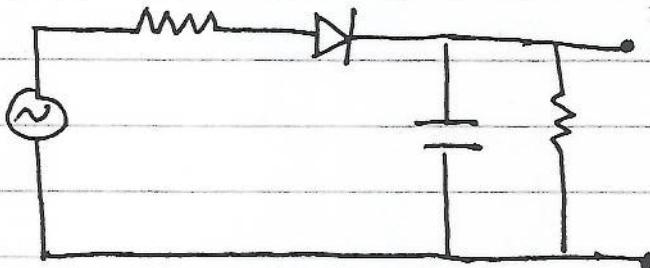

- Diode rectifies

Low pass filter choose $w_{rf} \gg \frac{1}{RC}$

but

$$w_{envelope} < \frac{1}{RC}$$


AM

$$V_{AM} = (1 + m \sin \omega_m t) V_c \sin \omega_c t$$

$$m = V_m / V_c$$

$$V_{AM} = V_c \sin \omega_c t + m V_c \sin \omega_m t \sin \omega_c t$$
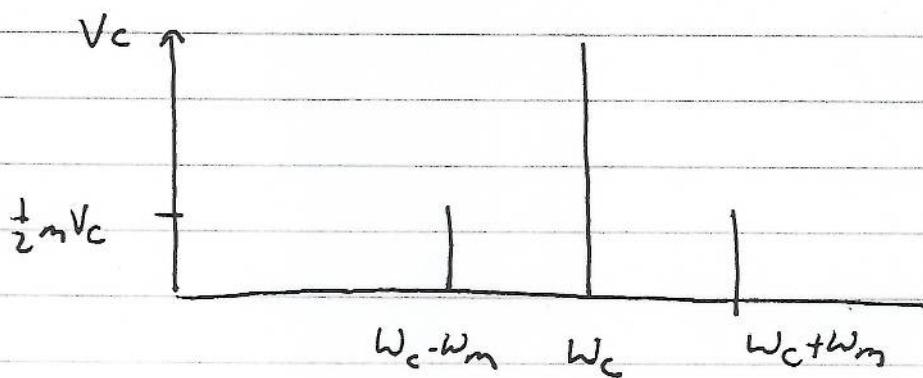
$$= V_c \sin \omega_c t + \frac{1}{2} m V_c \cos(\omega_c - \omega_m)t - \frac{1}{2} m V_c \cos(\omega_c + \omega_m)t$$



FM

frequency modulation

$$V_{FM} = \cos(\omega_c + k_f(t))t$$

PM

phase modulation

$$V_{PM} = \cos(\omega_c t + k_f(t))$$

angle modulation


FM 88 - 108 MHz $\Delta f = 75 \text{ kHz}$

AM 0.5 - 1.6 MHz

FM not used on AM band \rightarrow only 6 stations


FM detector




Recall

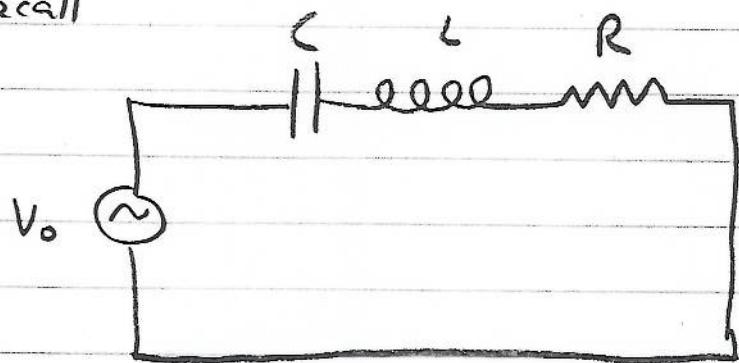


$$I_o = \frac{V_0}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

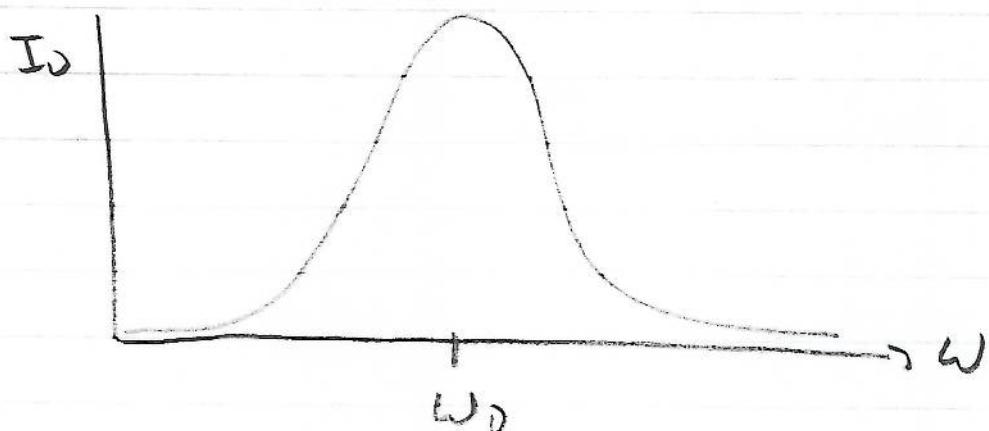

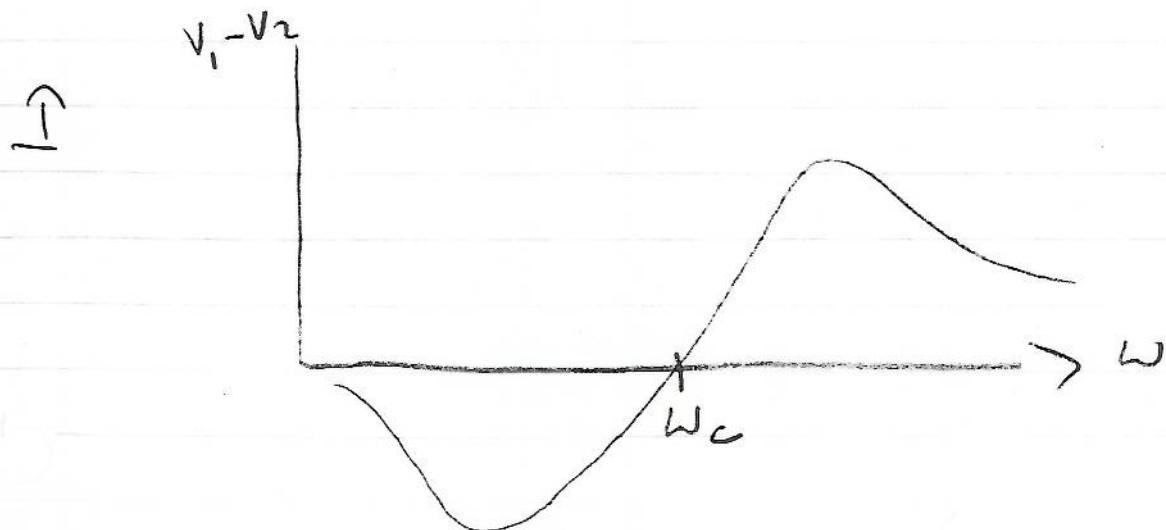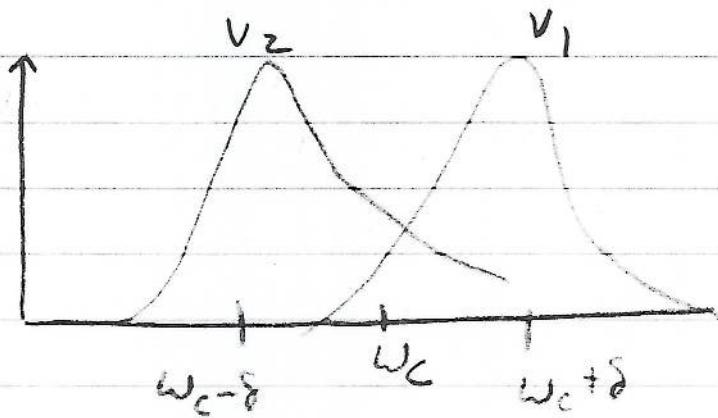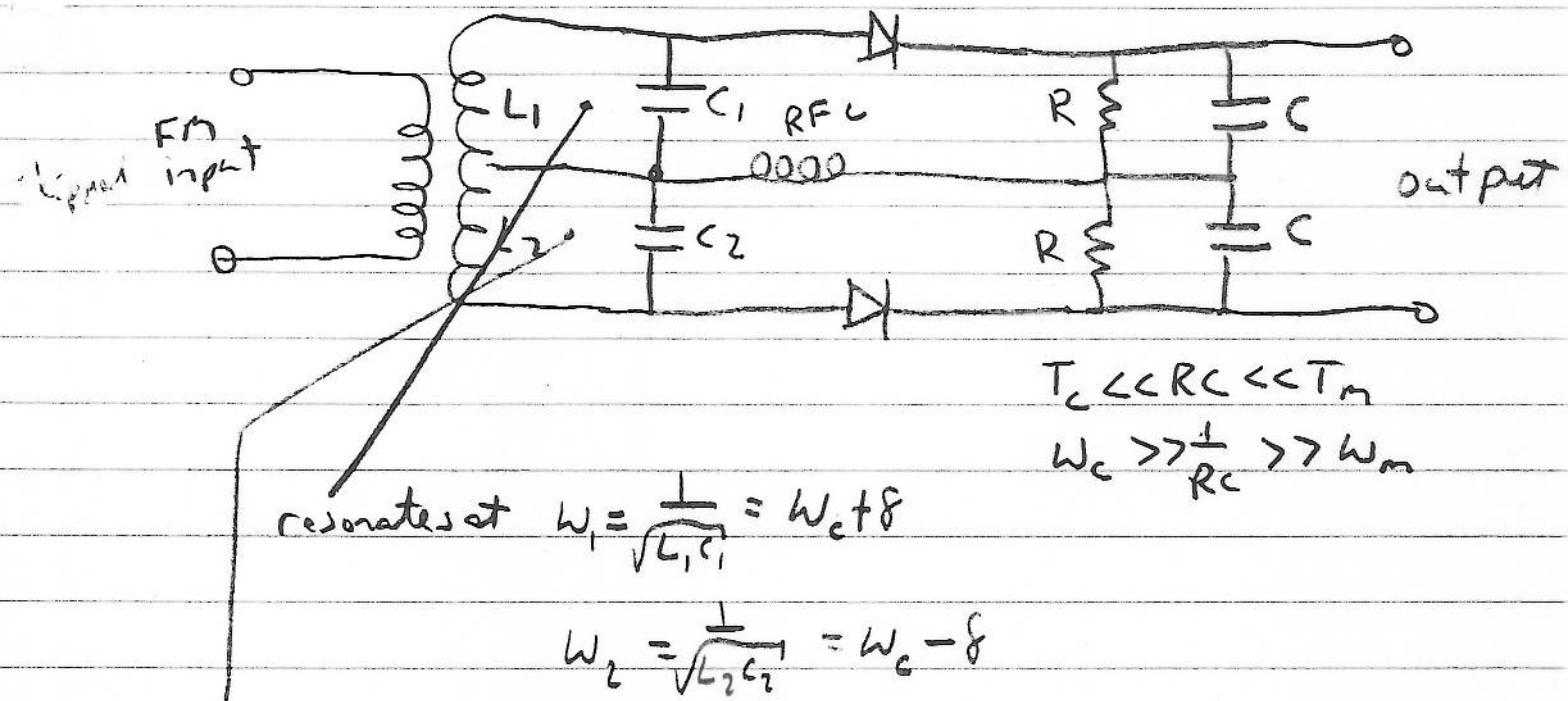

Voltage doubler



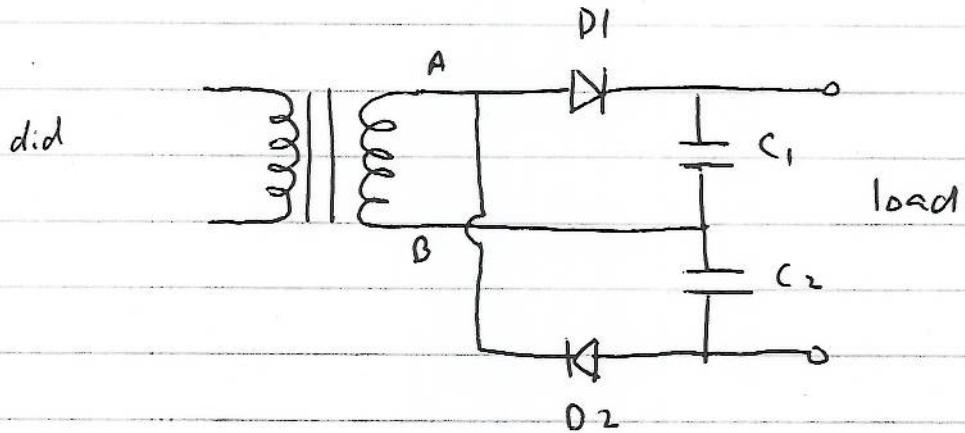


A^+ $\rightarrow C_1$ charges D1 conducts


A^- D2 conducts C₂ charges

Clipping circuit






diagram

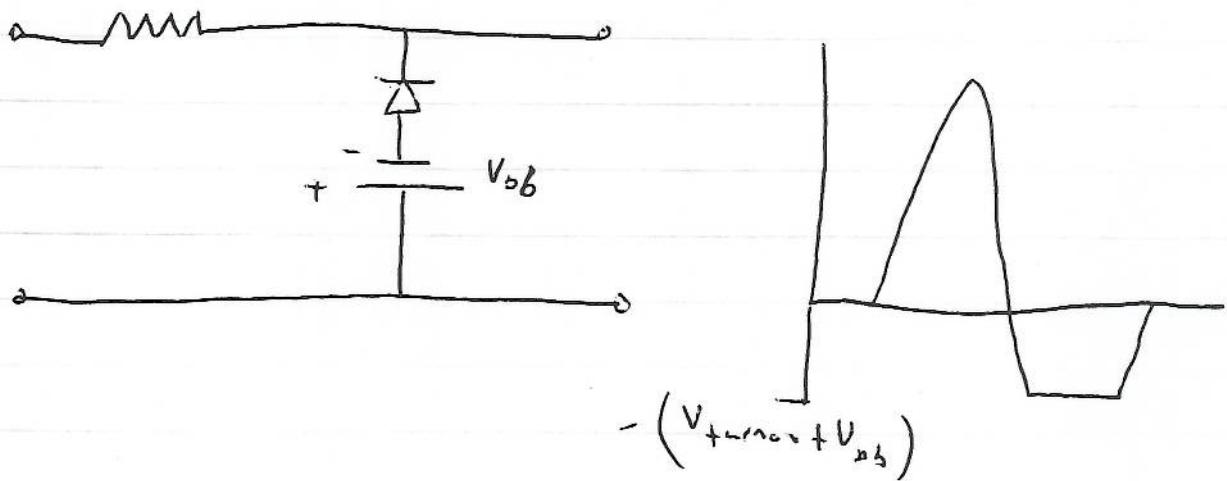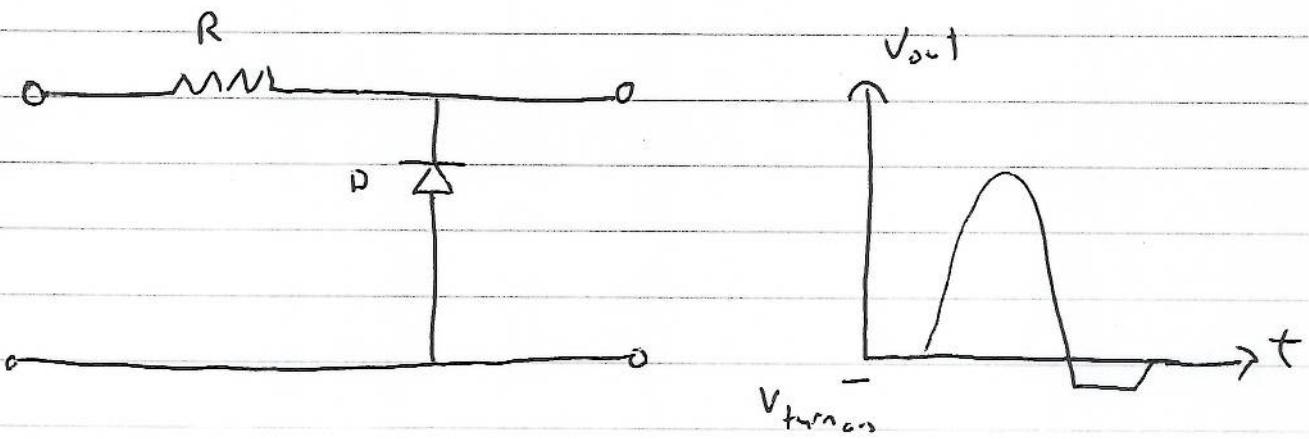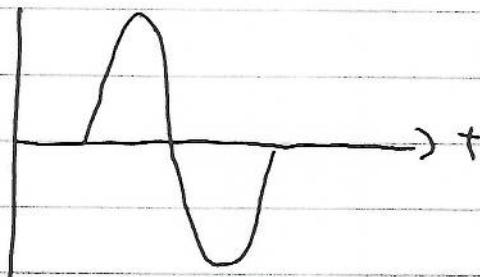

skip

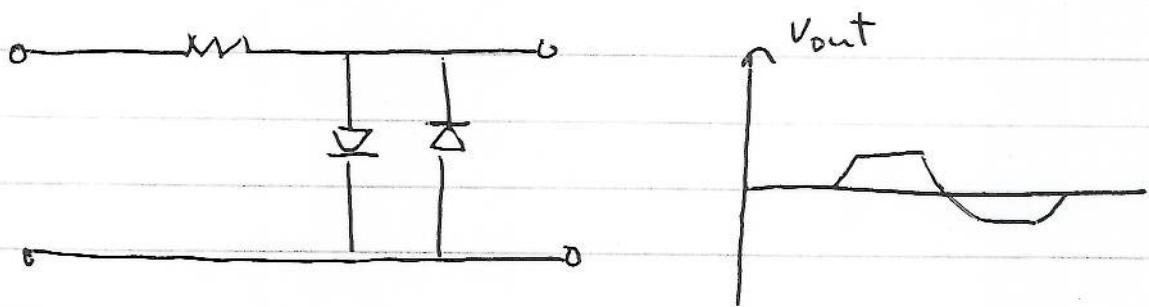

Baseline restoration

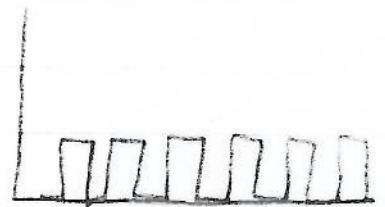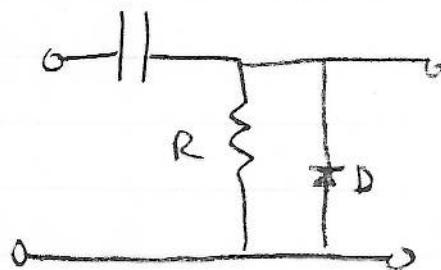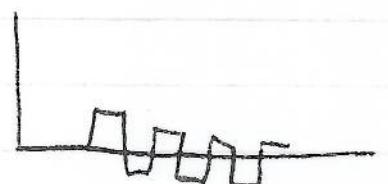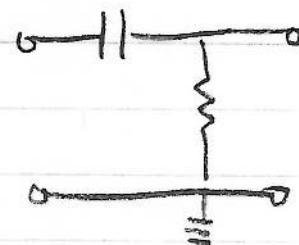
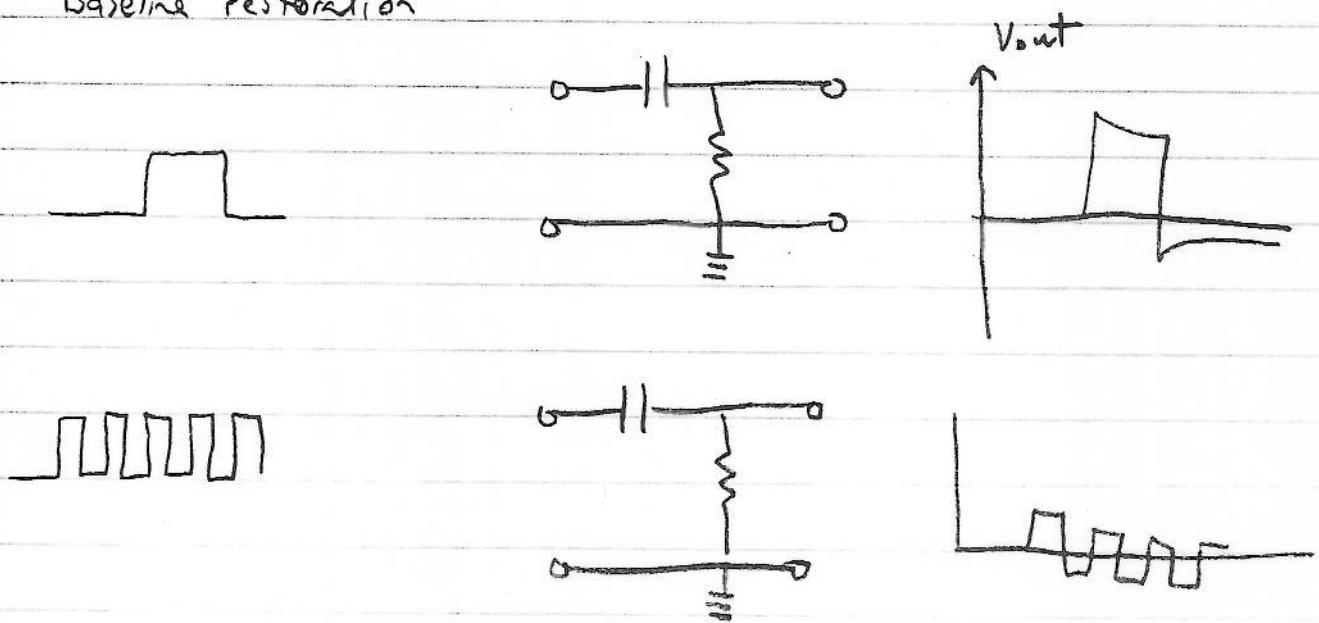


The Bipolar transistor


Punchline: Control a large current w/ a small one.

Recall n-p junction

unbiased

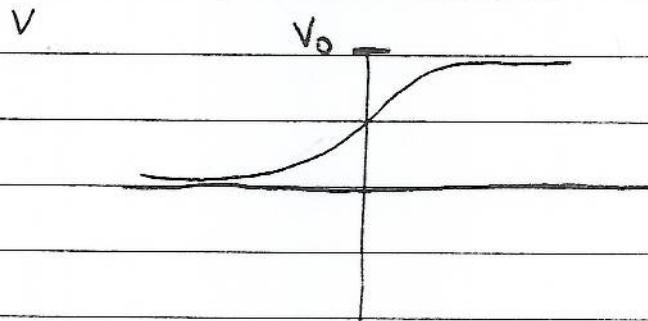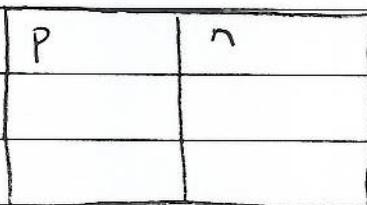

Forward biased

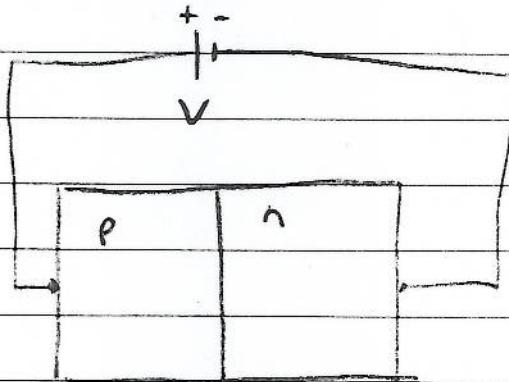


V_0 ← unbiased


$V_0 - V$ ← forward biased

If $|V| > |V_0| \rightarrow$ conduction


b) Reverse biased

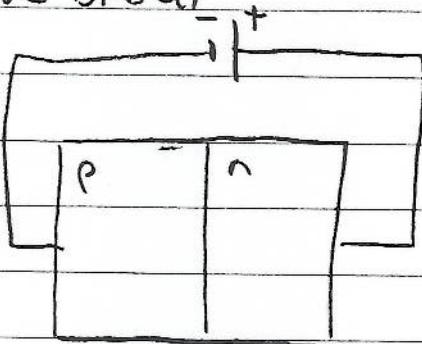


Reverse biased

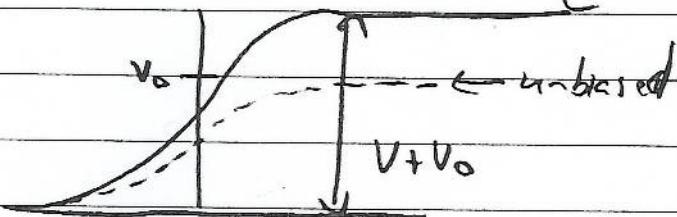


Now consider two junctions as follows

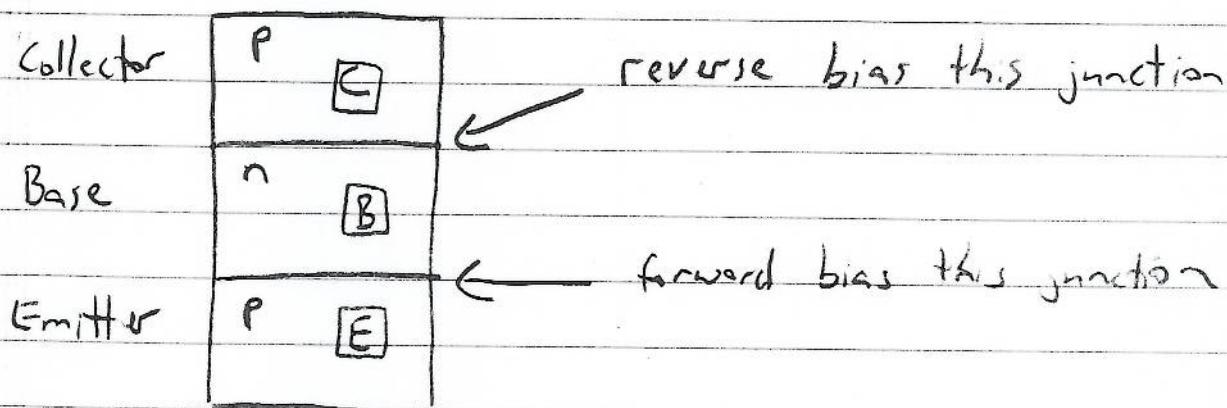

One way to realize this

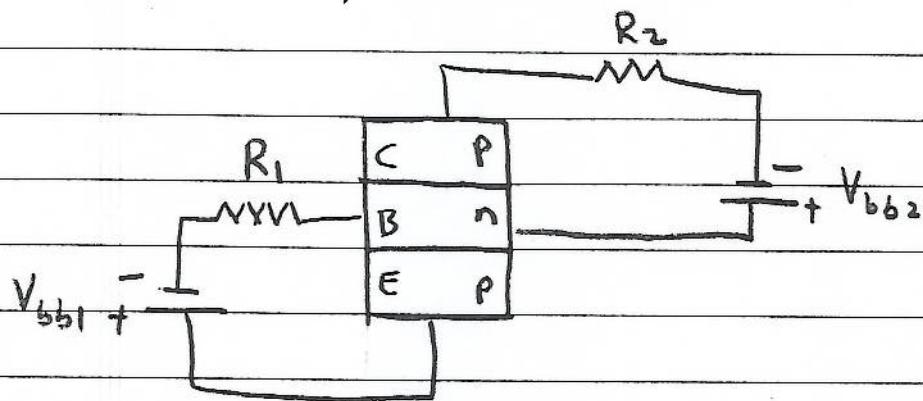


In practice

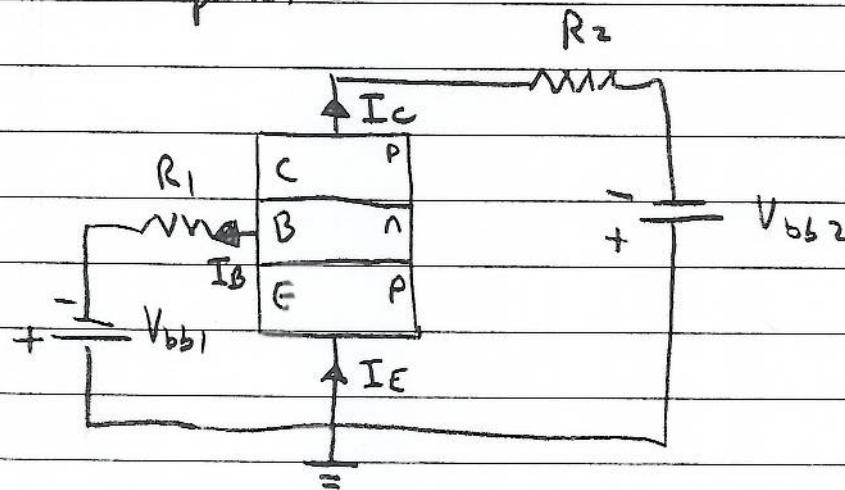

These two circuits are almost the same Why?


Recall diode

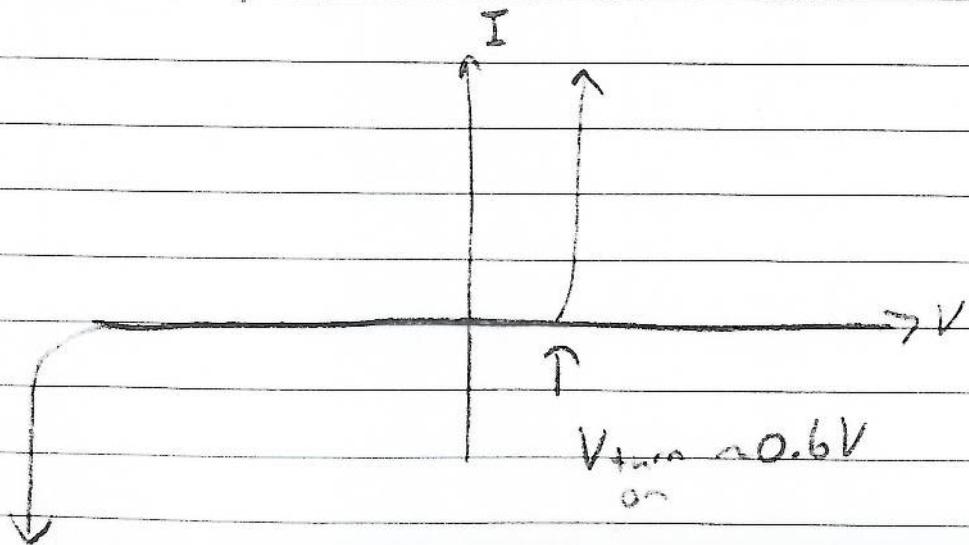

Since B-E junction is forward biased $V_{BE} \approx 0.6V$ (small)

Observations:

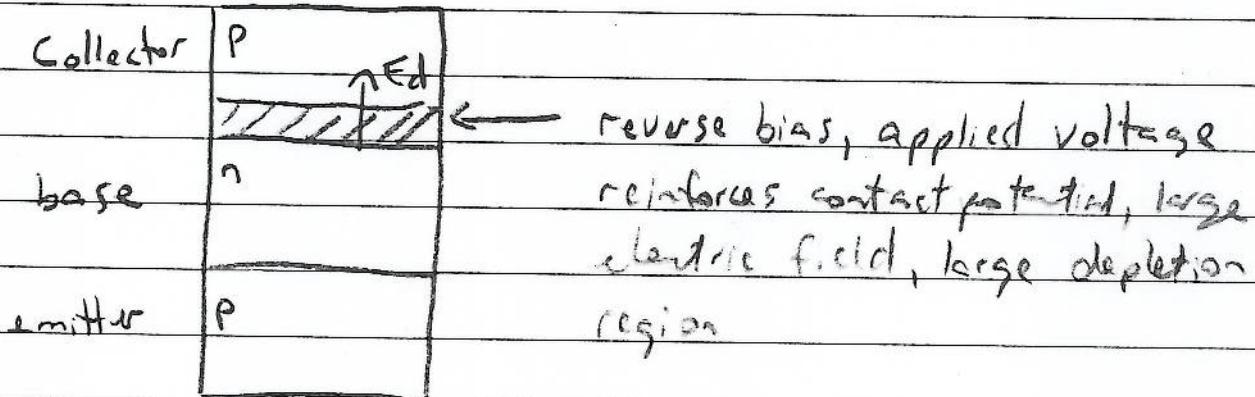- (1) Resistance between B & E is small (forward biased)
- (2) Resistance between B & C is large (reverse biased):



$$(3) I_E = I_B + I_C$$

Might expect I_B to be large compared to I_C but, we do a trick to make the reverse true

$$I_B \ll I_C$$

How do we do this?

Consider holes injected into emitter. Three things can happen

- 1) Combine w/ free electrons in base
- 2) Diffuse thru base, combine w/ electrons at wire } give lead attached to base } I_B
- 3) Diffuse across base to collector, be swept by E_d into collector

Fabrication trick:

Make base thickness small

$t_{\text{base}} \ll \text{mean free path of holes}$

* Holes usually are across C-B boundary before they have chance to recombine

Typically $I_B \sim 0.02 I_E$

Define $\alpha = I_C/I_E$ (≈ 0.99)

$$I_E = I_B + I_C$$

$$\frac{I_C}{\alpha} = I_B + I_C$$

$$I_C \left(\frac{1}{\alpha} - 1 \right) = I_B$$

$$\frac{I_C}{I_B} = \frac{\alpha}{1-\alpha}$$

$$I_B = I_E - I_C = I_E(1-\alpha)$$

$$I_C = \alpha I_E$$

Also define $\beta = \frac{\alpha}{1-\alpha}$

$$I_c = \beta I_B \quad \beta: 20 - 200$$

I_B is small

• Change $I_B \approx 1.1\text{mA}$, I_c changes $\approx 10\%$.

• If T_B considered input $\rightarrow I_c$ is amplified version of I_B

Amplification:

output > input

Voltage gain

$$A_v = \frac{V_{out}}{V_{in}}$$


Power gain

$$A_p = \frac{P_{out}}{P_{in}}$$

Current gain


$$A_i = \frac{I_{out}}{I_{in}}$$

E-B junction forward biased:

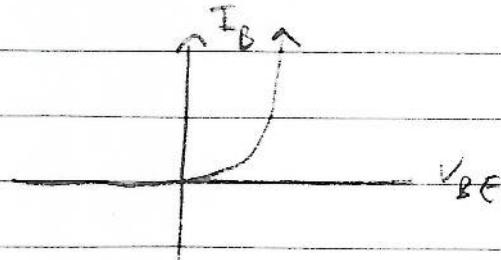

Small $\Delta V_{EB} \rightarrow$ large $I_B \rightarrow$ even larger I_c
 $(I_c = \beta I_B)$

Fabrication - PNP

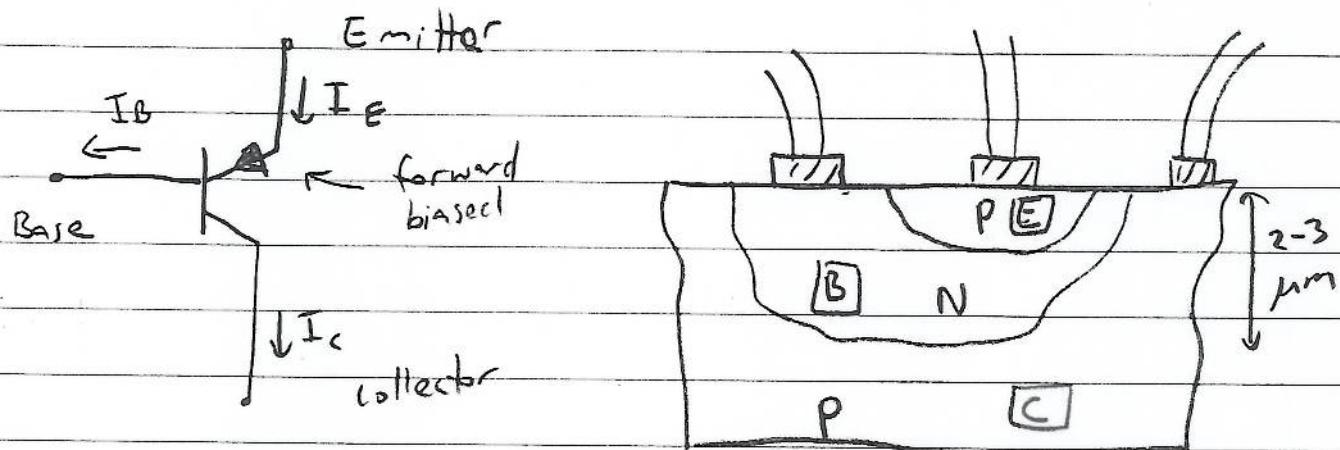

Collector is big



- I_C big
- Lot of heat to dissipate

Emitter doping is larger

- More holes going from emitter to base than electrons in base
- Minimizes recombination (1) & (2)
- Gives larger α & β

Can also have NPN

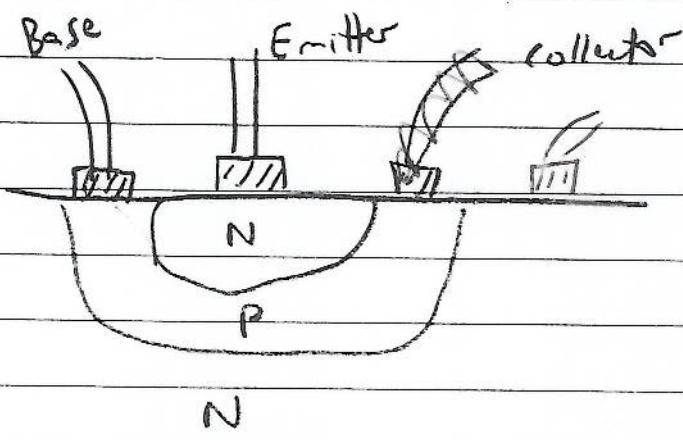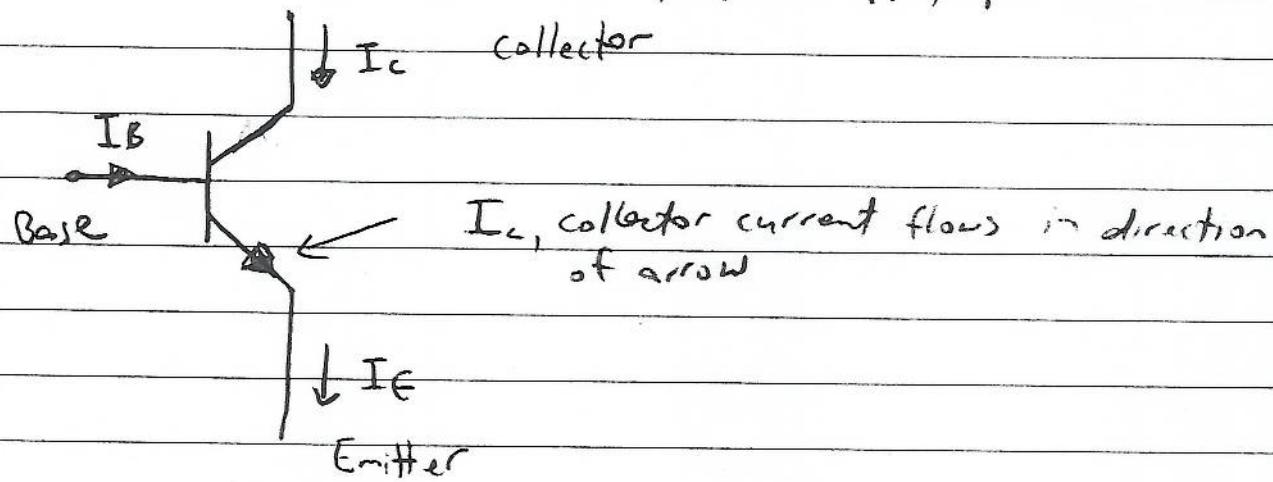Work like PNP's w/ power supply polarities reversed



Transistor is:

- 3 terminal device

- We are interested in I-V curve between two of the terminals


- 3rd terminal controls device

→ different I-V curve for each condition of 3rd terminal

- active device - power gen (with power supplied)

Ex of passive device:

Transformer

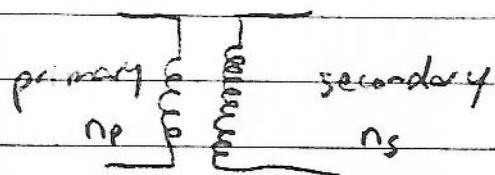



$$\text{Voltage gain} \quad \frac{V_s}{V_p} = \frac{n_s}{n_p}$$

But no power gain

$$\frac{I_s}{I_p} = \frac{n_p}{n_s} \quad P_p = P_s \quad , \text{passive device}$$


BJT

NPN

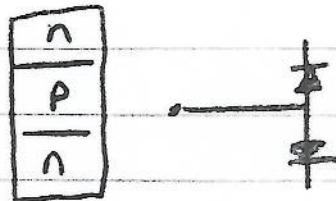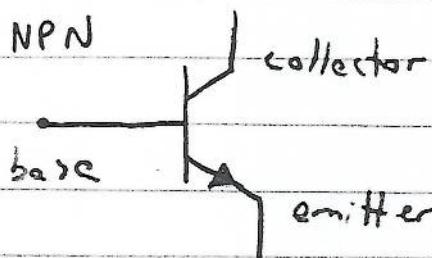

"never points in"


PNP

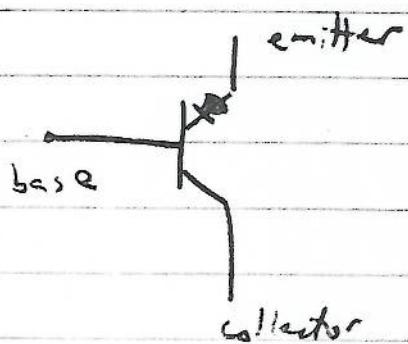

NPN

BE diode forward biased

BC diode reversed biased

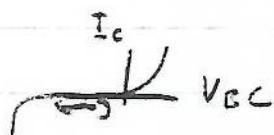

EC current flows in direction of arrow

Biasing and Graphical Treatment of BJT

transistor - 3 terminals


input \nparallel output

- 1) common emitter
- 2) common collector
- 3) common base


Common Emitter characteristics npn




$$V_{BE} \sim 0.6 \text{ V}$$

I_B varies a lot, look at it

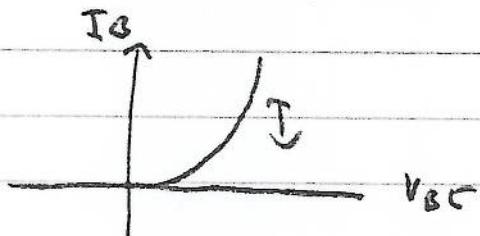

Also, focus on V_{BC}

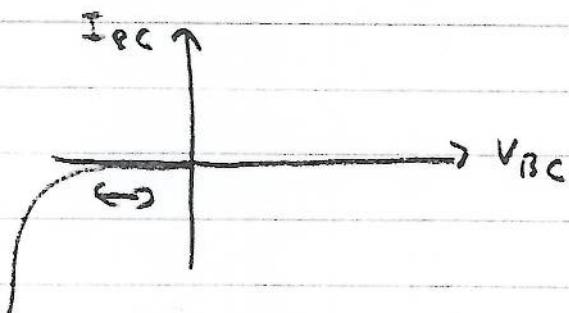

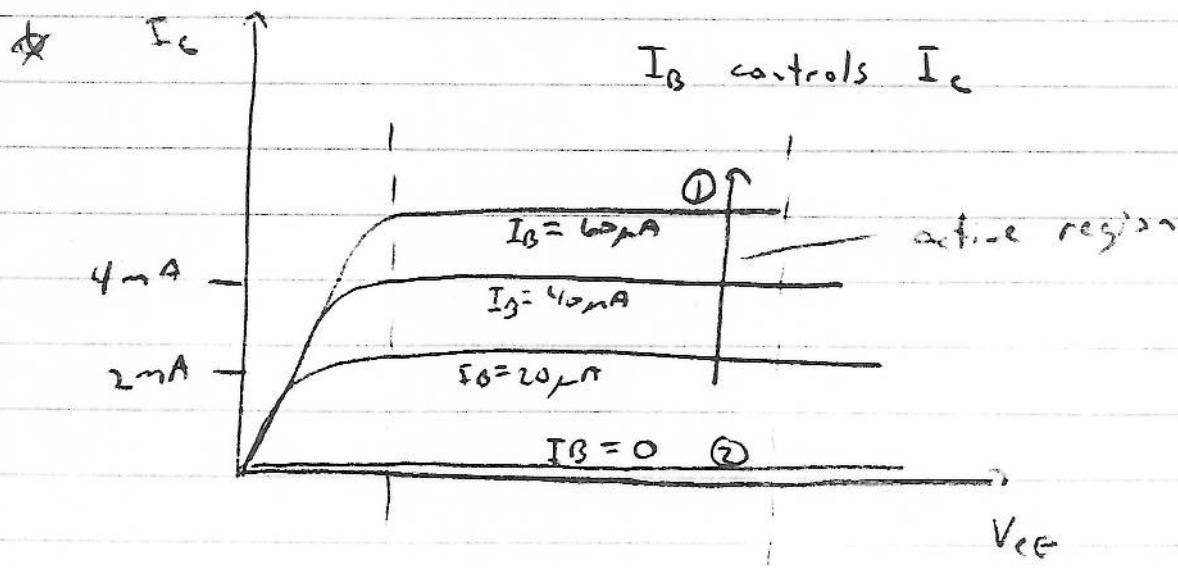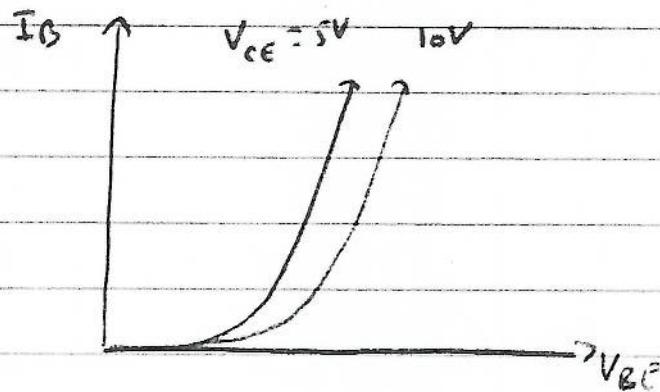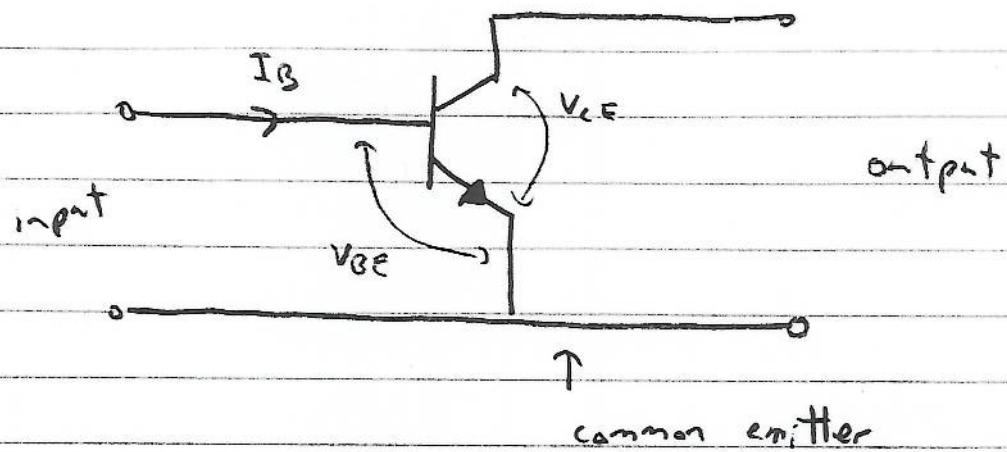

I_C independent of V_{CE} , but increases as I_B increases

3 regions of operation

* (1) active region

$$I_C = \beta I_B$$

(2) cut off region

$$I_C \rightarrow 0 \quad E_C \text{ open circuit}$$

(3) saturation region

$$V_{BC} \rightarrow 0 \quad E_C \text{ short circuit}$$

V_{CE} cannot supply enough current


* Current amplification

(1) base emitter forward biased

(2) base collector reverse biased

(3) stable (temperature, small perturbations, \rightarrow input, perturbation in transistor parameters)


Consider

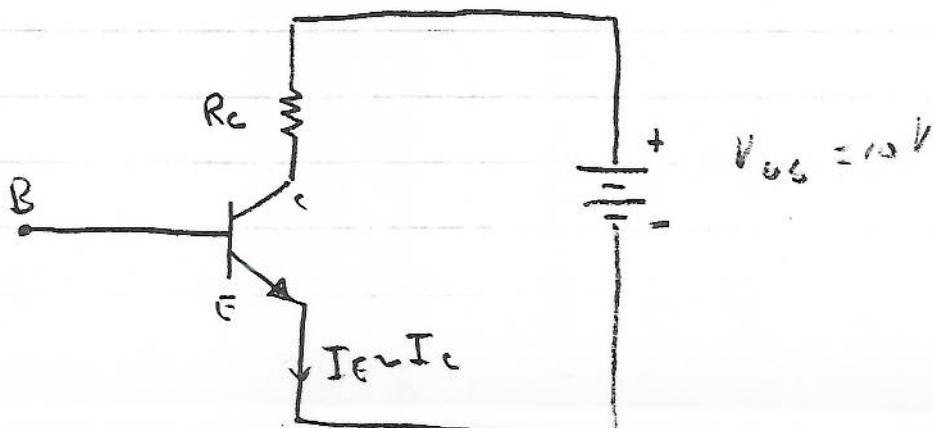

Kirchhoff

$$V_{bb} - V_{CE} - I_c R_c = 0$$
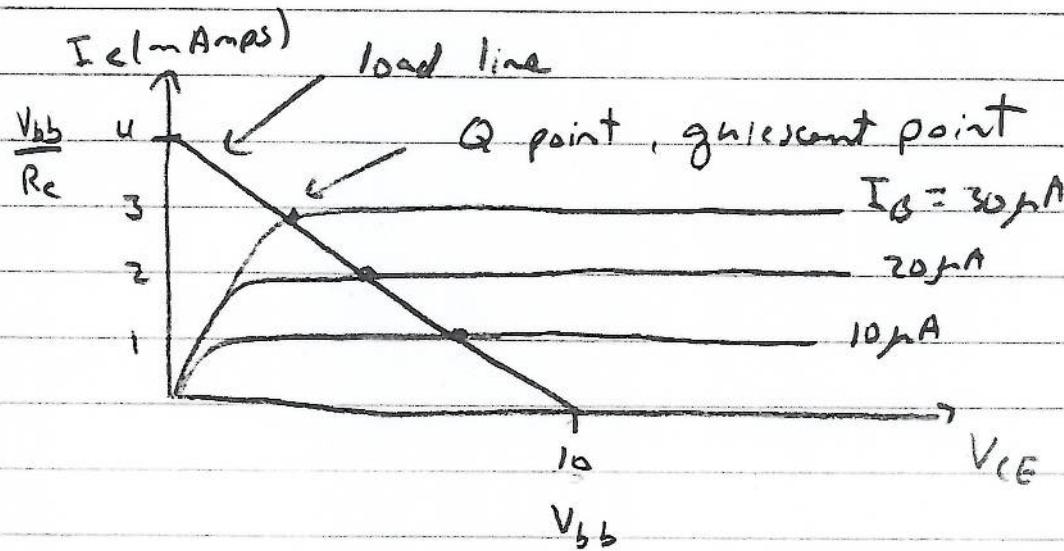
$$I_c = \frac{V_{bb}}{R_c} - \frac{V_{CE}}{R_c} \quad \text{must be satisfied}$$



$$I_c = \frac{V_{bb}}{R_c} \quad \text{transistor fully turned on}$$

$R_{\text{transistor}} = 0$ all voltage across the resistor

$V_{CE} = V_{bb}$ $R_{\text{transistor}} = \infty$ turned off

$I_c = 0$ no voltage across resistor

Can read current gain off graph

$$\text{current gain} = \frac{I_c}{I_B}$$

Large current gain - steep load line
 R_L : small


Large V_{ce} gain - flat load line
 R_L : large

Stability of operating point

Remember I_B controls I_C

How do we fix I_B ?

Soln 1 (not so good)

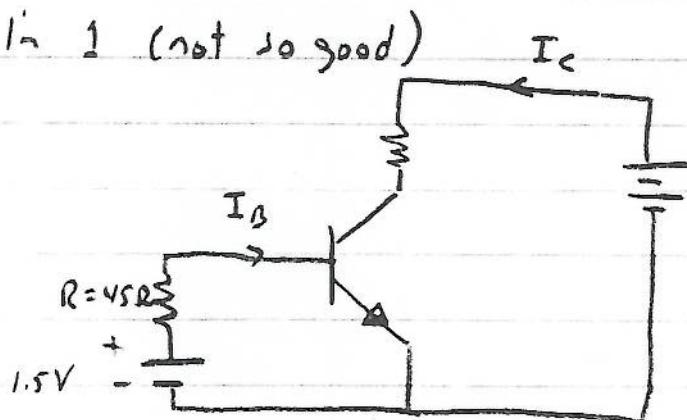

Why this $R \neq V$?

Kirchhoff

$$1.5V - 0.6V - I_B R = 0$$


$$\text{If } R = 45k\Omega \quad I_B = 20\mu\text{Amp}$$

This sets I_C

Bads things about this setup

- (1) two batteries
- (2) temperature instability
- (3) sensitive to β

Better solution

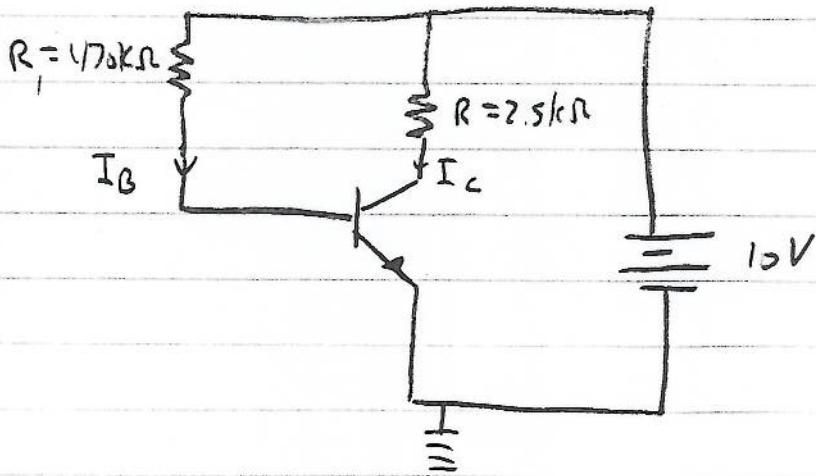

To forward bias BE $V_{BE} \sim 0.6V$


$$\beta = 100$$

$$\text{If } I_C = 2mA, \quad I_B = I_C/\beta = 20\mu A$$

$$R_1 = \frac{V_{bb} - V_B}{I_B} = \frac{10V - 0.6V}{20\mu A} = 470k\Omega$$

β dependence still there
T dependence.



To lessen T dep.

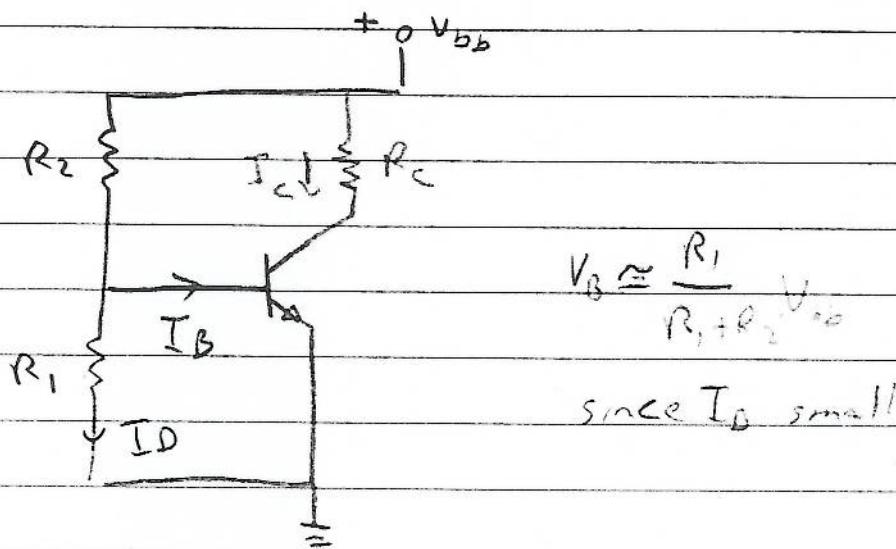



Ratio of R's matter \rightarrow vary w/ T in the same way

\rightarrow Temp still affects transistor

Amplifying AC signal

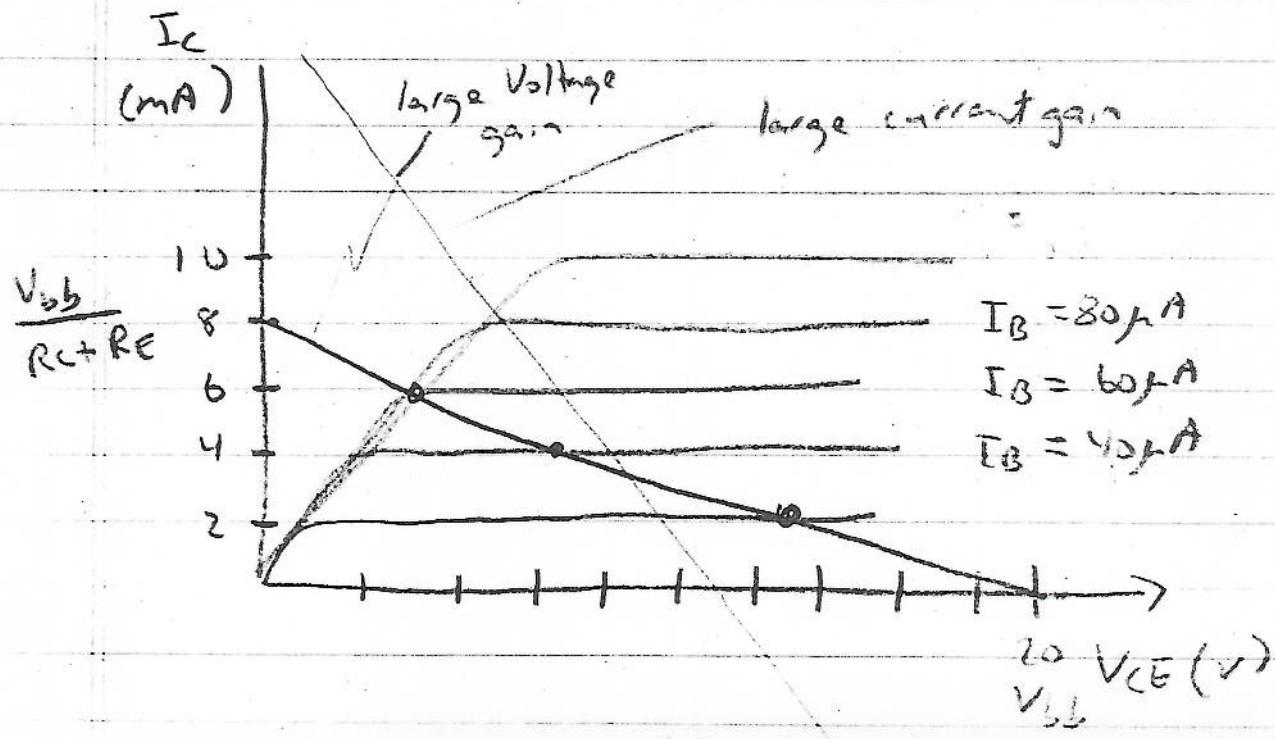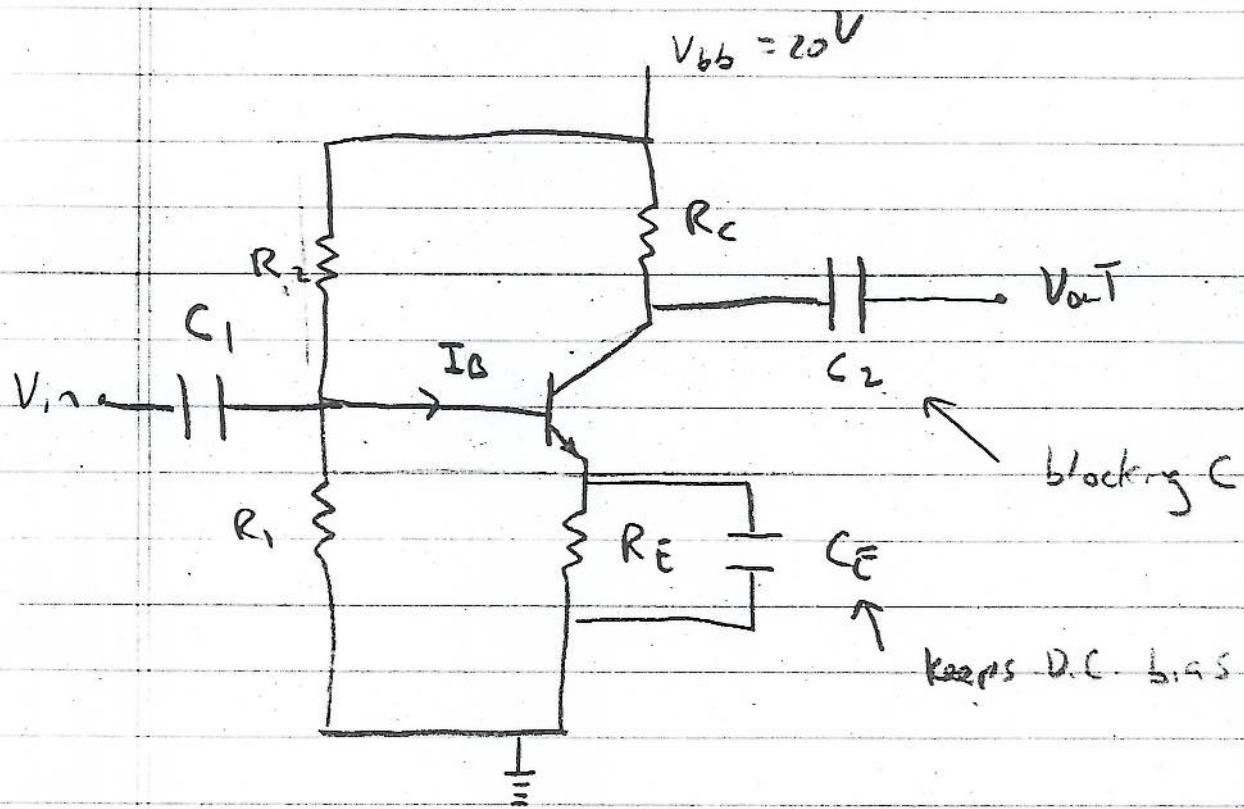

Transistor switches

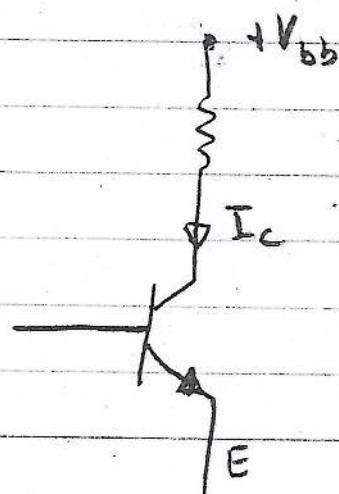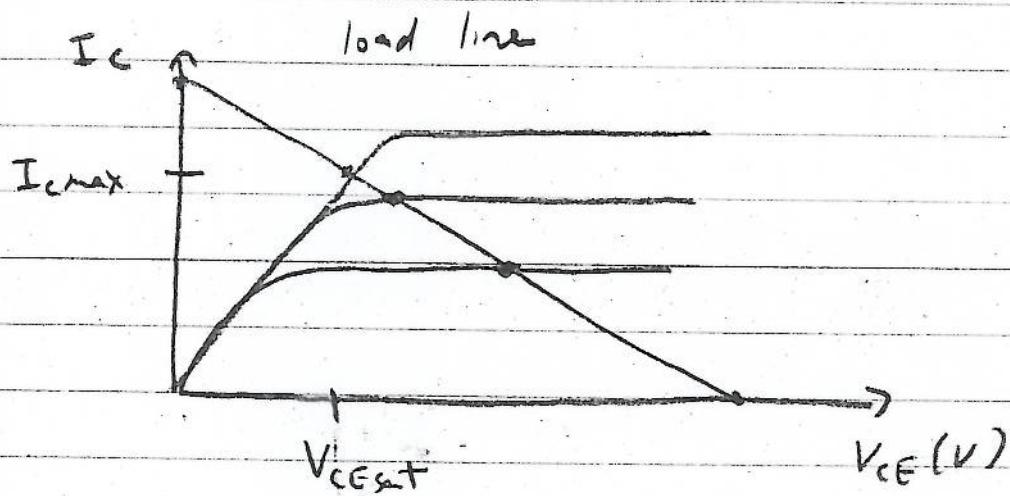

$$V_b = 0 \quad I_c = 0 \quad \underline{\text{off}}$$

Load line says V_{ce} not below V_{cesat}
 I_c not above I_{cmax}

Saturation

B-C junction forward biased

I_B increase does not increase I_C

$$I_C \neq \beta I_B$$

$$V_C \sim 0.2V \quad V_B \sim 0.6V$$


B-C junction reverse biased (amplifiers)

$$I_C = \beta I_B$$


& Switch example:

Solenoid valve $R_s = 50\Omega$ $I = 200mA$ to open

Computer supplies 3.5V 5mA open signal

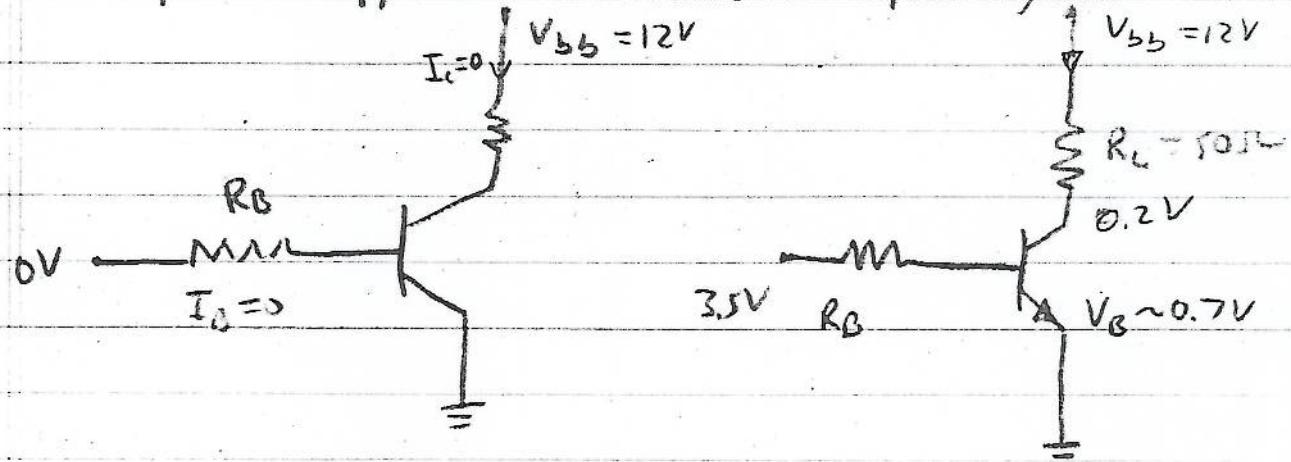

B

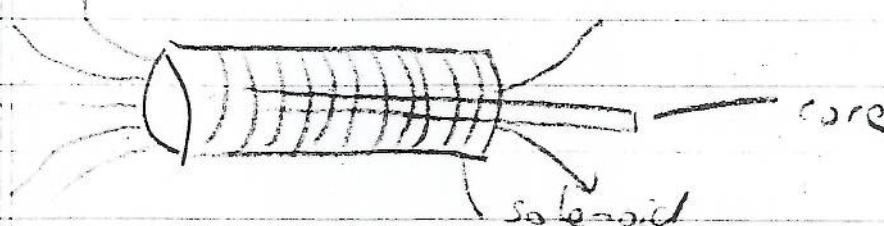

0-

(*)

$$\beta = 50$$

$$V_L = 50\Omega (20A) = 10V$$

$$\rightarrow V_{bb} = 12V$$

OFF

$$I_B = 0 \quad I_C \approx 0$$

ON

$$V_B = 3.5V$$

$$I_B = \frac{3.5V - V_B}{R_B} = \frac{3.5V - 0.7V}{R_B}$$

$$R_B \downarrow \quad I_B \uparrow \quad I_C = \beta I_B \text{ even larger if not saturated}$$

* For npn when $I_C = I_{C\max}$ $V_C = 0.7V$

$$I_{C\max} = \frac{V_{bb} - V_C}{R_L} = \frac{12V - 0.7V}{50\Omega} = 236mA$$

$$I_B = \frac{I_{C\max}}{\beta} = \frac{236}{50} = 4.72mA$$

(computer can supply
5mA \rightarrow ok)

$$R_B = \frac{3.5V - 0.7V}{4.72mA} = 590\Omega$$

$R_B = 590\Omega$ allows input to drive transistor to edge of saturation




The point

Changing V_B

→ gives I_B

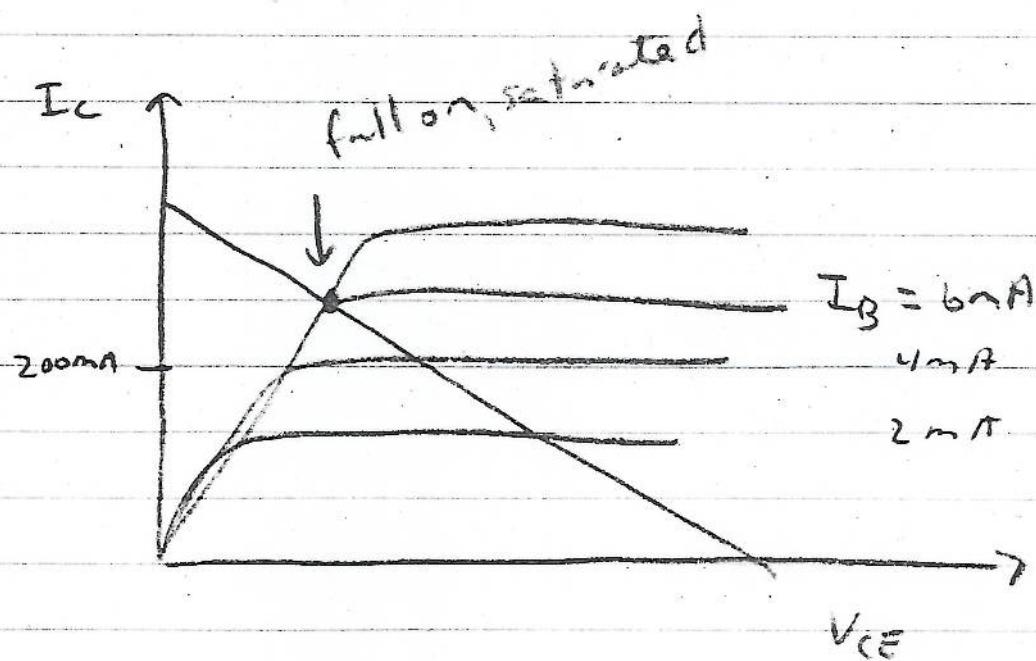→ choose R_B so I_B is big enough to make $I_C = 200mA$



If $I_B < 4mA$, $I_C < 200mA$, solenoid will open