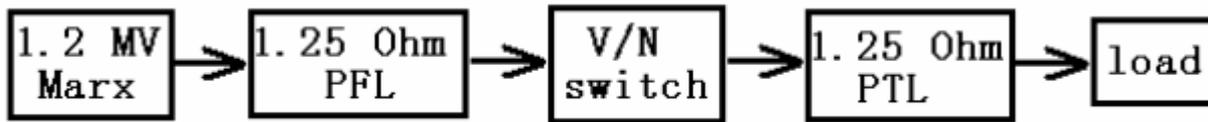


# ISIS Induction-Cell Driver Modification to High Current X-Pinch Radiation Source

Roman Shapovalov  
IAC  
Jan 28, 2013

# Overview: Pulsed Power Generator (PPG-1), Beijing



(b) A photograph of PPG-I

max current: 400 kA  
pulse width: 100 ns

## X-Pinch

two 25  $\mu\text{m}$  (or 13  $\mu\text{m}$ ) Mo wires  
anode/cathode distance: 10 mm


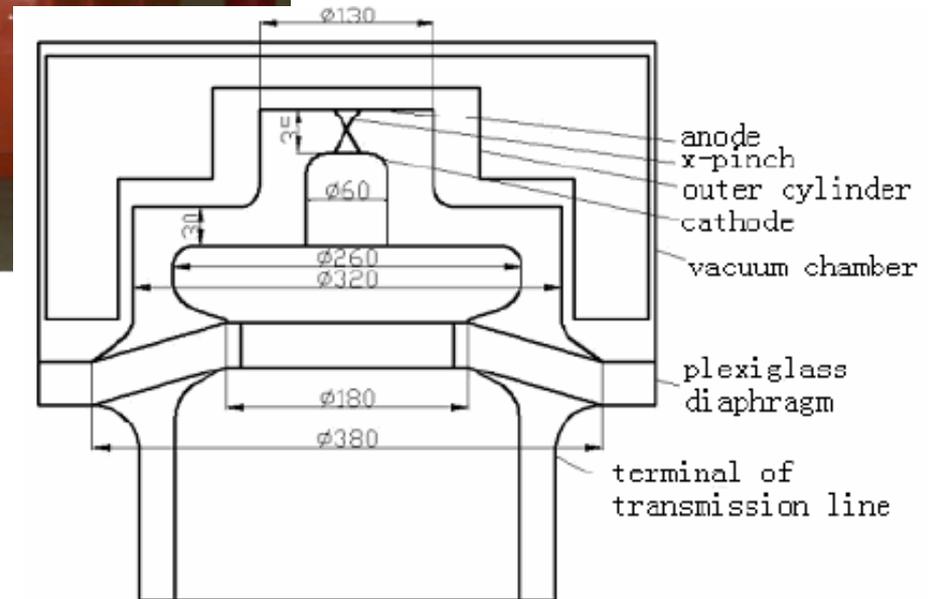


Figure 3. The sketch of the load section.
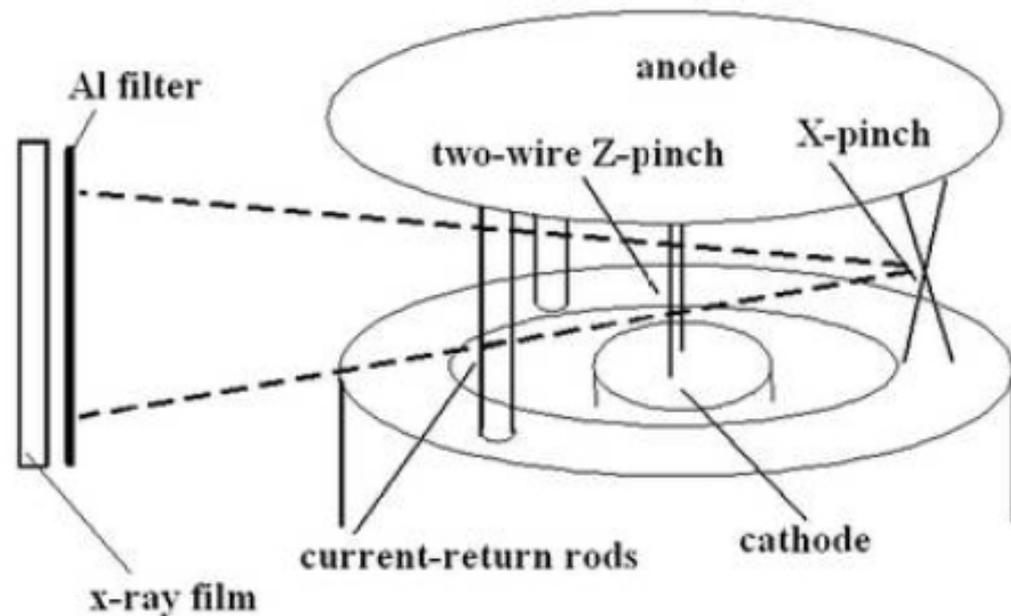
# Overview: Pulsed Power Generator (PPG-1), Beijing



Experimental arrangements for backlighting of Z-pinch using X-pinch as x-ray source


## X-ray backlighting images of two-wire z-pinch

X-pinch: two 13  $\mu\text{m}$  Mo wires


Z-pinch: two 50  $\mu\text{m}$  Mo wires

a) 61 ns and 155 kA, shot No.2009042216

b) 86 ns and 215 kA, shot No.2009060417

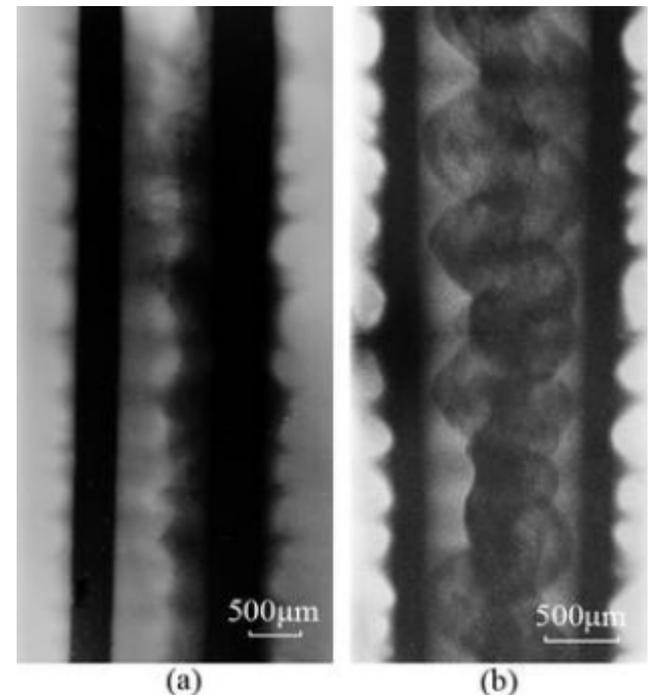

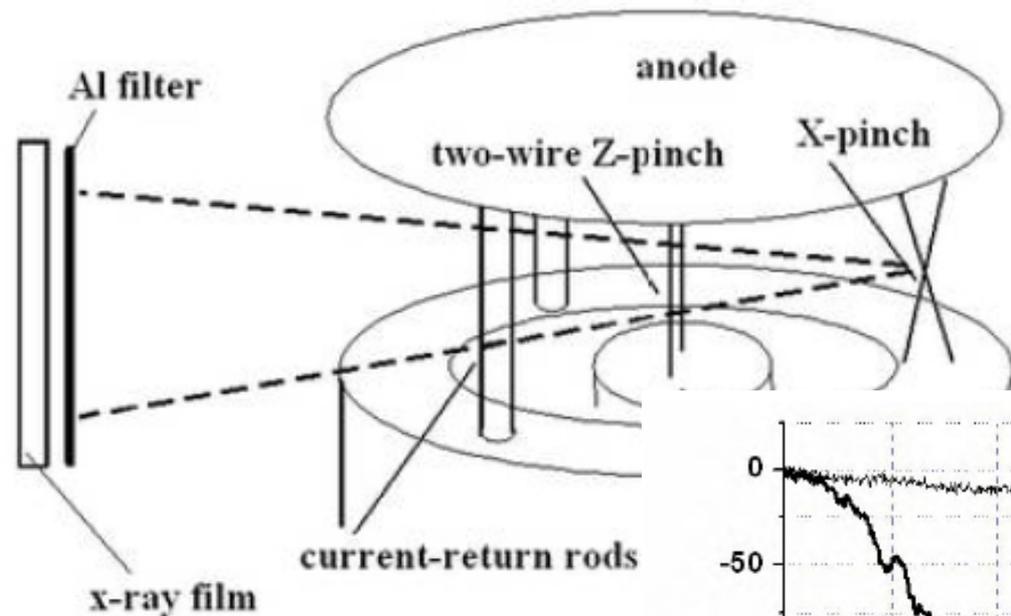
# Overview: Pulsed Power Generator (PPG-1), Beijing




Experimental arrangements for backlighting of Z-pinch using X-pinch as x-ray source

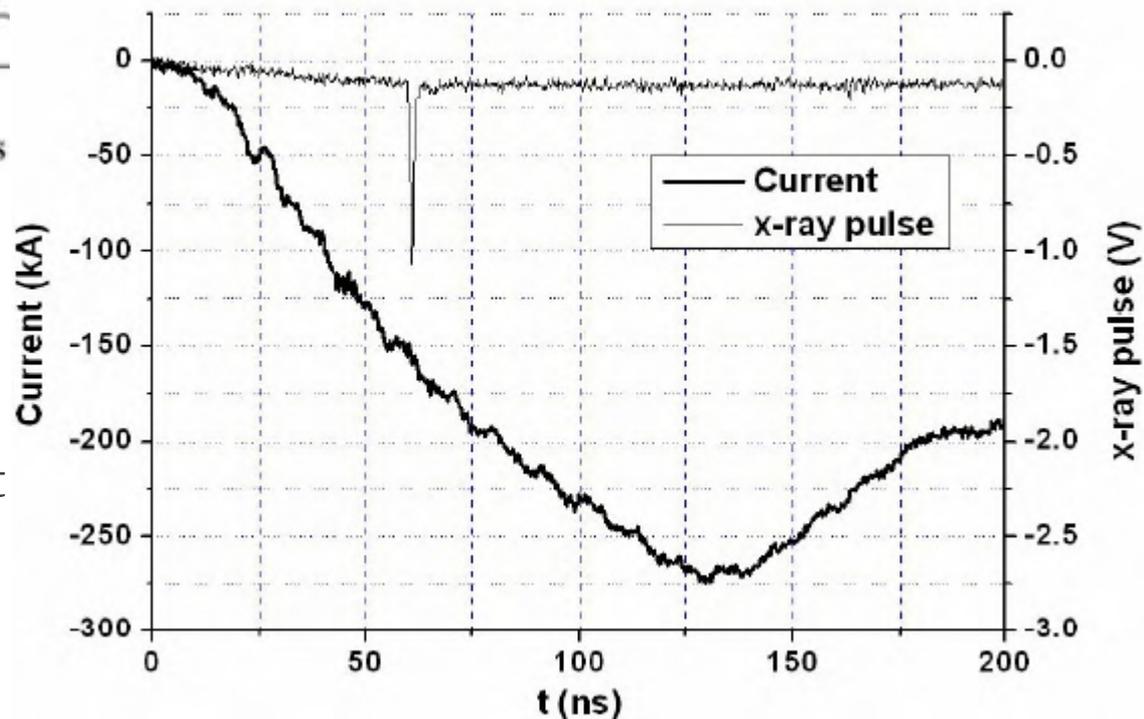Waveforms of the x-ray pulse and the Z-pinch current for shot NO. 2009042216.


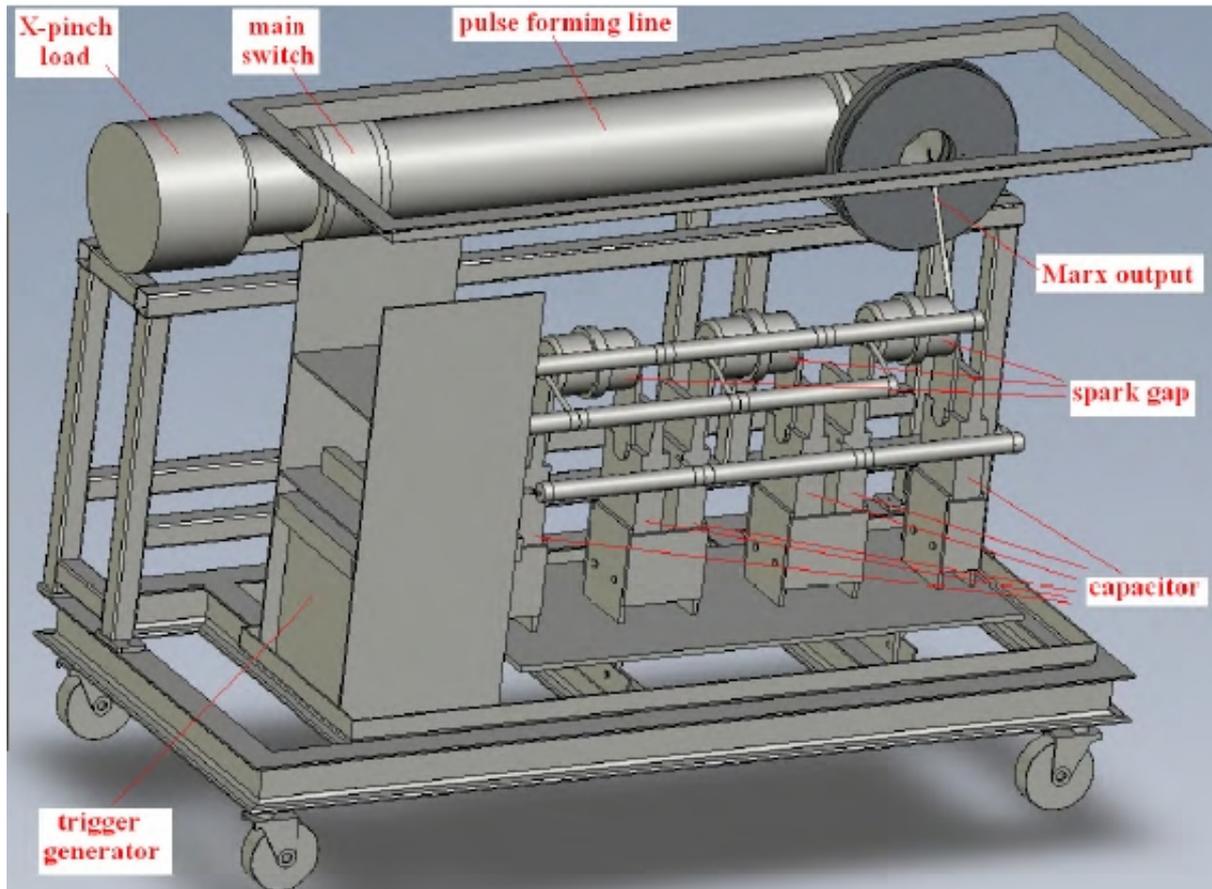
# Overview: Compact Table-Top X-Pinch Device, Beijing



The size of the device:

2m in length,

1.1m in width,

1.2m in height

current: 100 kA

pulse width: 60 ns

impedance: 1.2  $\Omega$

Fig.8. Design drawing of the compact table-top X-pinch device

# Overview: Laboratory of Plasma Studies, Cornell University

## XP facility


- \* 470 kA peak current
- \* 100 ns pulse duration

## X-Pinch 1 and 2 (backlighter)

- \* 235 kA peak current
- \* Two 17-30  $\mu\text{m}$  Mo wires
- \* 1.5 cm long
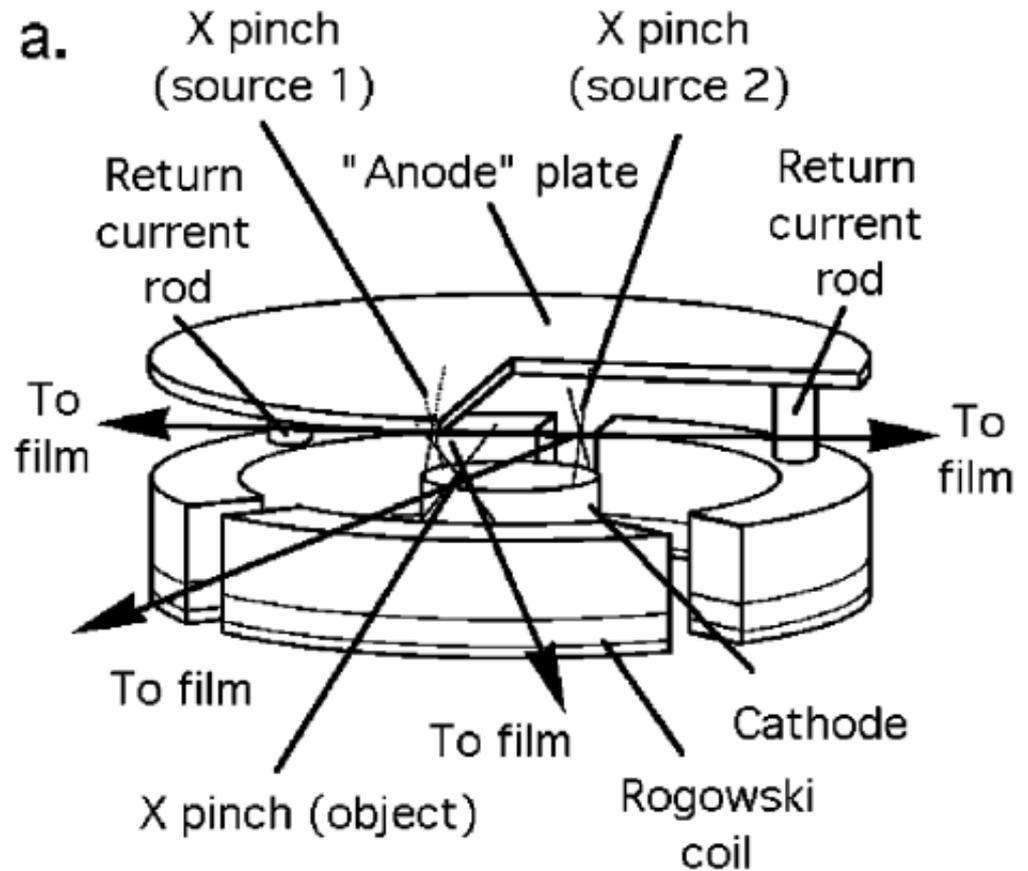
## Object X-Pinch

- \* 90-120 kA peak current
- \* W, Mo, Au, or Al wires
- \* 1.5 cm long



# Overview: Laboratory of Plasma Studies, Cornell University

## XP facility


- \* 470 kA peak current
- \* 100 ns pulse duration

## X-Pinch 1 and 2 (backlighter)


- \* 235 kA peak current
- \* Two 17-30  $\mu\text{m}$  Mo wires
- \* 1.5 cm long
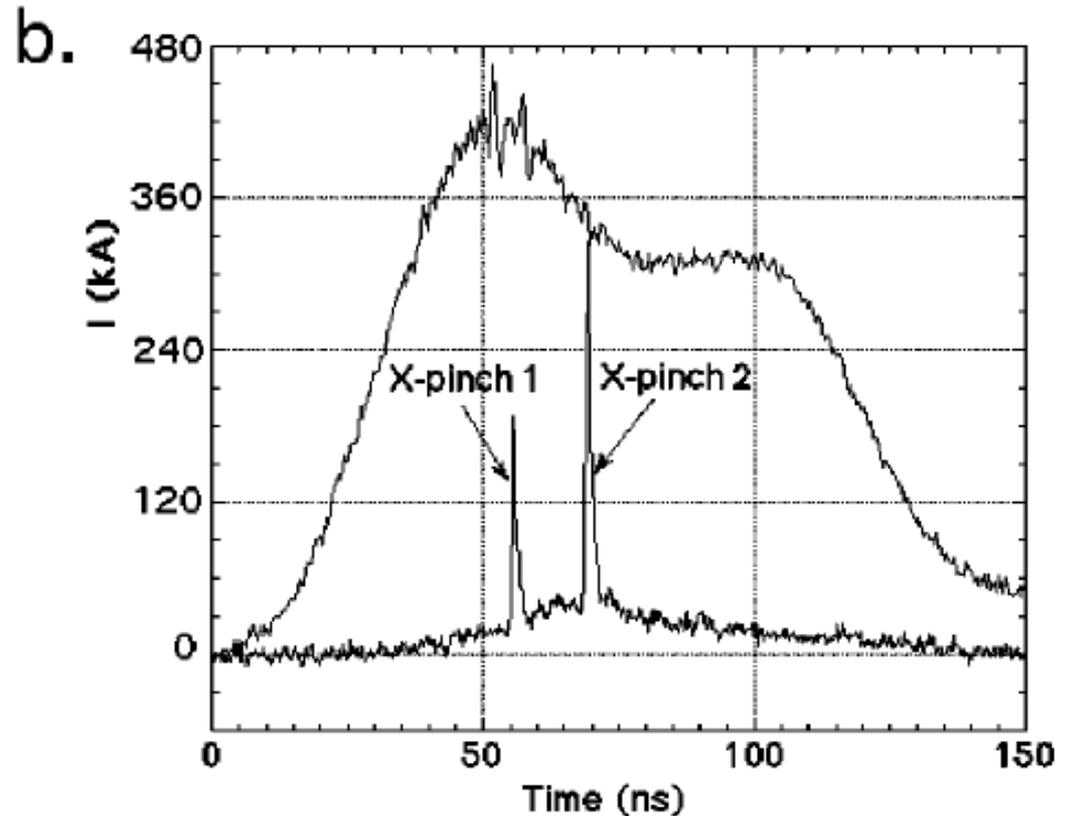
## Object X-Pinch

- \* 90-120 kA peak current
- \* W, Mo, Au, or Al wires
- \* 1.5 cm long


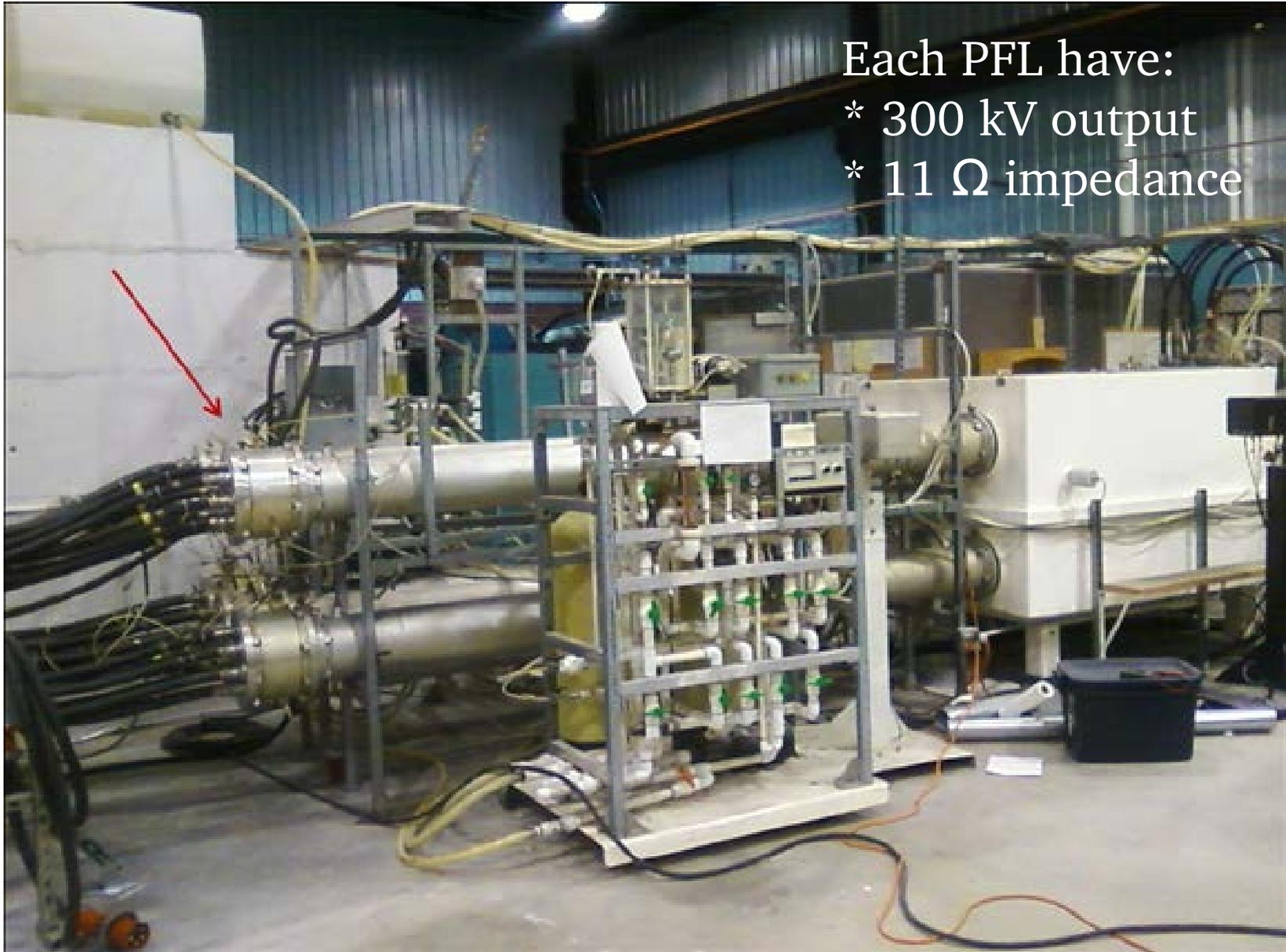
# ISIS Induction-Cell Driver: 5 Pulse Forming Lines



Each PFL have:

- \* 300 kV output

- \* 11  $\Omega$  impedance

# ISIS Induction-Cell Driver: X Pinch Radiation Source

**Step 1:** Combine five 300 kV Pulse Forming Lines (PFLs) into one low impedance ( $< 1 \text{ Ohm}$ ) output (impedance transformer).

**Step 2.** Fed this transformer into Vacuum Chamber

**Step 3.** Maximize current at X – Pinch

Design Criteria: simplicity, low-cost, high reliability

# ISIS Induction-Cell Driver: 5 Pulse Forming Lines


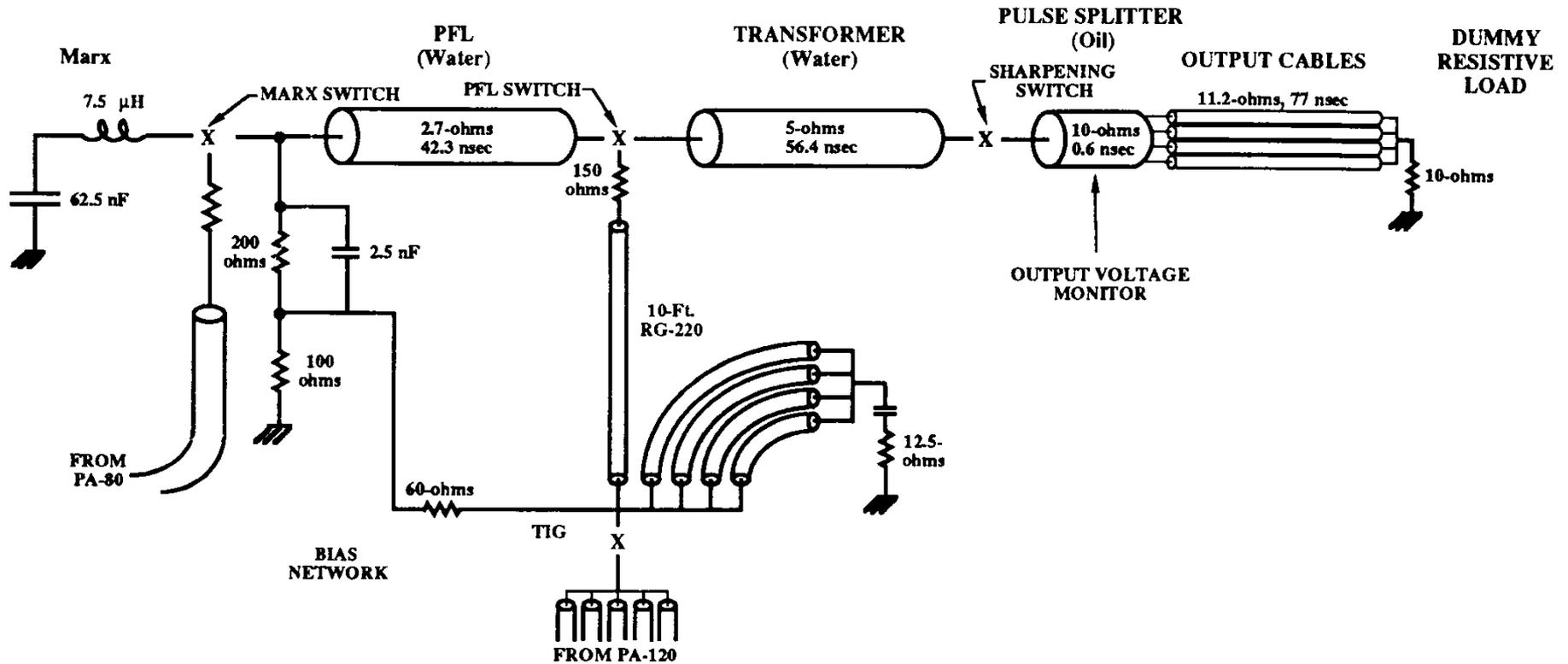


Figure 1. Prototype power supply circuit.

*P. Corcoran et al.* "Experimental Tests of the Power Supply and Prototype Cell for 1.5 MeV SLIA Accelerator Unit", Particle Accelerator Conference, 1991 IEEE
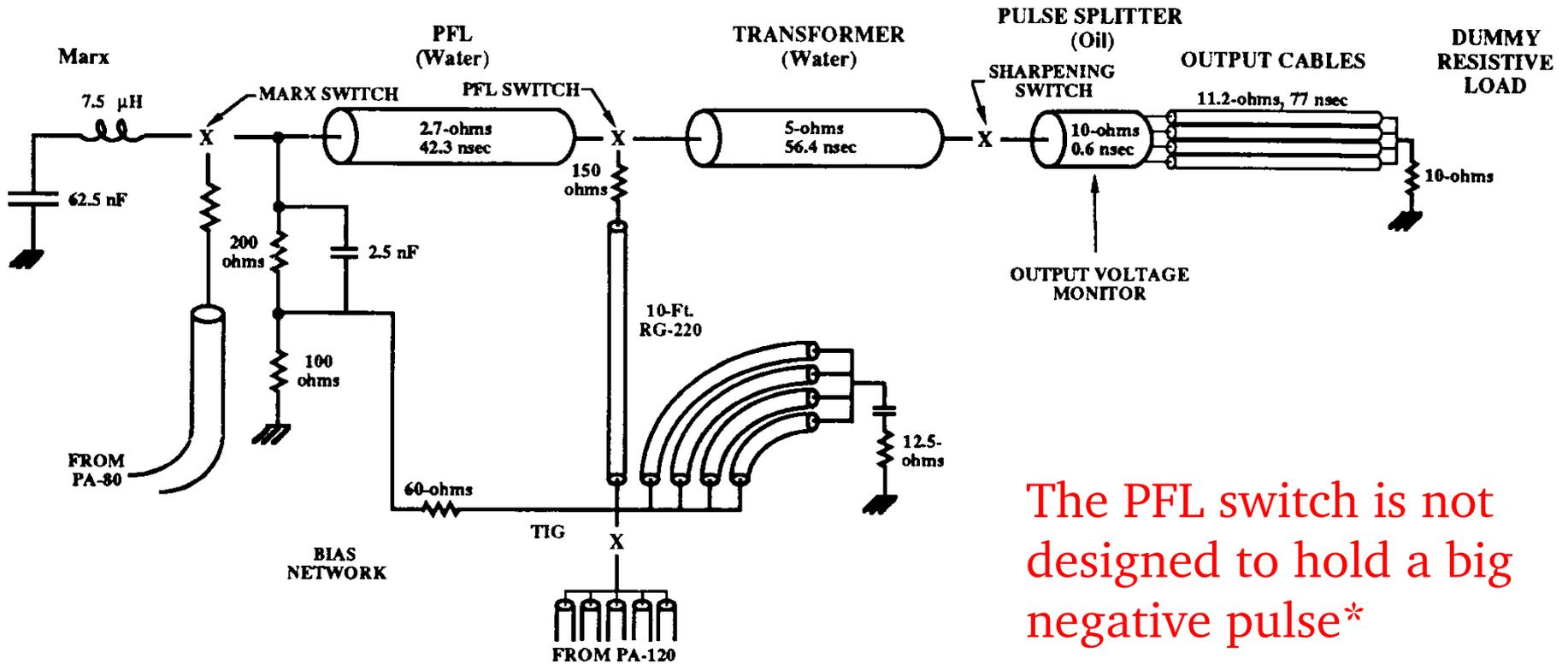
# ISIS Induction-Cell Driver: 5 Pulse Forming Lines




The PFL switch is not designed to hold a big negative pulse\*



Figure 1. Prototype power supply circuit.

\*From private talk with Dr. V. Dimitrov
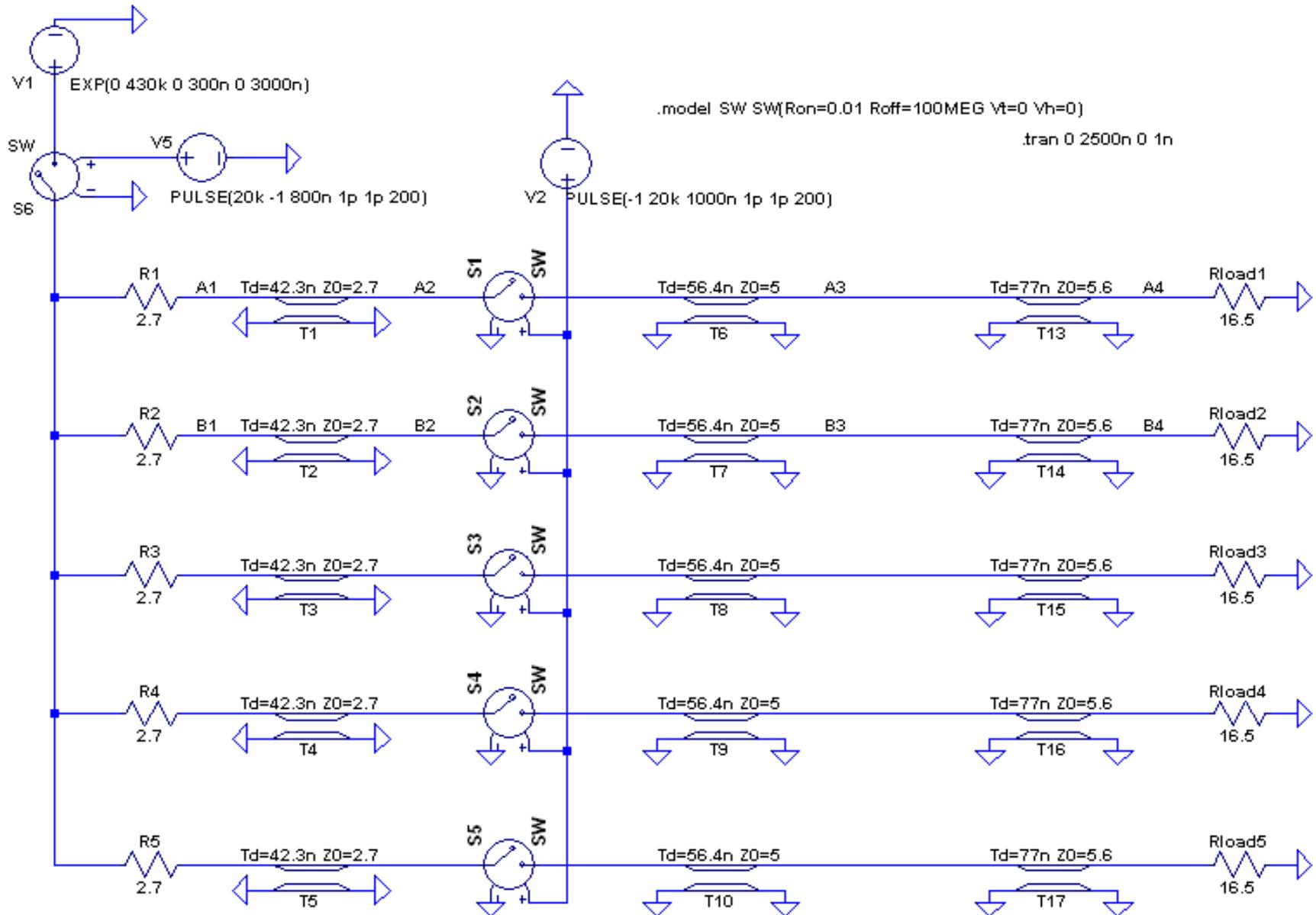
# ISIS Induction-Cell Driver: LTspice schematics



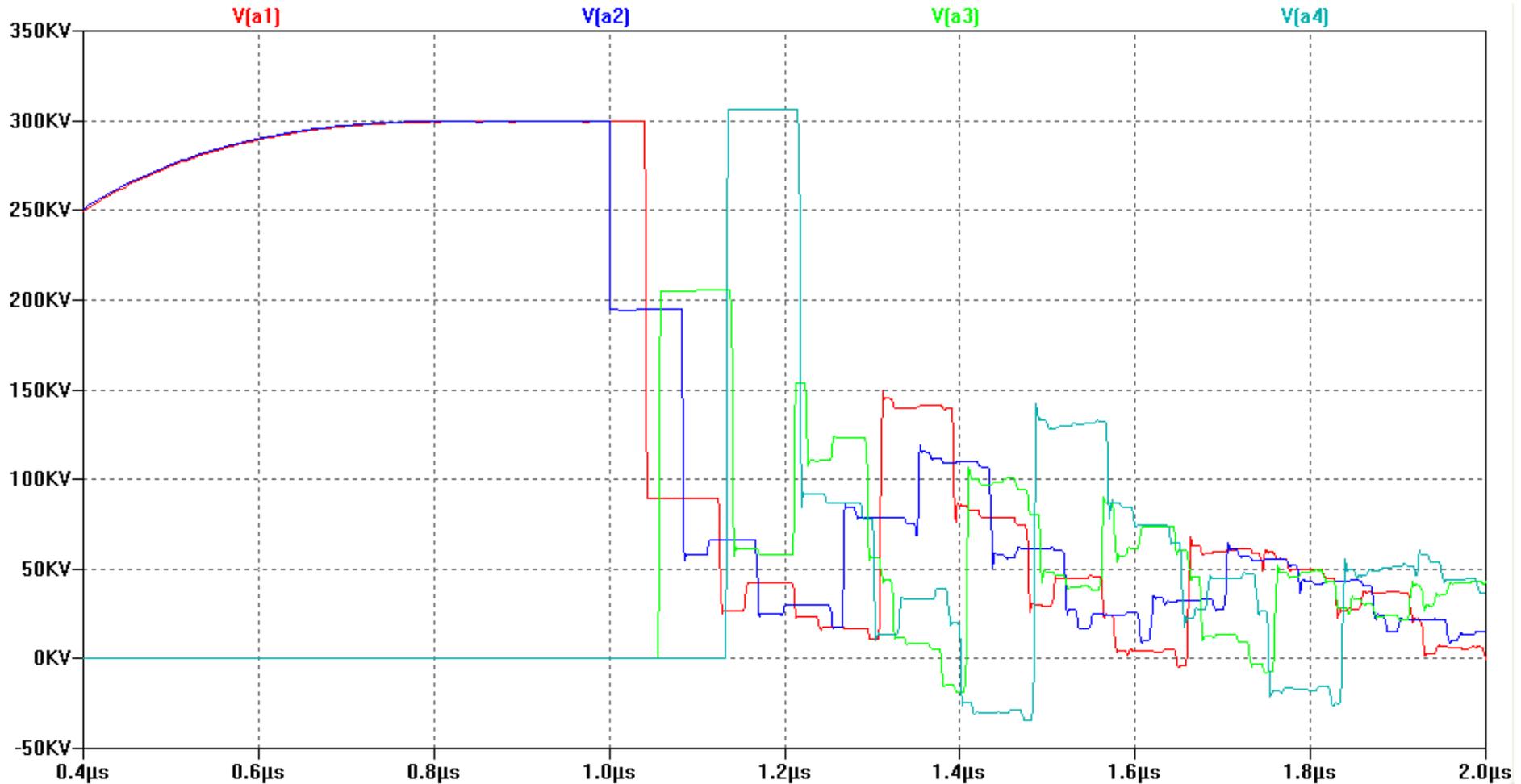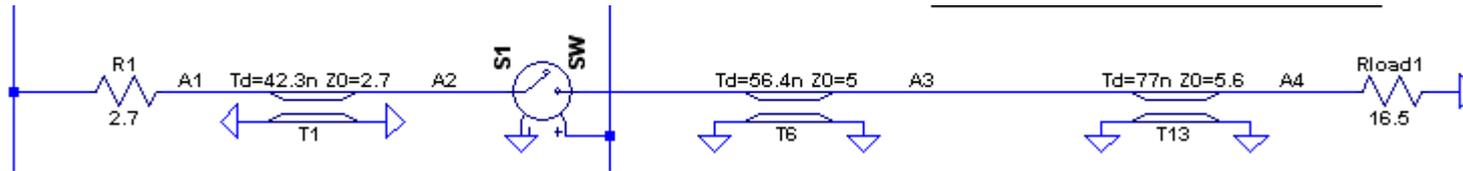
# ISIS Induction-Cell Driver: LTspice simulation



# Wire resistance and inductance


material	$\rho, 10^{-8}$ $\Omega \cdot m$	L, mm	d, $\mu m$	R, $\Omega$	L, nH	L, nH
Au	2.44	15	30	0.52	20.6	18.5
Al	2.82	15	30	0.60	20.6	18.5
Mo	5.20	15	30	1.10	20.6	18.5
W	5.60	15	30	1.19	20.6	18.5
Au	2.44	15	40	0.29	19.7	17.6
Al	2.82	15	40	0.34	19.7	17.6
Mo	5.20	10	40	0.41	12.3	10.9
W	5.60	10	40	0.45	12.3	10.9
Au	2.44	15	50	0.19	19.0	16.9
Al	2.82	15	50	0.22	19.0	16.9
Mo	5.20	15	50	0.40	19.0	16.9
W	5.60	15	50	0.43	19.0	16.9
Au	2.44	15	75	0.08	17.8	15.7
Al	2.82	15	75	0.10	17.8	15.7
Mo	5.20	15	75	0.18	17.8	15.7
W	5.60	15	75	0.19	17.8	15.7
Au	2.44	15	100	0.05	16.9	14.9
Al	2.82	15	100	0.05	16.9	14.9
Mo	5.20	15	100	0.10	16.9	14.9
W	5.60	15	100	0.11	16.9	14.9

# ISIS Induction-Cell Driver + X-Pinch

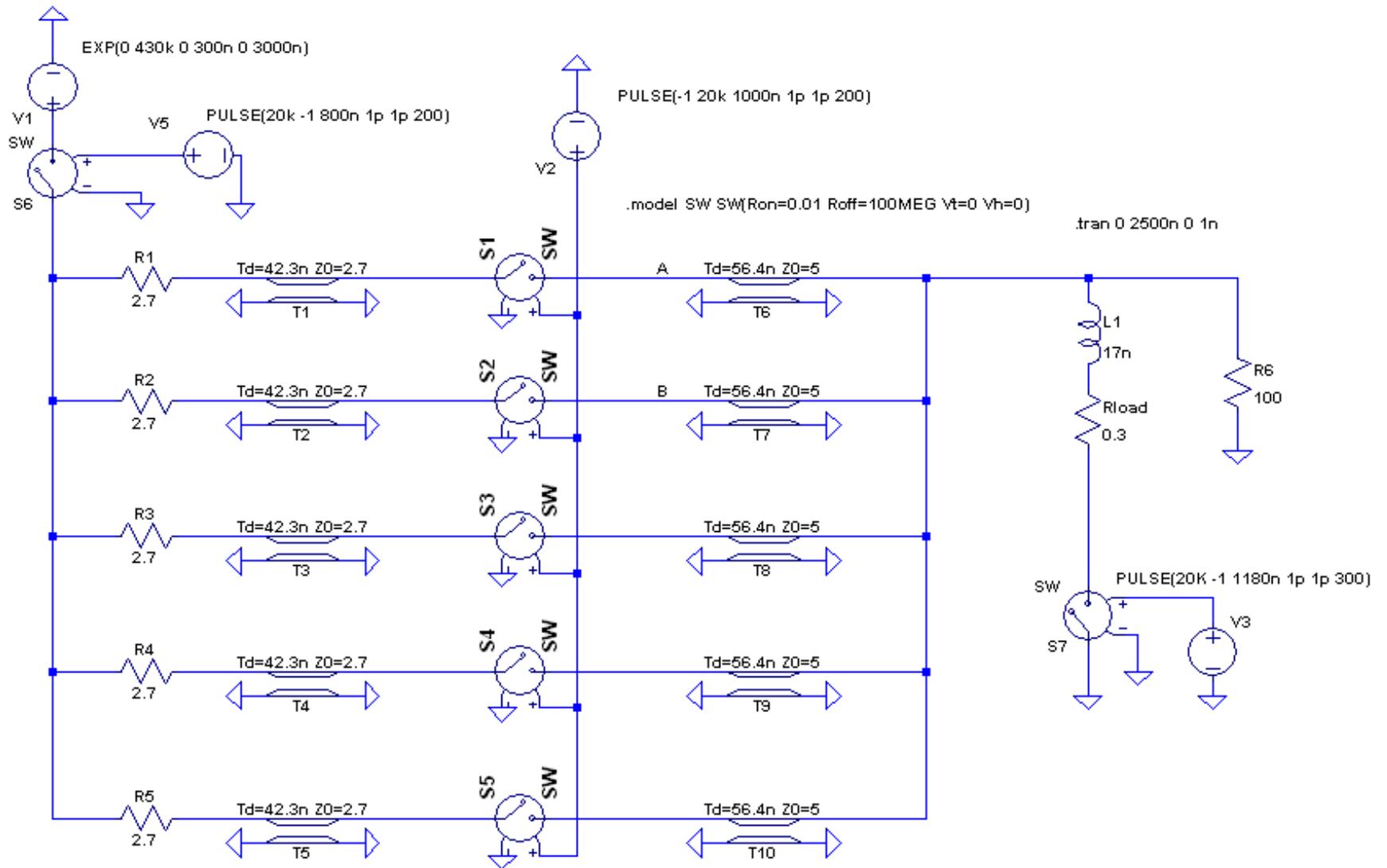


# ISIS Induction-Cell Driver + X-Pinch: **fire**

300 kA current  
-120 kV at SW

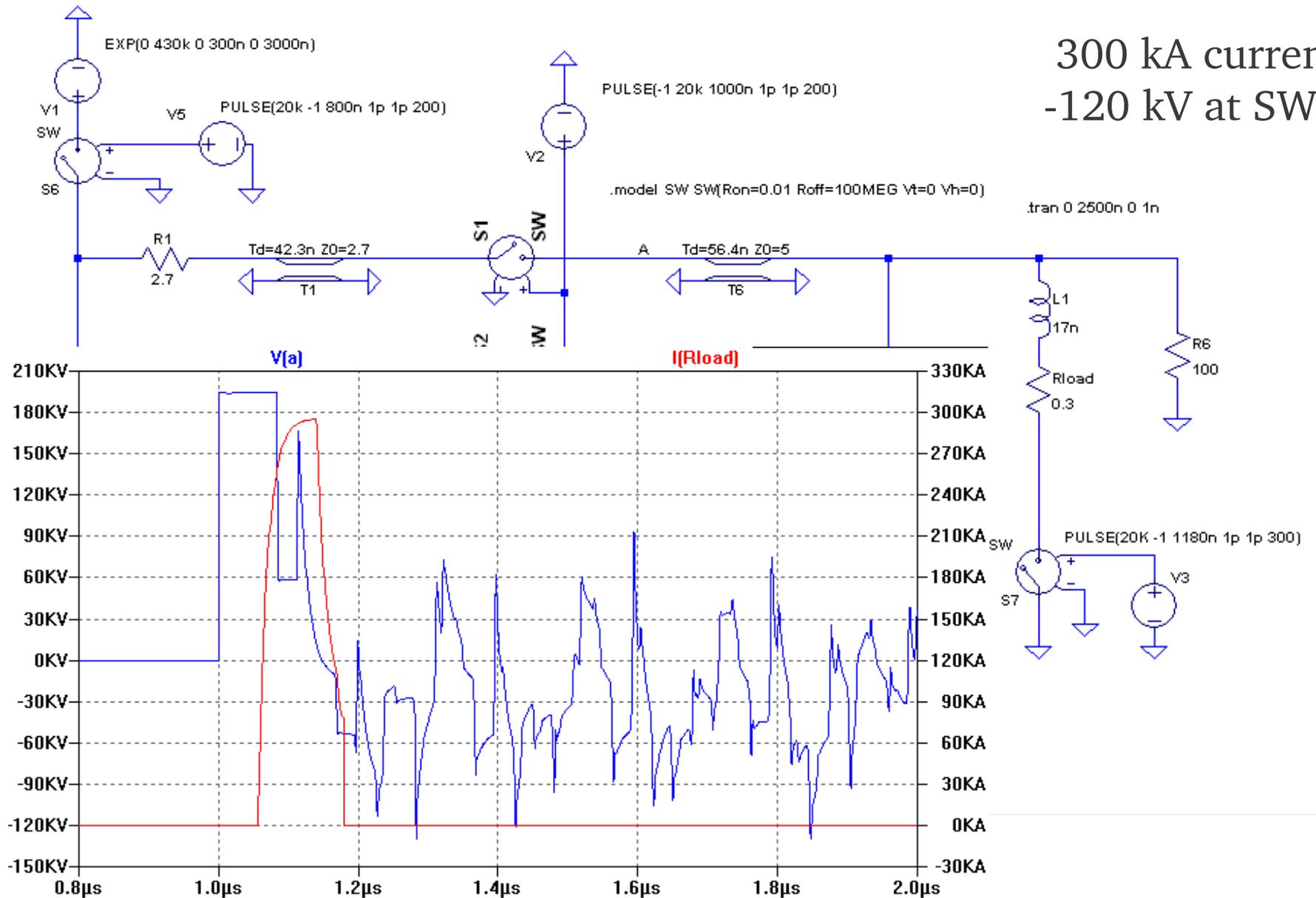
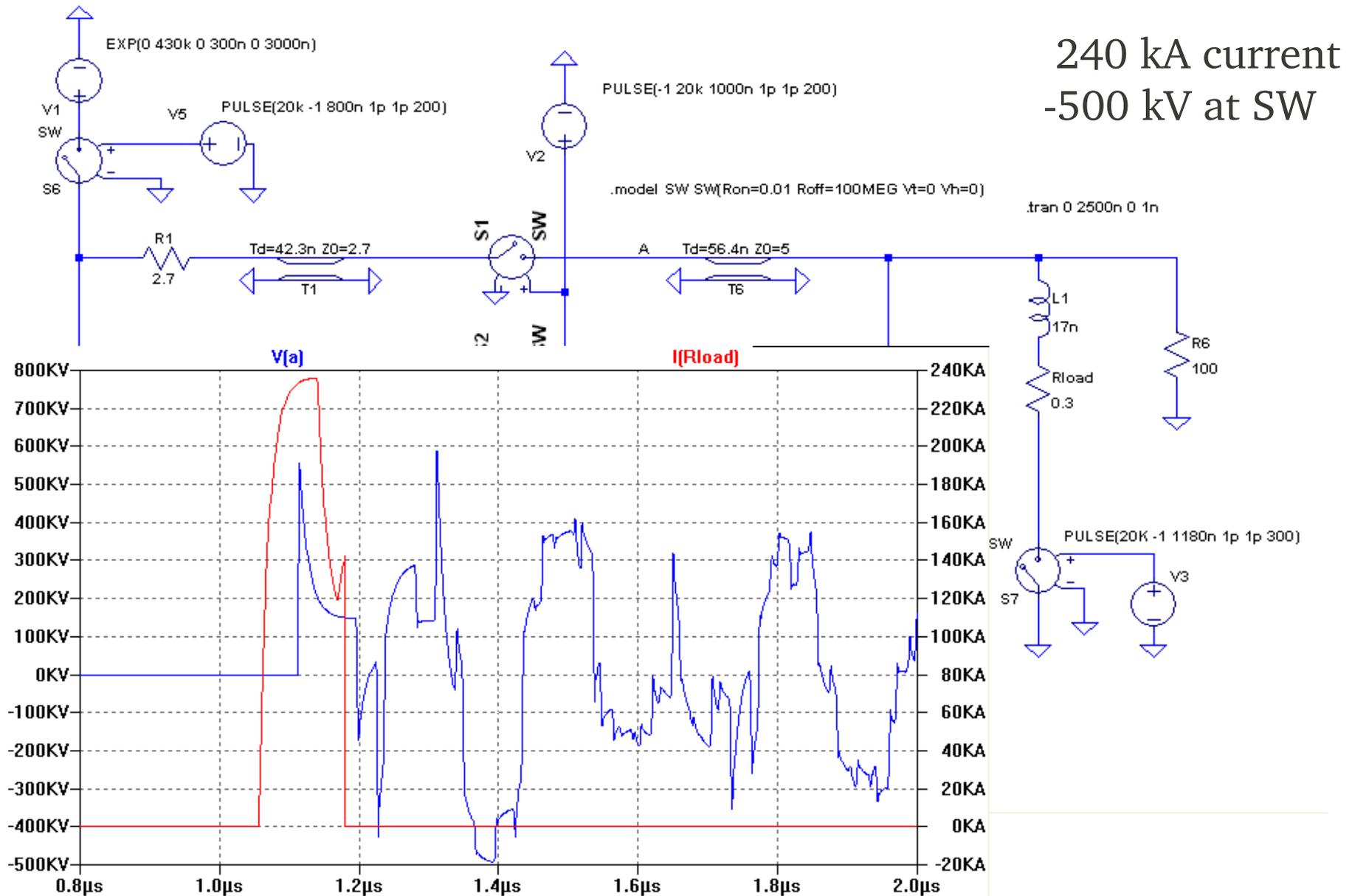
# ISIS Induction-Cell Driver + X-Pinch: **misfire**



# ISIS Induction-Cell Driver + X-Pinch: **danger**


## **Danger:**

The negative pulse at PFL switch will probably destroy the Induction Cell Driver


## **Solution:**

Minimize the possible dangerous negative wave at PFL switch

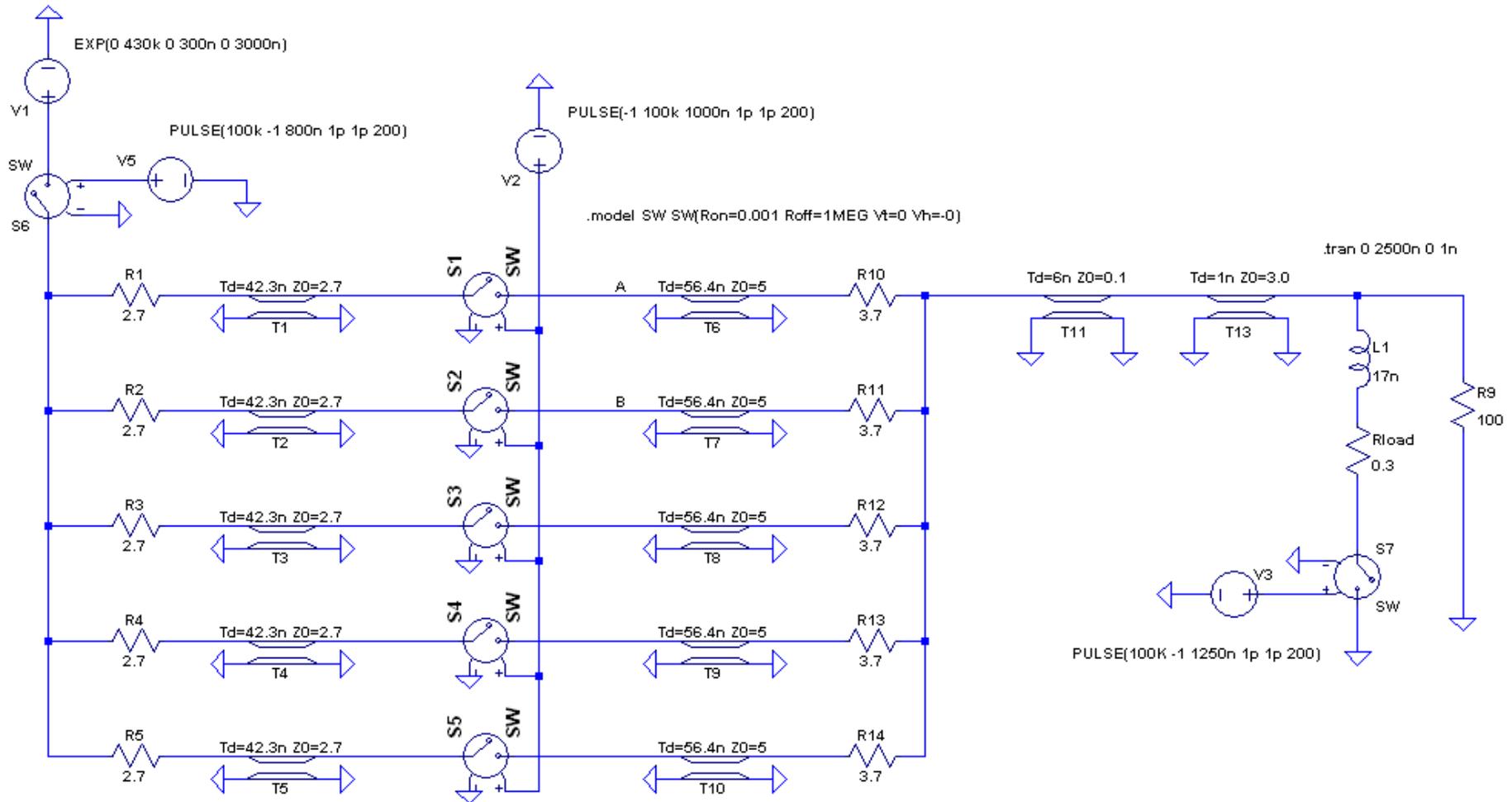
# ISIS Induction-Cell Driver + Transformer: $0.3 \Omega$ load


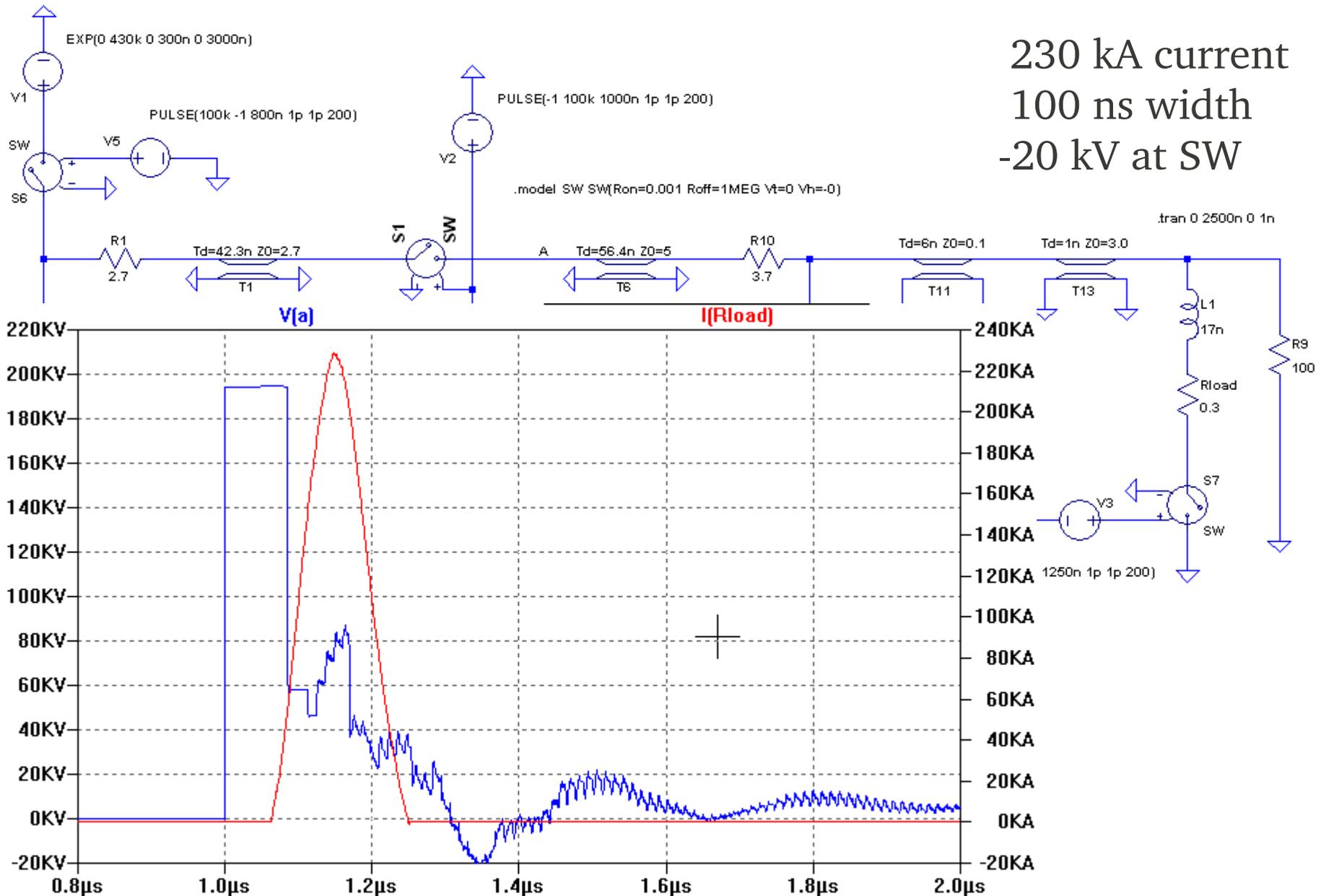
# ISIS ICD + Transformer: $0.3 \Omega$ load, fire


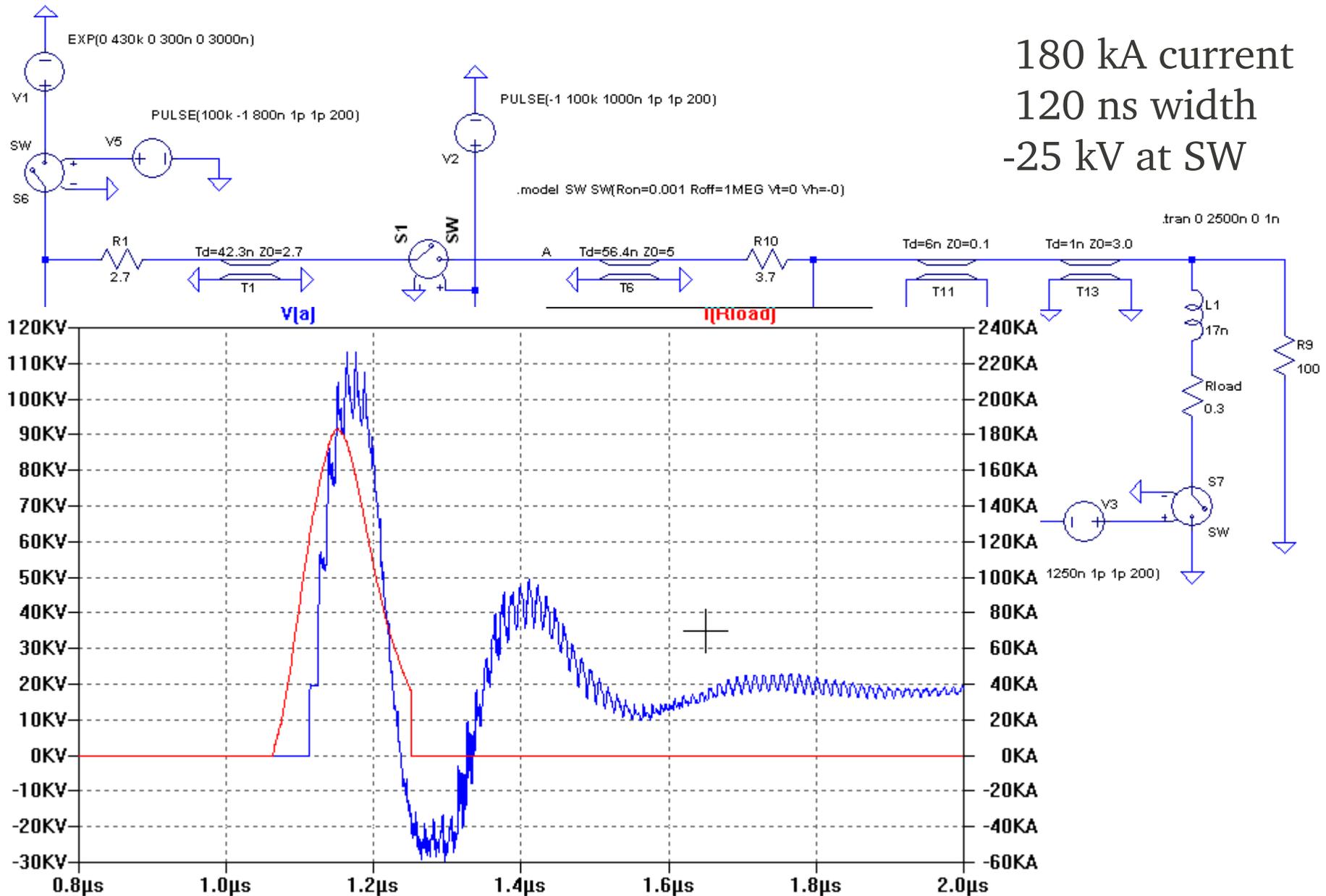
# ISIS ICD + Transformer: 0.3 $\Omega$ load, misfire




# Modified ISIS Induction-Cell Driver: **What We Need**

1. Five high power resistors:  $3.7 \Omega$  each

2. Transformer/combiner:

$$T = 6 \text{ ns}$$

$$Z_0 = 0.1 \Omega$$

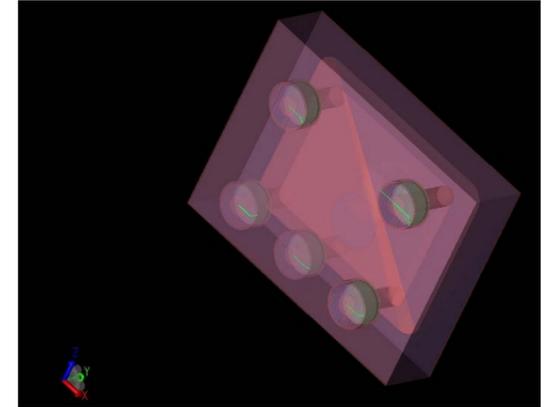

3. Vacuum Chamber:

$$T = 1 \text{ ns}$$

$$Z_0 = 3 \Omega$$



4. X-Pinch wires (Load):

$R = 0.3 \Omega$  and more

$L = 17 \text{ nH}$  and more

$l = 25 \text{ mm}$  long

# Modified ISIS Induction-Cell Driver: **Transformer**

$$T = 6 \text{ ns}$$


$$Z_0 = 0.1 \ \Omega$$

## Transformer Length:

$$30 \text{ cm/ns} * 6 \text{ ns} = 180 \text{ cm (in vacuum)}$$

$$180 \text{ cm} / 9 = 20 \text{ cm (in water)}$$

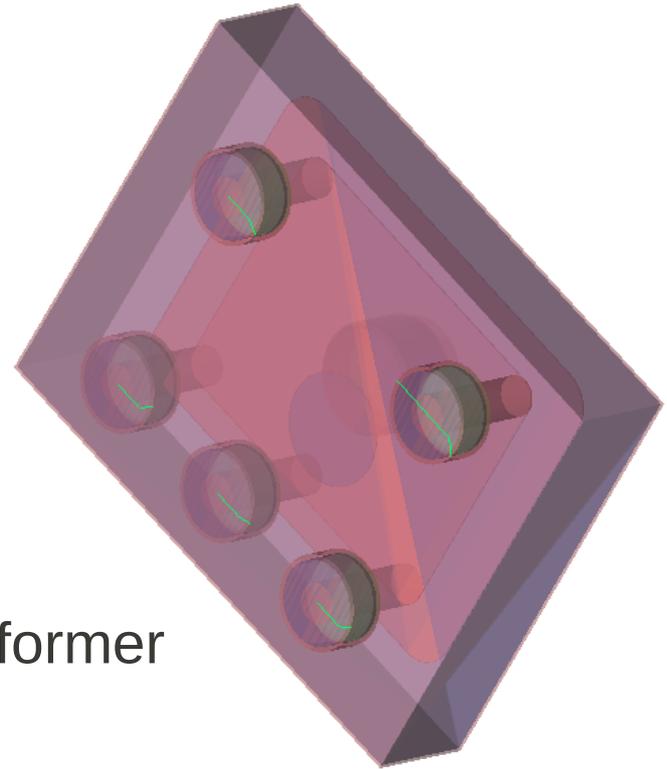We can do 20 cm long water filled transformer



## Transformer Impedance:

$$Z = L/C$$

Challenge to design, but can be done with XFDTD