

ISIS Induction-Cell Driver Modification to High Current X-Pinch Radiation Source

Roman Shapovalov
IAC
Jan 28, 2013

Overview: PPG-1 Tsinghua University, Beijing

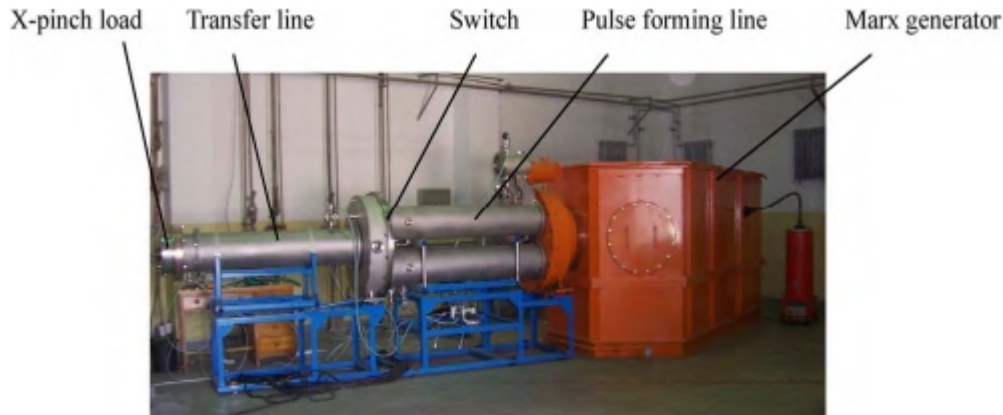


Fig. 1. View of the PPG-I.

Pulsed Power Generator PPG-1

max output current: 400 kA
pulse width: 100 ns

X-Pinch Performance:

output current: ~ 200 kA
X-pinch: two 25 μm (or 13 μm) Mo wires
distance between anode and cathode: 10 mm


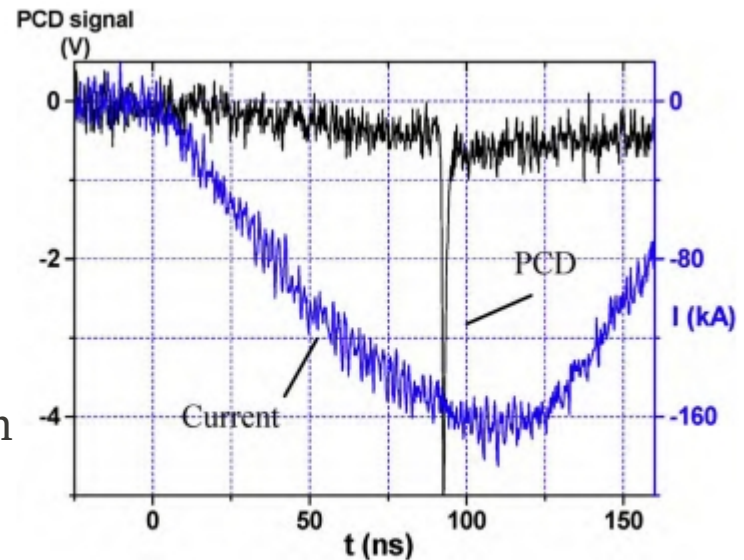


Fig.2. Typical X-ray burst measured with a PCD detector and the load current measured with a Rogowski coil.

Ran Zhang et al. "X-pinch applications in X-ray radiography and design of compact table-top X-pinch device" 2010 IEEE

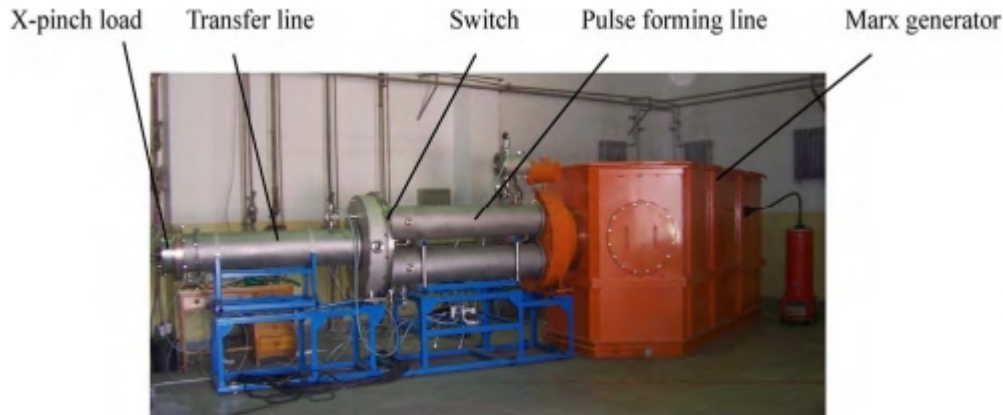Overview: PPG-1 Tsinghua University, Beijing



Pulsed Power Generator PPG-1

max output current: 400 kA
pulse width: 100 ns

Fig. 1. View of the PPG-I.

Backlighting Experiment

X-pinch current: ~ 100 kA
X-pinch: two 13 μm Mo wires
Z-pinch: two 50 μm Mo wires
anode/cathode distance: 10 mm

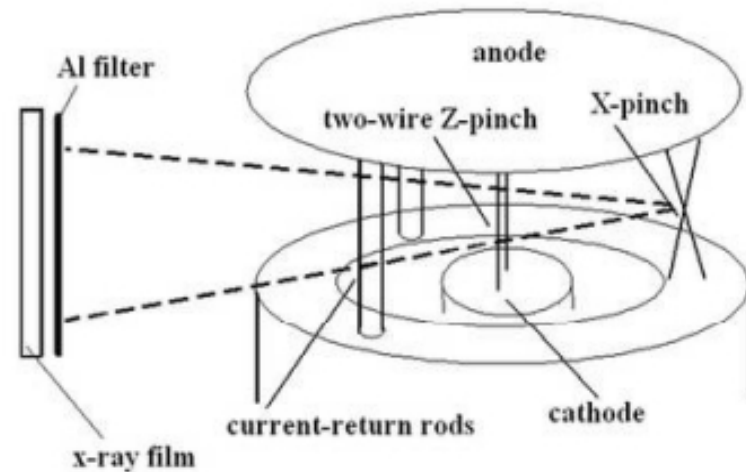


Fig. 3. Experimental arrangements for backlighting of Z-pinch using X-pinch as x-ray source.

Ran Zhang *et al.* "X-pinch applications in X-ray radiography and design of compact table-top X-pinch device" 2010 IEEE

Overview: PPG-1 Tsinghua University, Beijing

Compact Table-Top X-Pinch Device

output current: 100 kA

pulse width: 60 ns

Load: X-pinch with a few μm

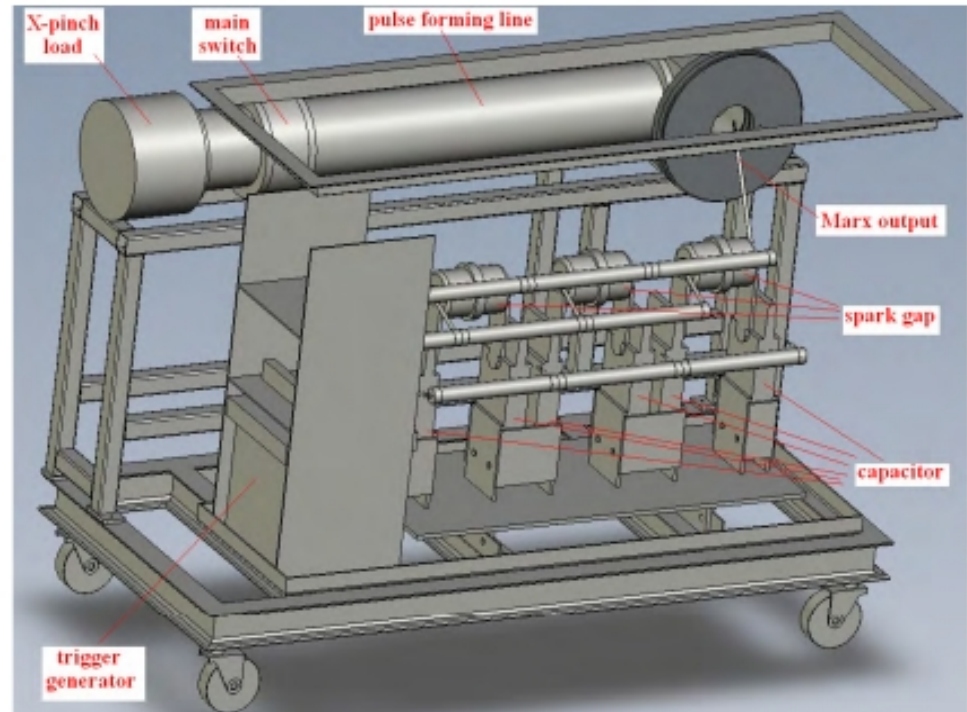


Fig.8. Design drawing of the compact table-top X-pinch device.

Overview: Laboratory of Plasma Studies, Cornell University

XP facility


- * 470 kA peak current
- * 100 ns pulse duration

X-Pinch 1 and 2 (backlighter)

- * 235 kA peak current
- * Two 17-30 μm Mo wires
- * 1.5 cm long


Object X-Pinch

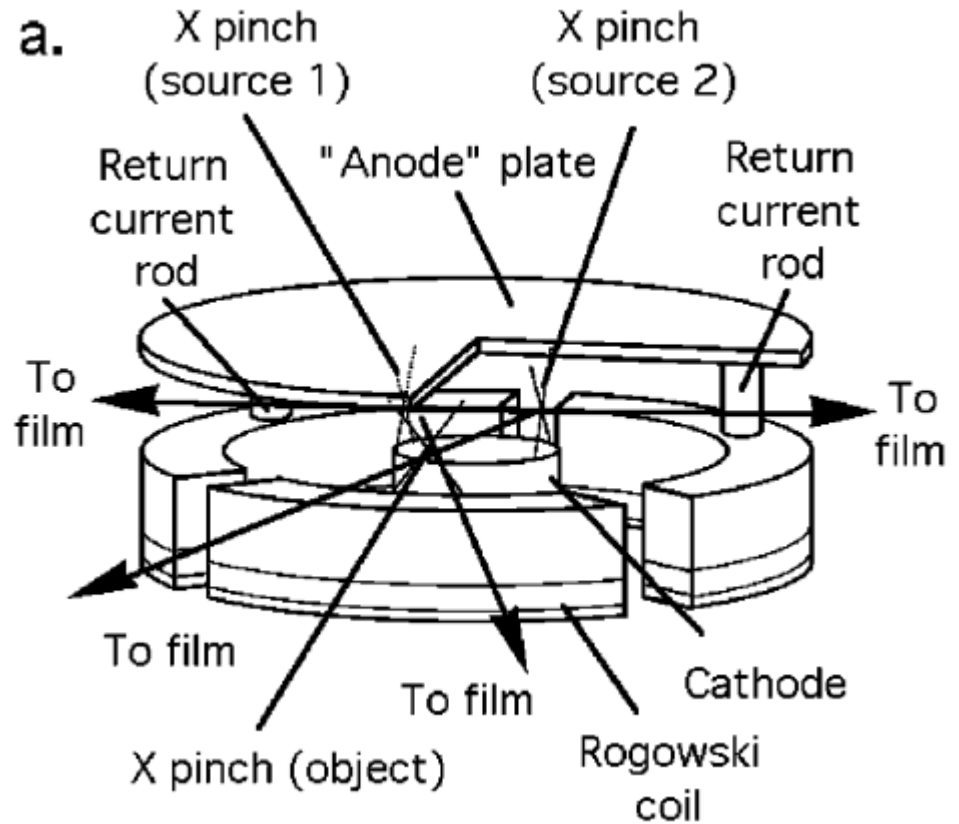- * 90-120 kA peak current
- * W, Mo, Au, or Al wires
- * 1.5 cm long



T. A. Shelkovenko et. al. "Radiographic and spectroscopic studies of X-pinch plasma implosion dynamics and x-ray burst emission characteristics" 2001 AIP

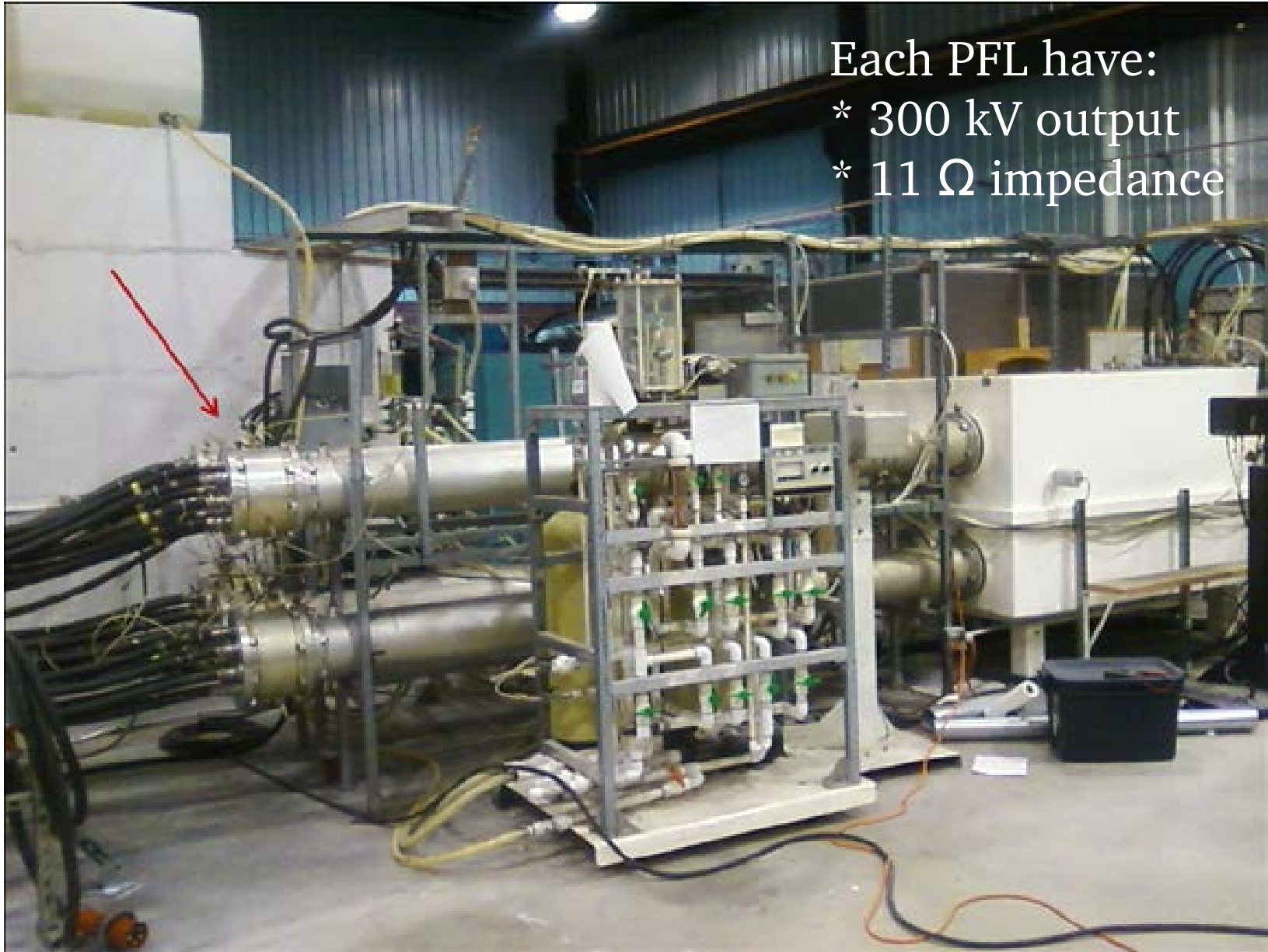ISIS Induction-Cell Driver: 5 Pulse Forming Lines



Each PFL have:

- * 300 kV output

- * 11 Ω impedance

ISIS Induction-Cell Driver: X Pinch Radiation Source

Step 1: Combine five 300 kV Pulse Forming Lines (PFLs) into one low impedance (< 1 Ohm) output (impedance transformer).

Step 2. Fed this transformer into Vacuum Chamber

Step 3. Maximize current at X – Pinch

Design Criteria: simplicity, low-cost, high reliability

ISIS Induction-Cell Driver: 5 Pulse Forming Lines



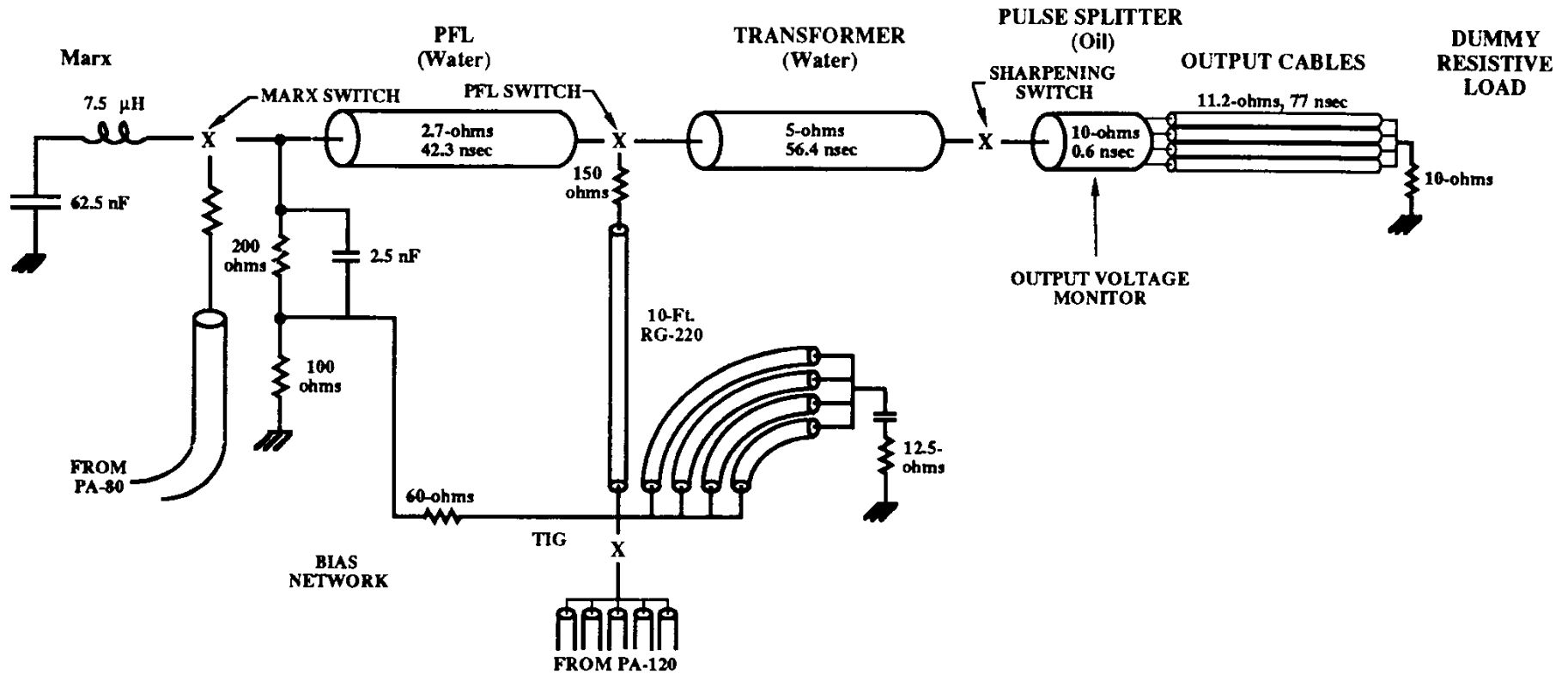


Figure 1. Prototype power supply circuit.

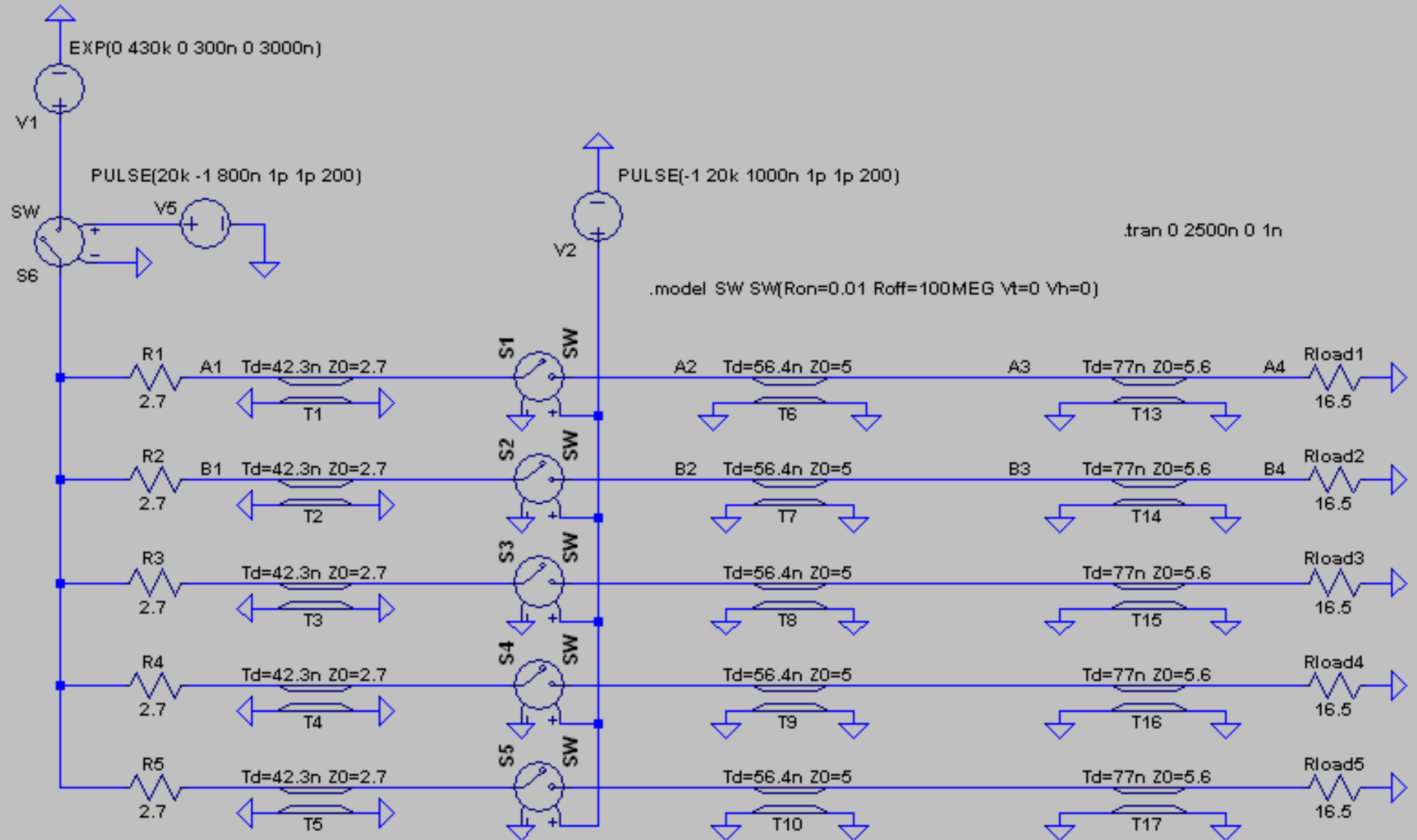
ISIS Induction-Cell Driver: LTspice schematics



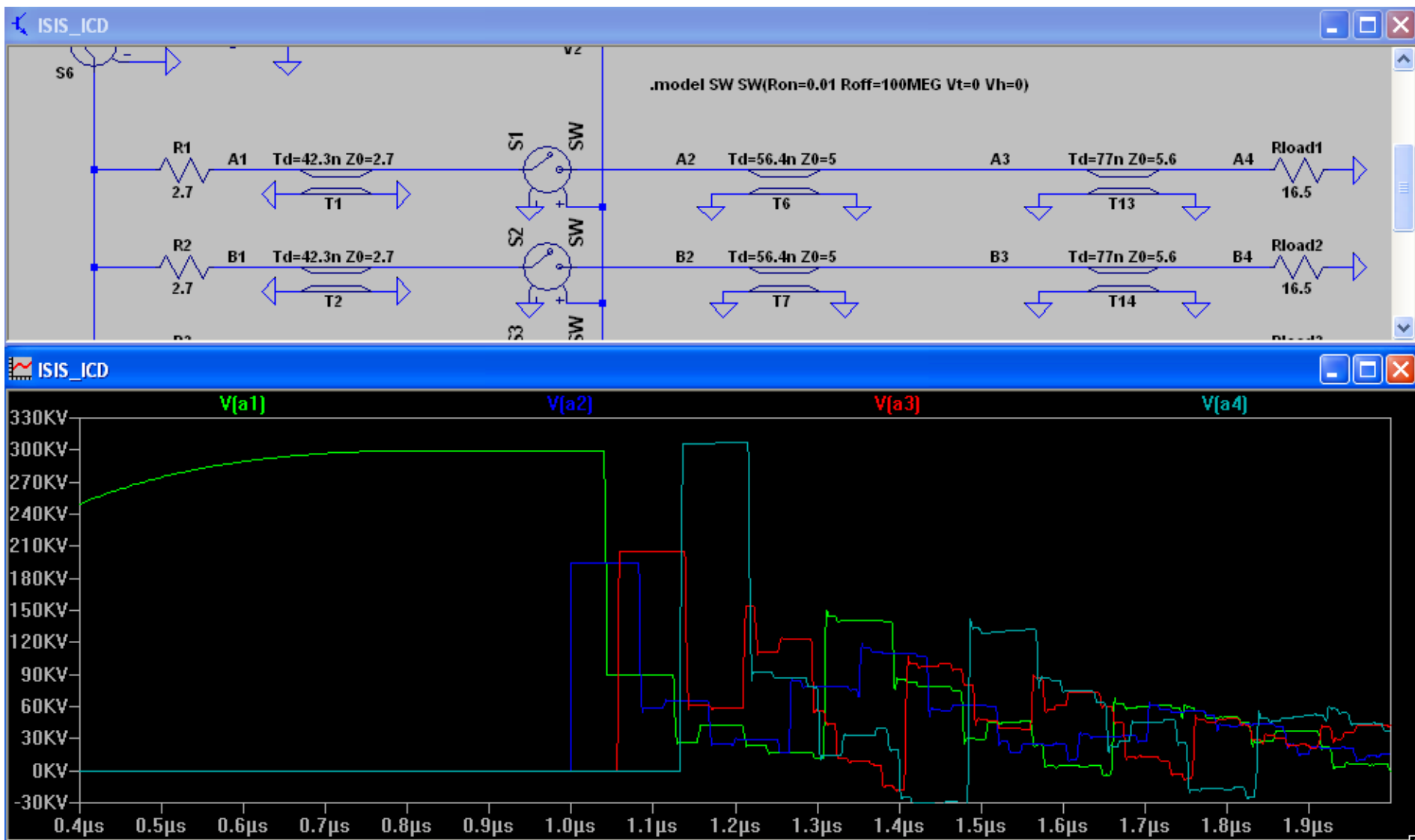ISIS Induction-Cell Driver: LTspice simulation



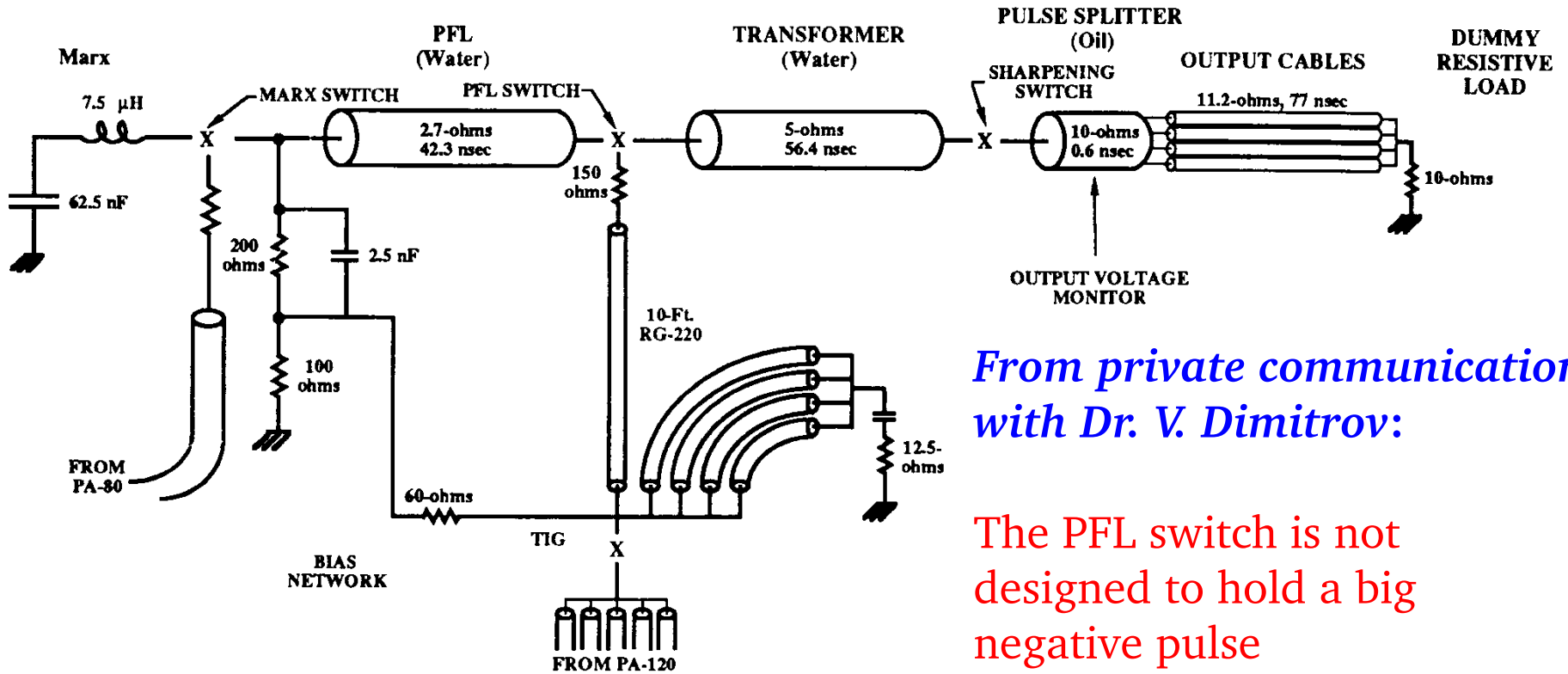ISIS Induction-Cell Driver: 5 Pulse Forming Lines






From private communication with Dr. V. Dimitrov:

The PFL switch is not designed to hold a big negative pulse

Figure 1. Prototype power supply circuit.

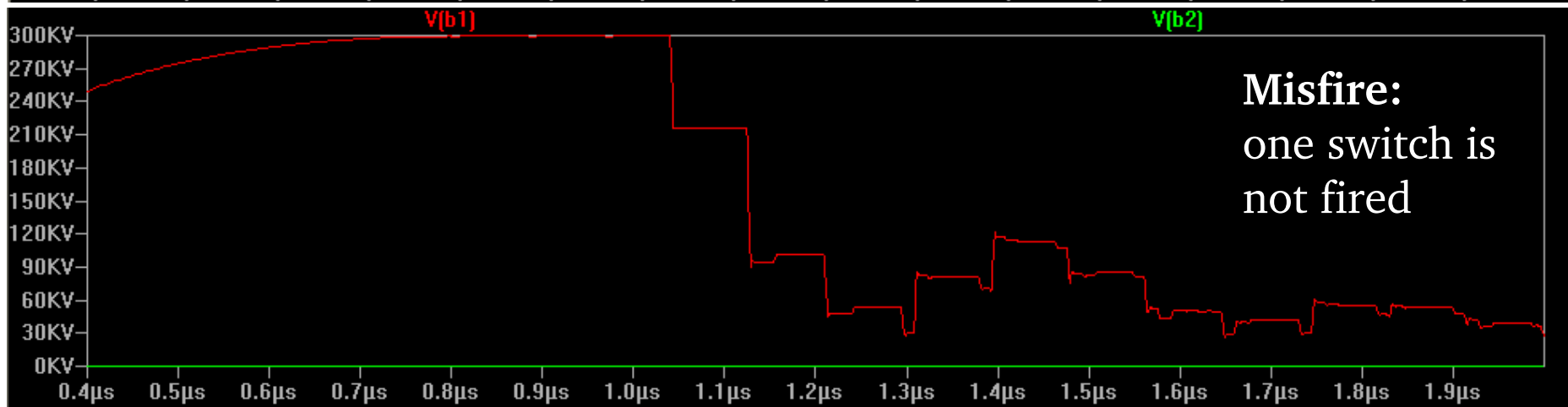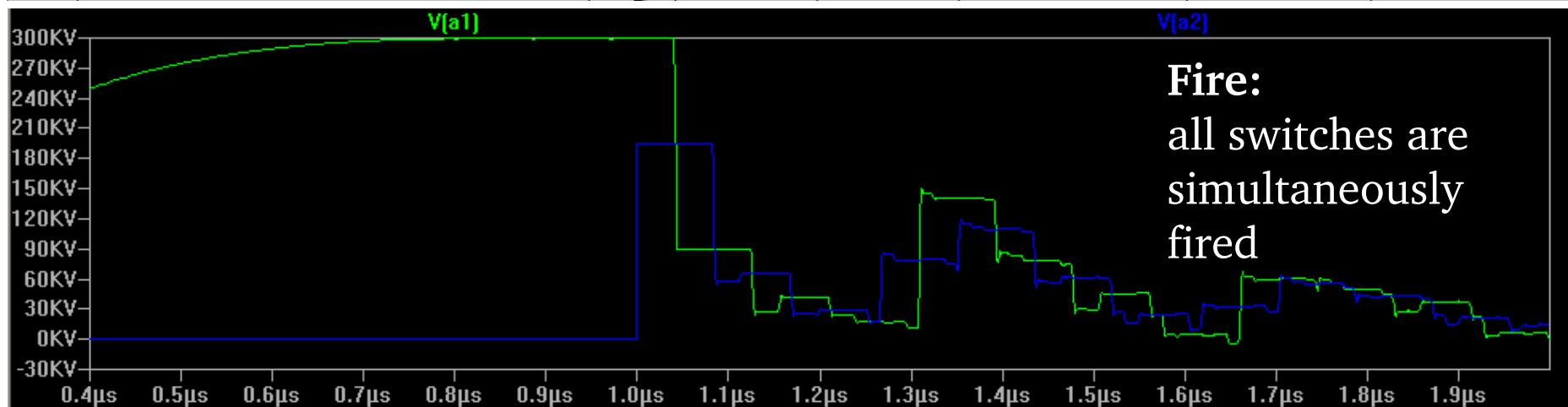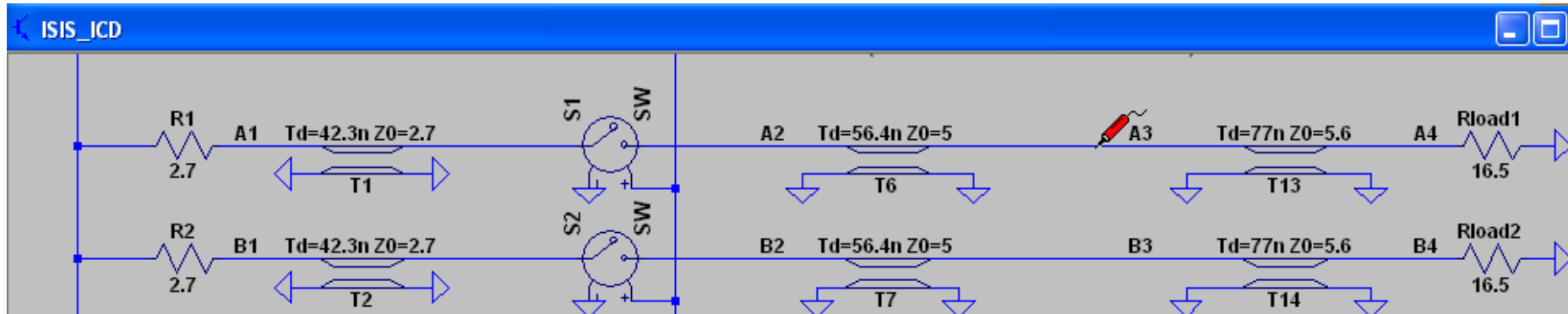ISIS Induction-Cell Driver: fire and misfire



ISIS Induction-Cell Driver: **facts**

From private communication with Dr. V. Dimitrov:

The PFL switch is not designed to hold a big negative pulse


From LTspice simulation:

There are always positive pulse at PFL switch during fire and possible misfire

Wire resistance and inductance


material	ρ , 10^{-8} $\Omega \cdot \text{m}$	L, mm	d, μm	R, Ω	L, <u>nH</u>
Aluminium	2.82	25.00	5	35.92	45.8
Gold	2.44	25.00	5	31.08	45.8
Molybdenum	5.20	25.00	5	66.24	45.8
Tungsten	5.60	25.00	5	71.34	45.8
Aluminium	2.82	25.00	10	8.98	42.3
Gold	2.44	25.00	10	7.77	42.3
Molybdenum	5.20	25.00	10	16.56	42.3
Tungsten	5.60	25.00	10	17.83	42.3
Aluminium	2.82	25.00	30	1.00	36.8
Gold	2.44	25.00	30	0.86	36.8
Molybdenum	5.20	25.00	30	1.84	36.8
Tungsten	5.60	25.00	30	1.98	36.8
Aluminium	2.82	25.00	50	0.36	34.3
Gold	2.44	25.00	50	0.31	34.3
Molybdenum	5.20	25.00	50	0.66	34.3
Tungsten	5.60	25.00	50	0.71	34.3

Modified ISIS Induction-Cell Driver

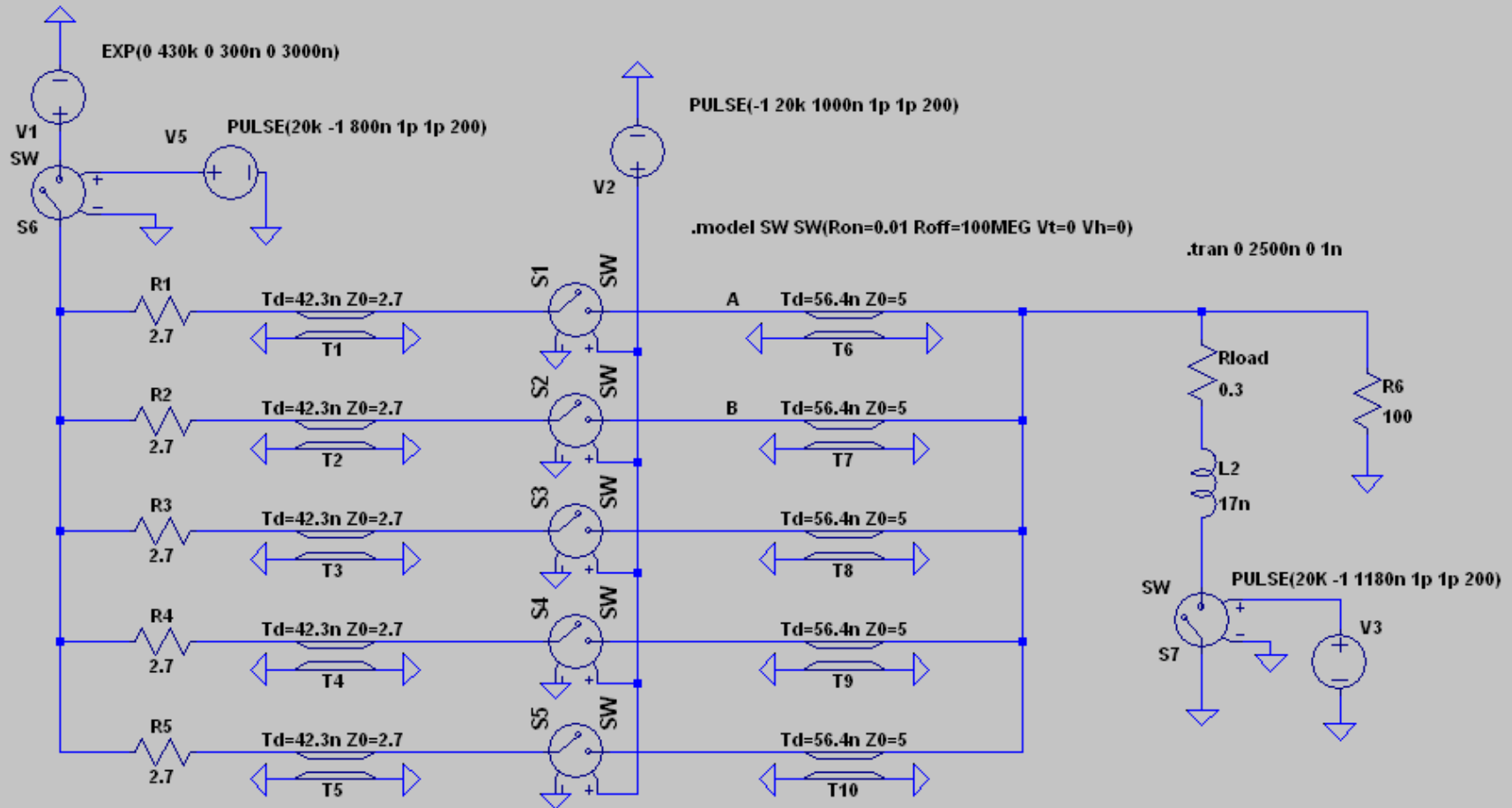


Modified ISIS Induction-Cell Driver: **fire and misfire**

Fire:
300 kA current
-120 kV at S1-S6

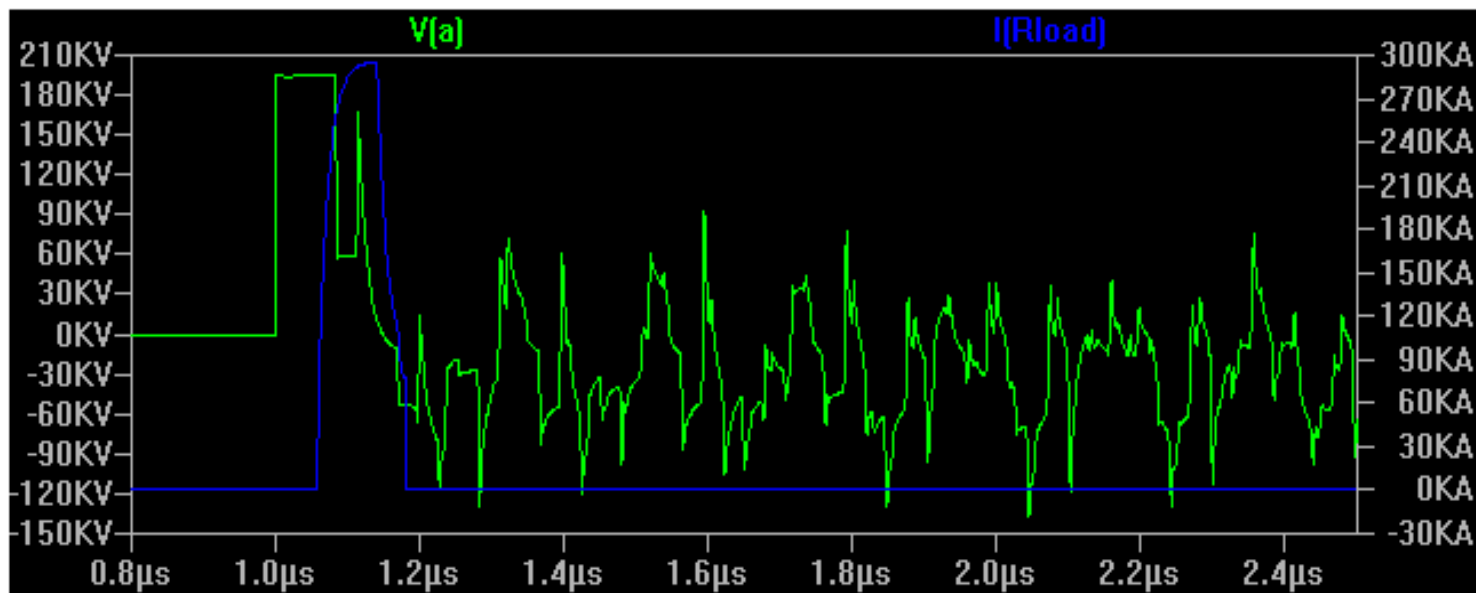

Misfire:

-400 kV
at switch SW2

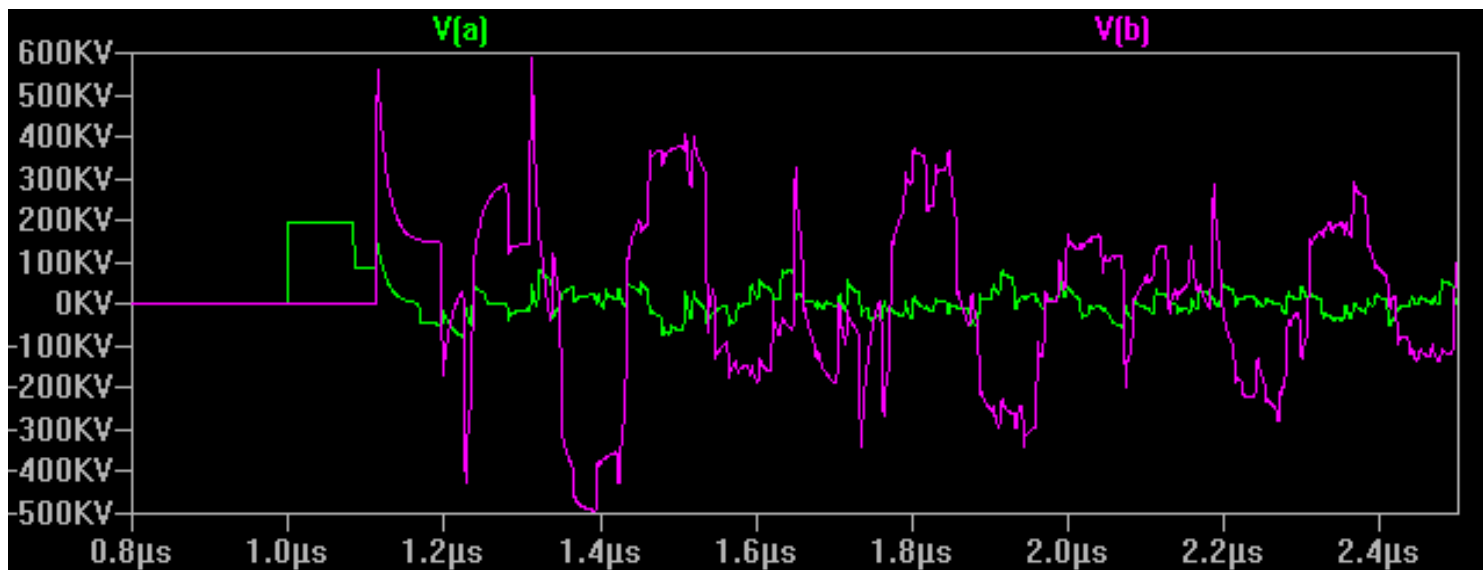

Modified ISIS Induction-Cell Driver


Danger:

The negative pulse at PFL switch will probably destroy the Induction Cell Driver



Solution:

Minimize the possible dangerous negative wave at PFL switch


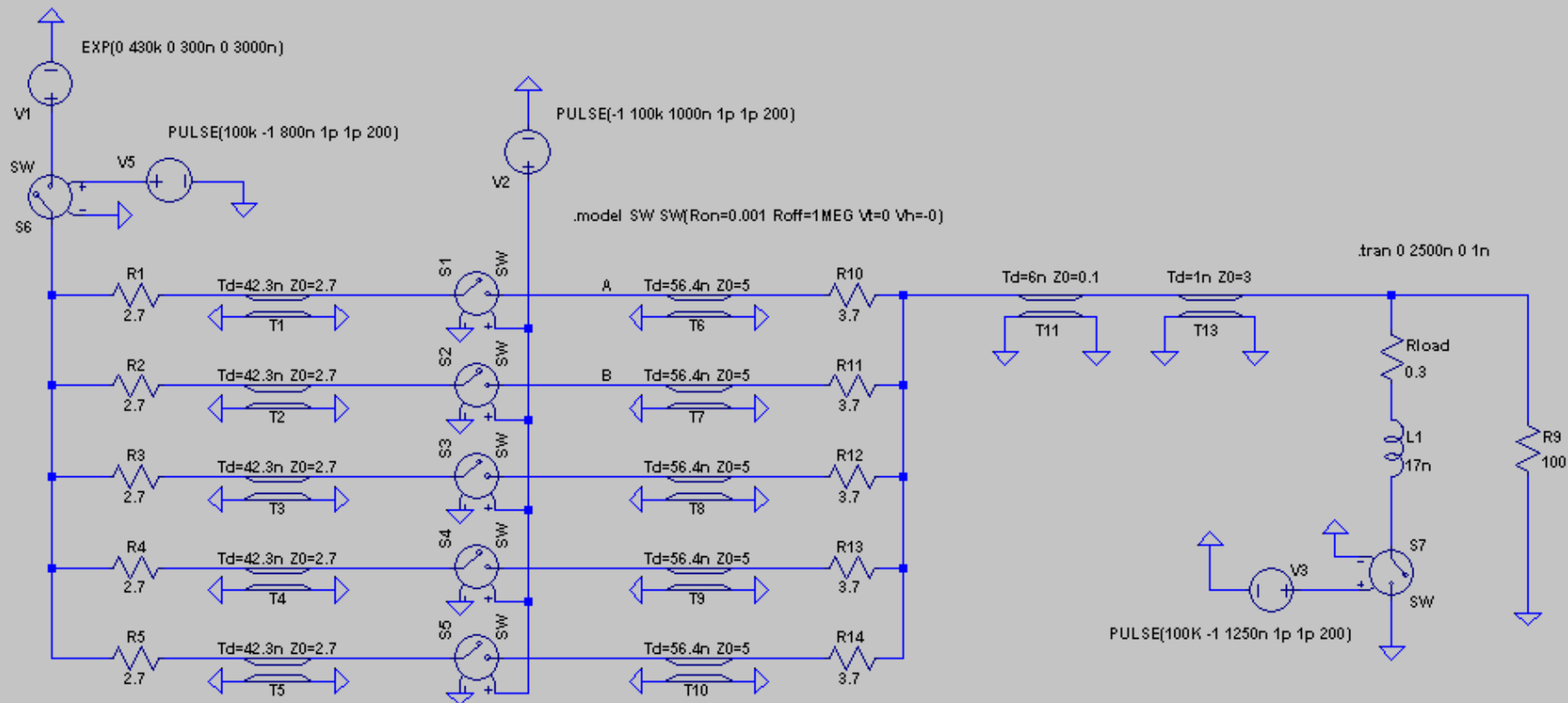
Modified ISIS Induction-Cell Driver: **0.3 Ω load**



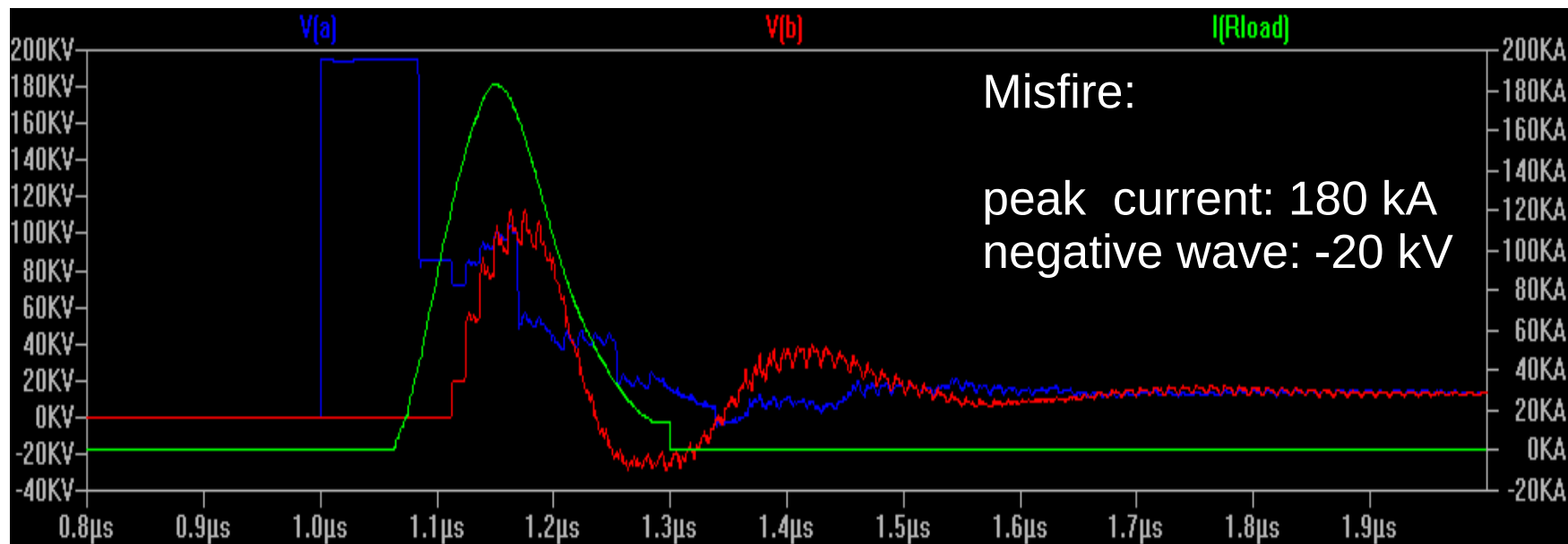
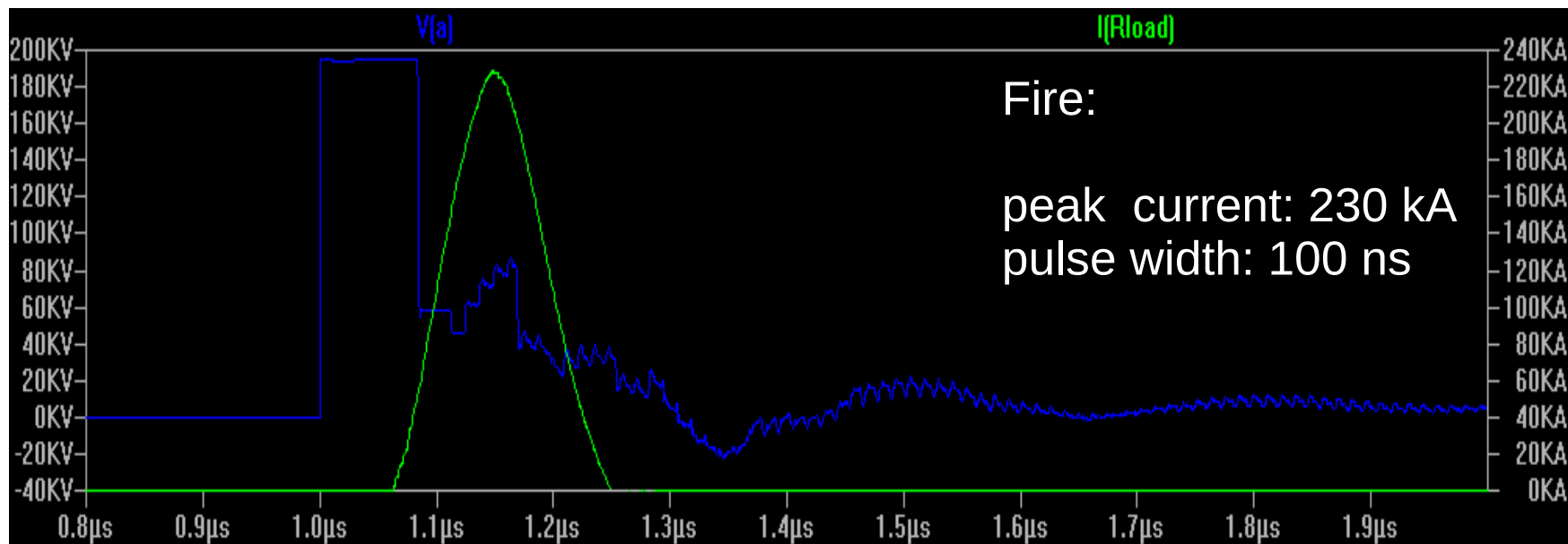
Modified ISIS Induction-Cell Driver: **0.3 Ω load**



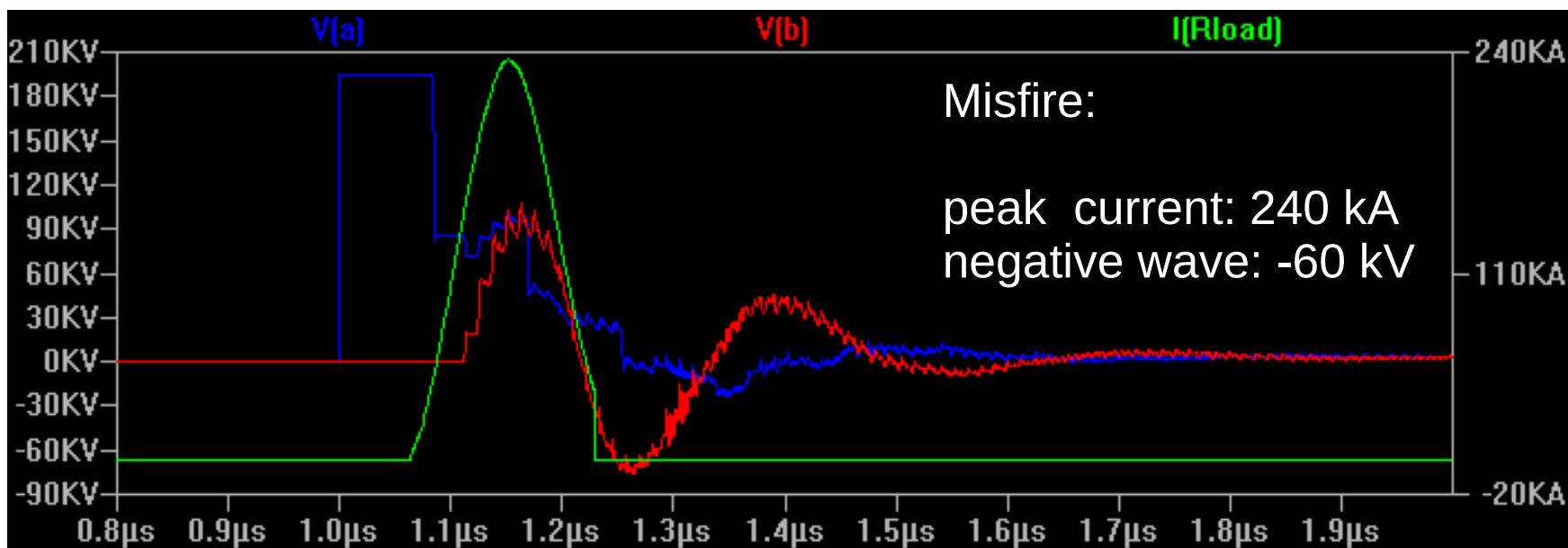
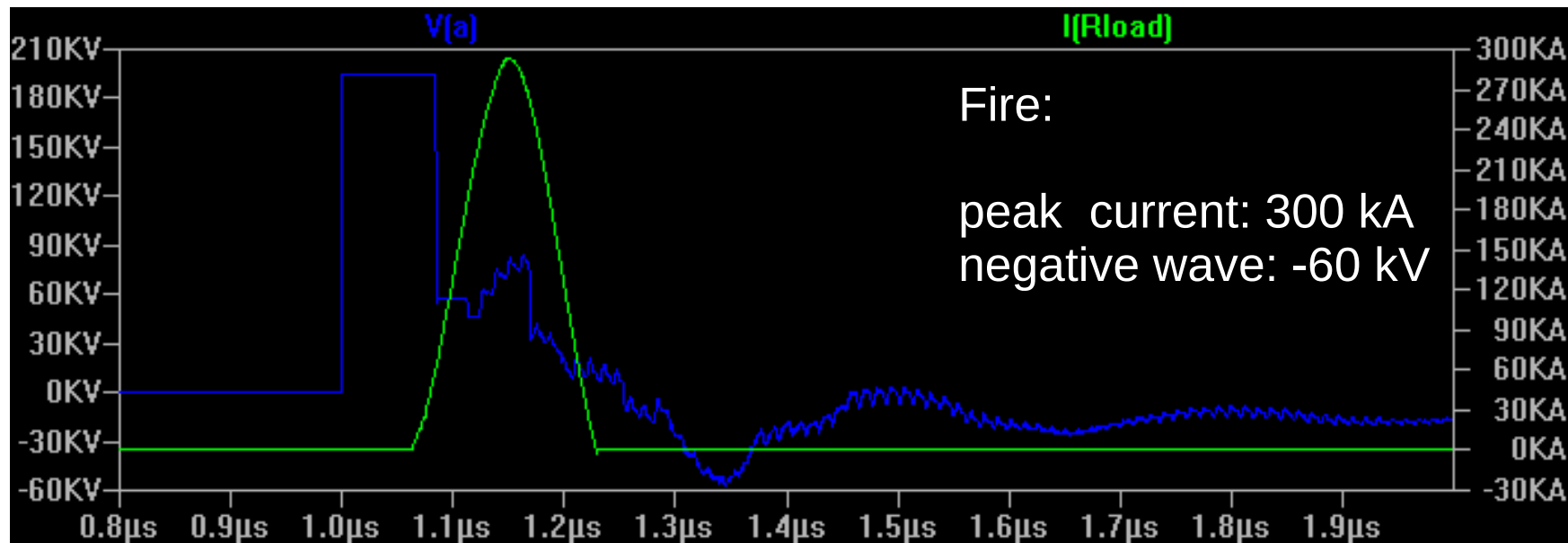
Modified ISIS Induction-Cell Driver: **0.1 Ω load**



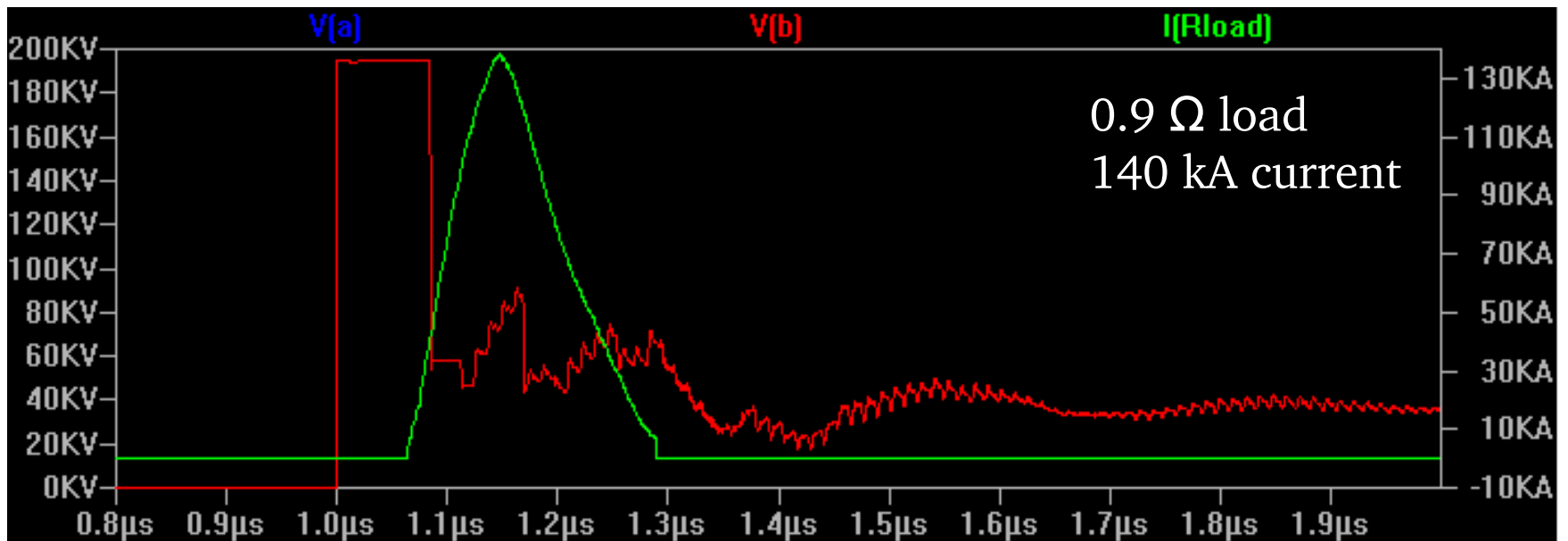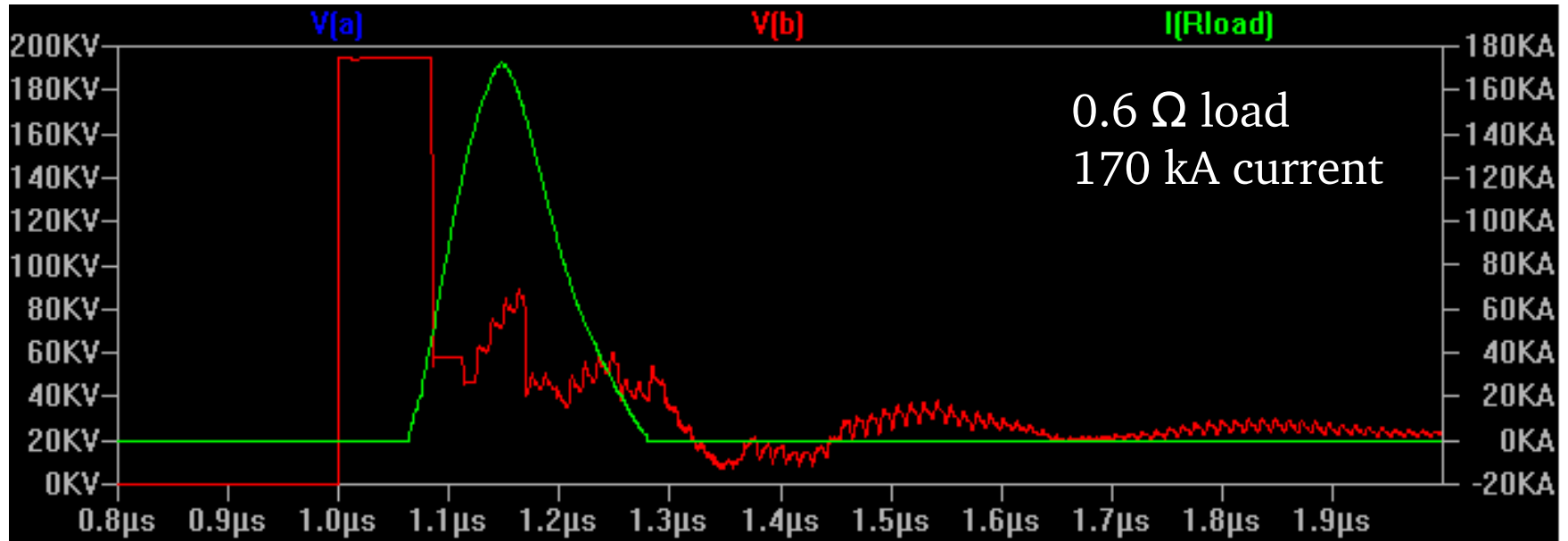Modified ISIS Induction-Cell Driver: 0.3, 0.9 Ω loads



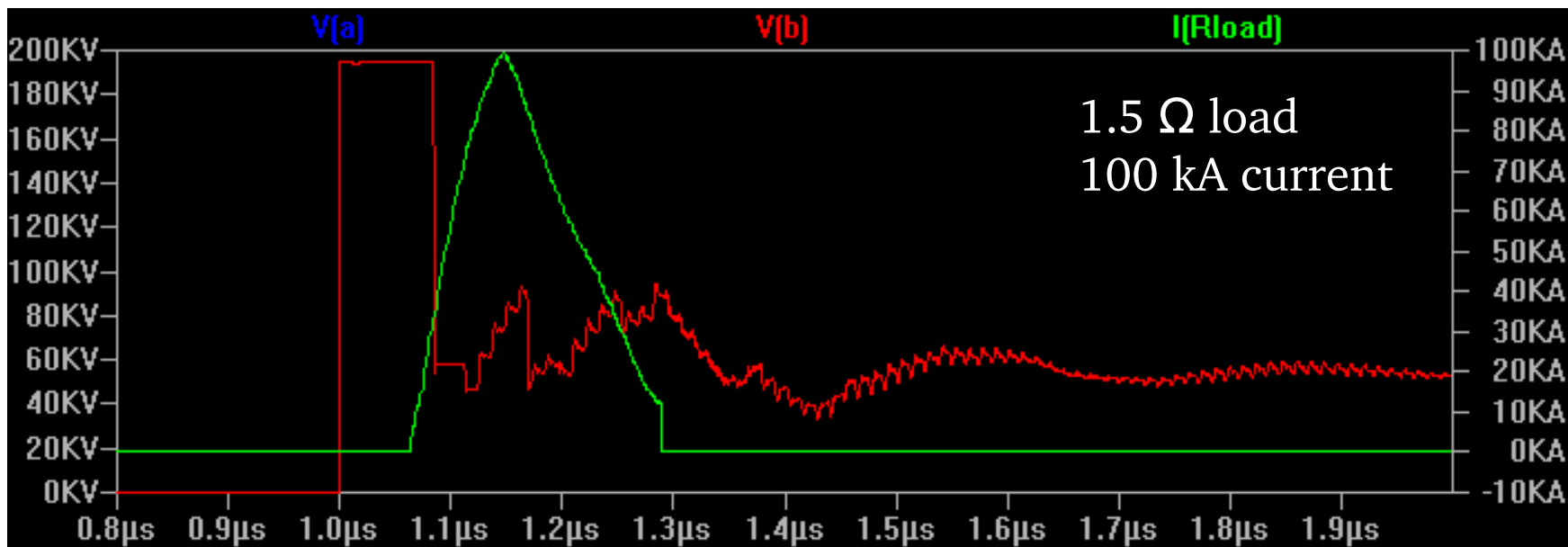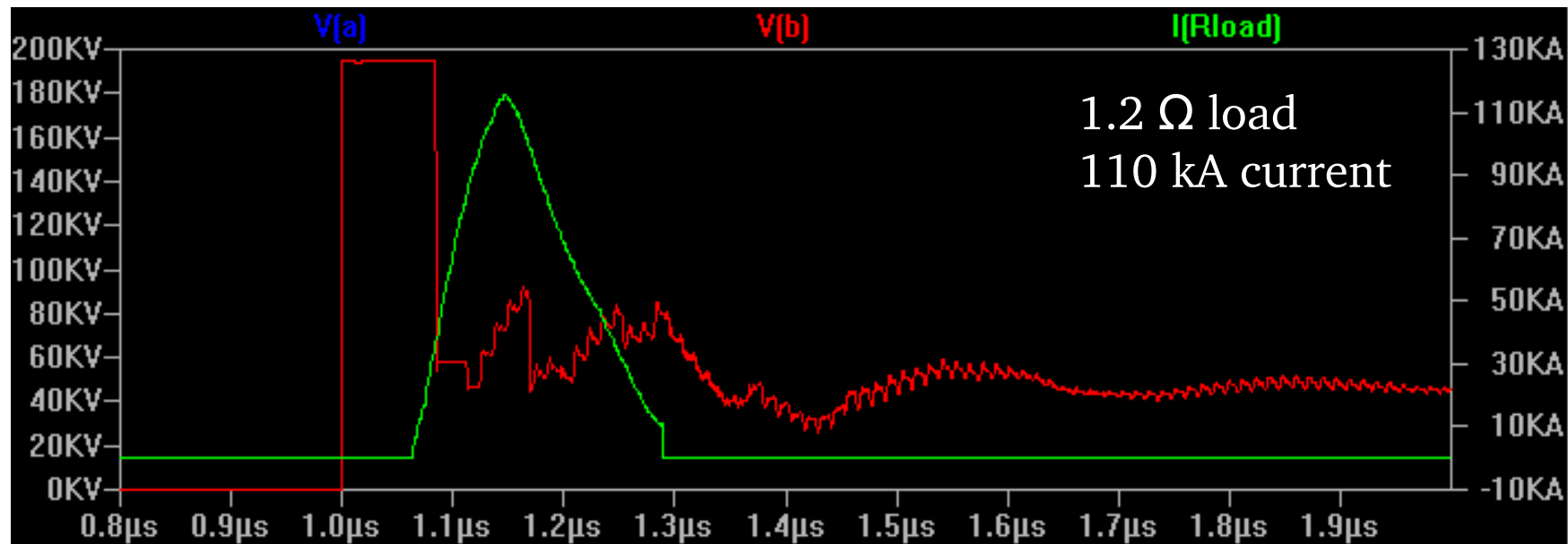Modified ISIS Induction-Cell Driver: 1.2, 1.5 Ω loads




Modified ISIS Induction-Cell Driver: **What We Need**

1. Five high power resistors: 3.7Ω each

2. Transformer/combiner:

$$T = 6 \text{ ns}$$

$$Z_0 = 0.1 \Omega$$

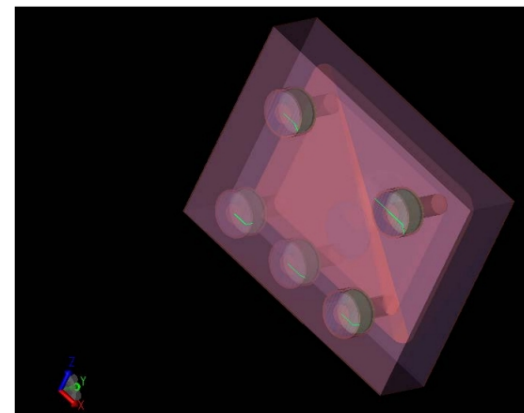

3. Vacuum Chamber:

$$T = 1 \text{ ns}$$

$$Z_0 = 3 \Omega$$



4. X-Pinch wires (Load):

$R = 0.3 \Omega$ and more

$L = 17 \text{ nH}$ and more

$l = 25 \text{ mm}$ long

Modified ISIS Induction-Cell Driver: **Transformer**

$$T = 6 \text{ ns}$$


$$Z_0 = 0.1 \ \Omega$$

Transformer Length:

$$30 \text{ cm/ns} * 6 \text{ ns} = 180 \text{ cm (in vacuum)}$$

$$180 \text{ cm} / 9 = 20 \text{ cm (in water)}$$

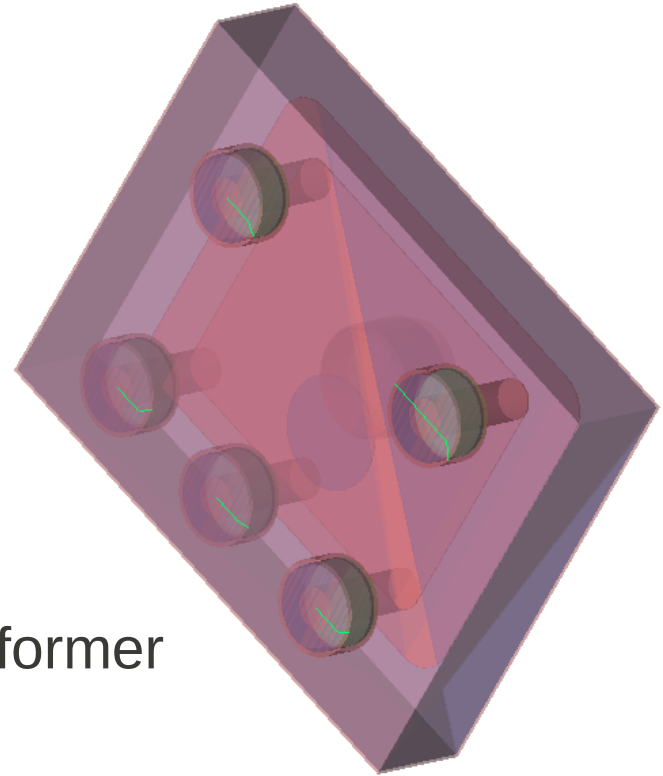We can do 20 cm long water filled transformer



Transformer Impedance:

$$Z = L/C$$

Challenge to design, but can be done with XFDTD