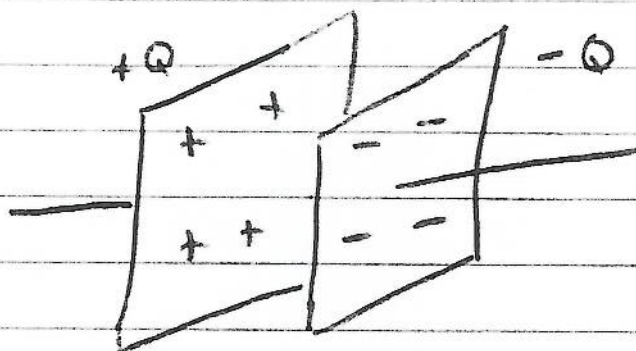


Capacitance

Suppose I have two conductors



- V is constant over conductor
why?

- Can speak of the potential difference between them

$$V_{ab} = - \int_a^b \vec{E} \cdot d\vec{\rho}$$

If I double Q

→ V doubles

$$V = \frac{Q}{C}$$

$\frac{1}{C}$: proportionality constant b/w V & Q

C : capacitance

- > 0 , always a + quantity
- measure of ability to store charge
- units $\frac{\text{Coulombs}}{\text{Volts}} \equiv \text{farad}$

• symbol 

C is a geometrical quantity


Determined by

- sizes of conductors
- shapes of conductors
- relative orientation
- separation of conductors

→ A constant which describes the two conductor system


Circuit configurations

Connected in parallel

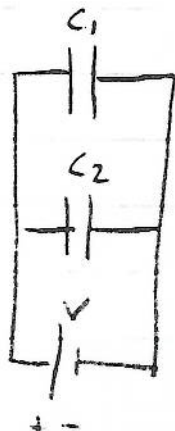


Same potential across each

Connected in series

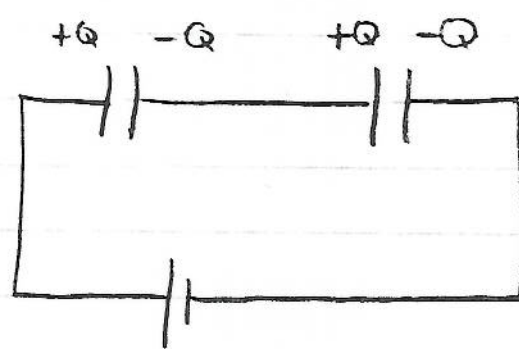


Same charge
on each

Consider C's in parallel

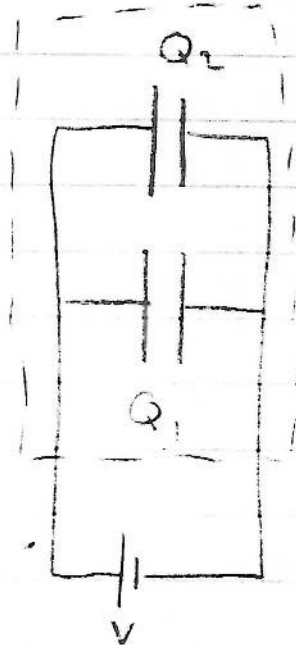

Important trick:

Replace w/ one capacitor

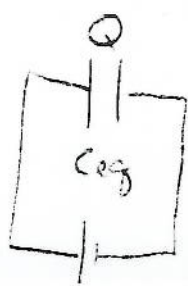

42

C_{eq} has same effect on circuit as
 C_1 and C_2

$$Q_1 = C_1 V$$

$$Q_2 = C_2 V$$

$$Q = (C_1 + C_2) V$$

$$= C_{eq} V$$

$$C_{eq} = C_1 + C_2$$


For more than two capacitors

$$C_{eq} = C_1 + C_2 + C_3 + \dots$$


Equivalent capacitance of capacitors in parallel is the sum of the individual capacitances.

→ Capacitors in parallel, C_{eq} is greater than individual capacitances

Capacitors in series - Open switch

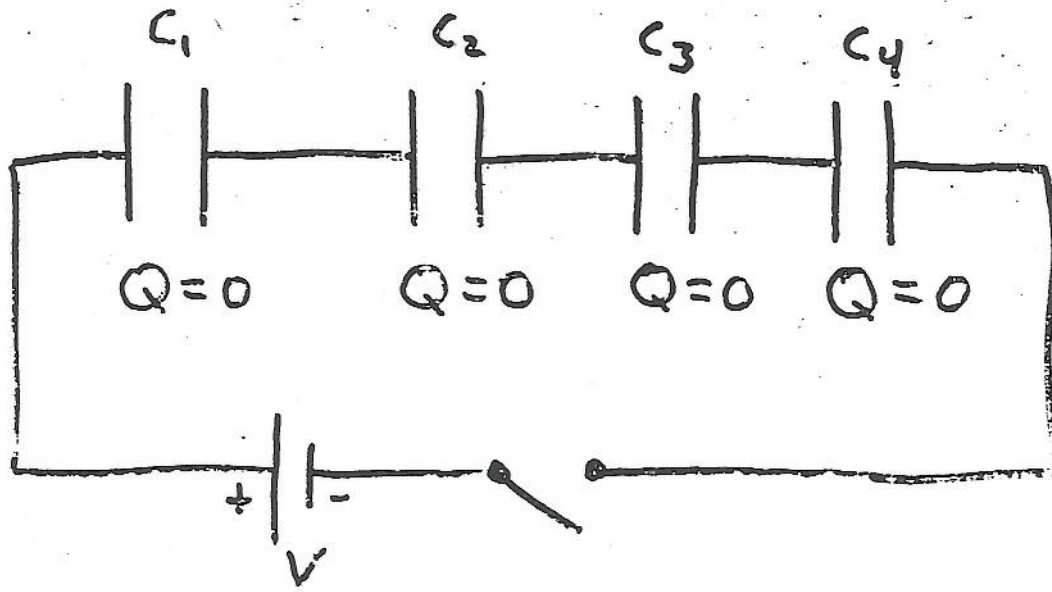


Closed switch

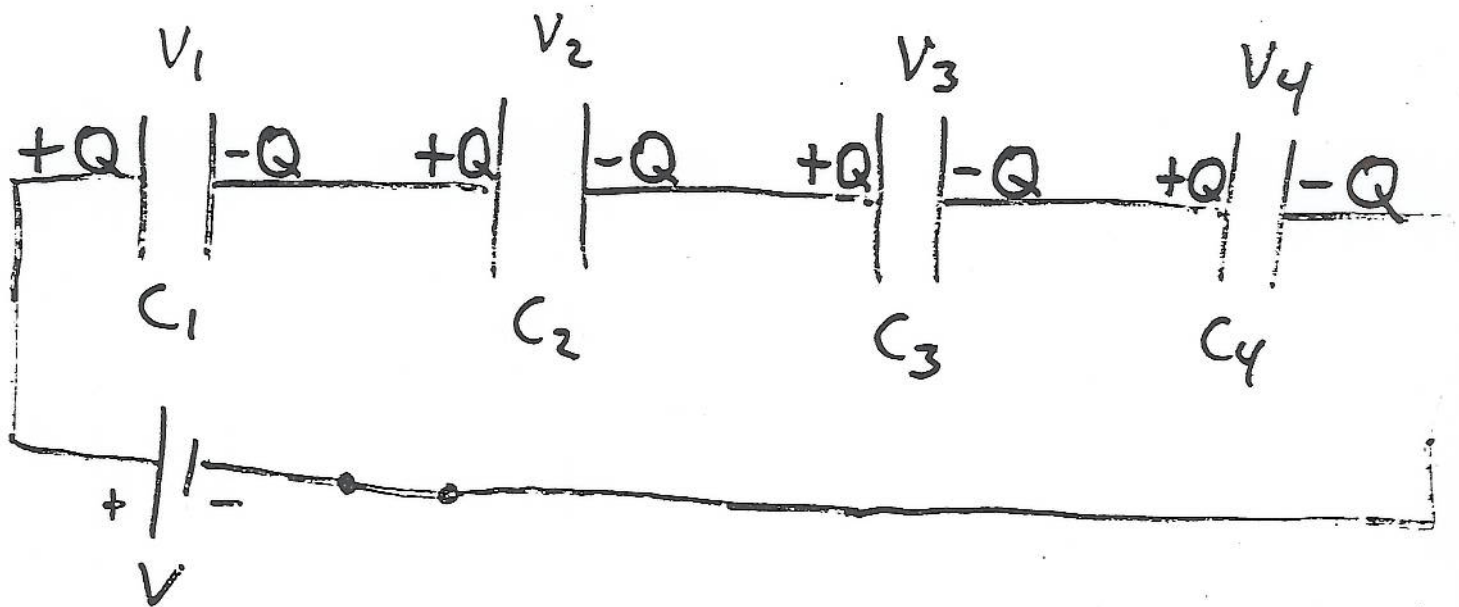

Charge does not jump gap, yet it flows
 $\rightarrow$ induction.


What's our equivalent capacitor?

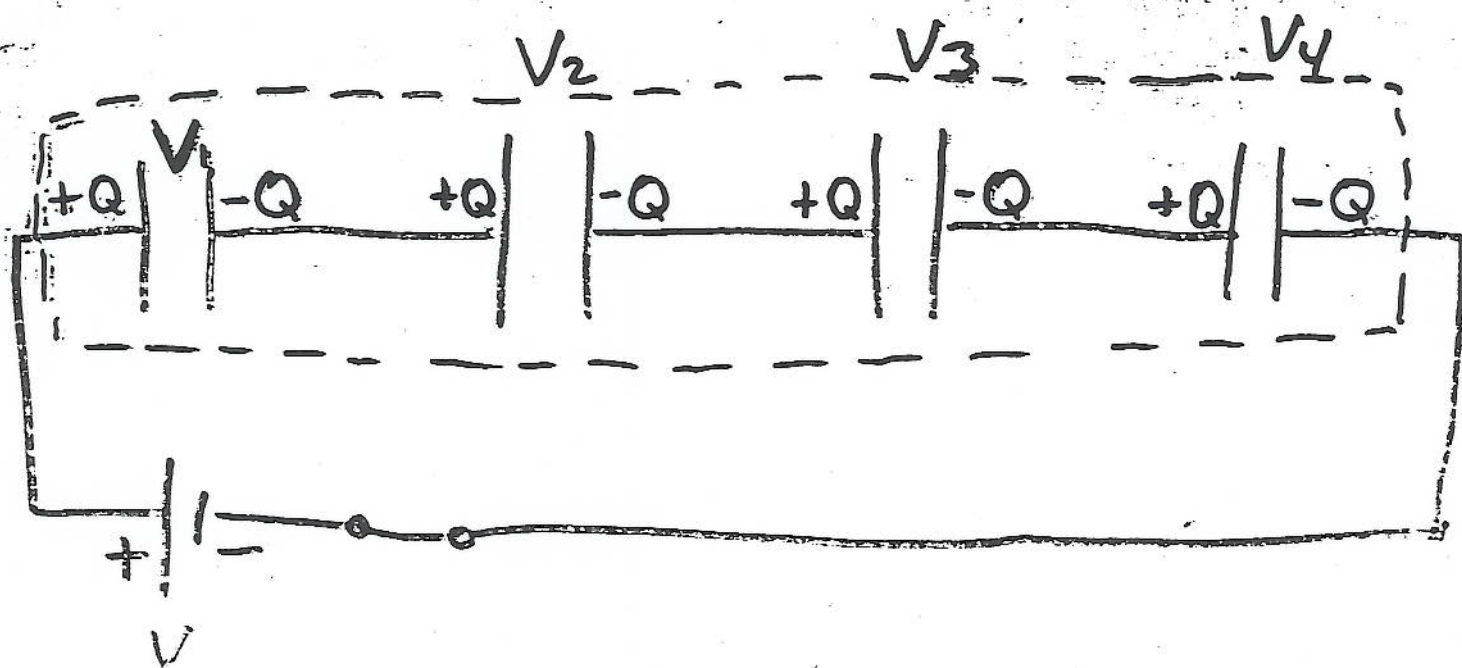

Replace



$\Rightarrow$

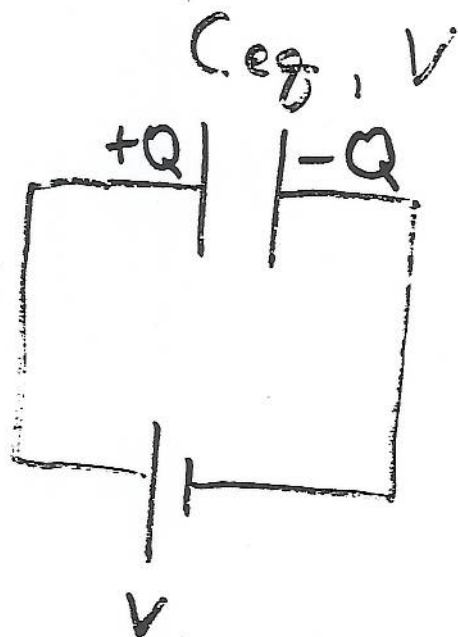

So, we have

$$V = \frac{Q}{C_{eq}}$$

$$V = V_1 + V_2 + V_3 + V_4$$

$$V_1 = \frac{Q}{C_1} \quad V_2 = \frac{Q}{C_2} \quad V_3 = \frac{Q}{C_3} \quad V_4 = \frac{Q}{C_4}$$



$$V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} \right)$$

$$\boxed{\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots}$$

Capacitors in
series


C_{eq} is always less than individual
 C 's when in series

Which has greater C_{eq} ?

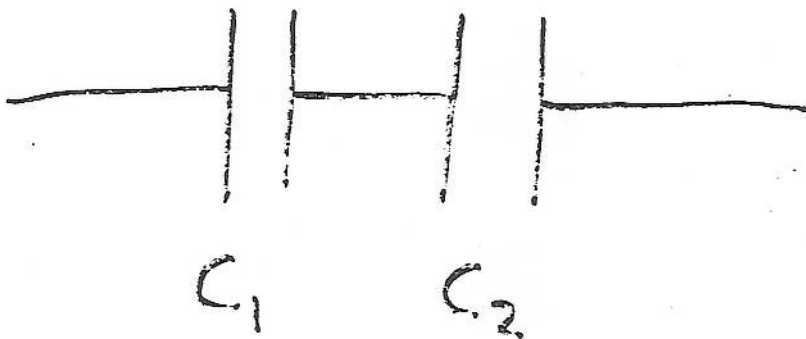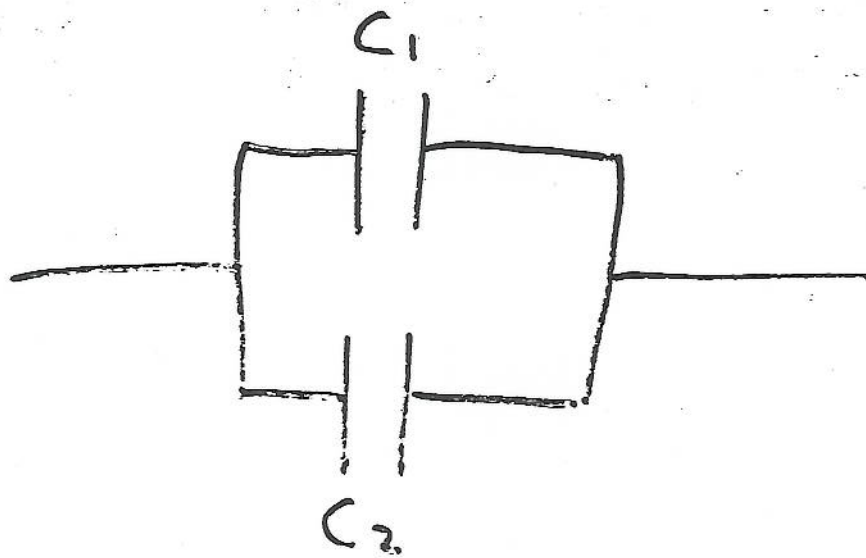

X

Capacitive AC circuit

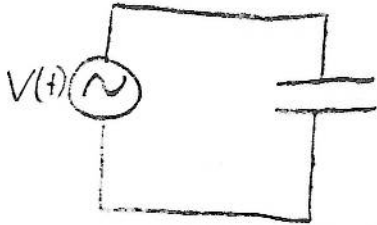

$$Q = VC$$

$$V(t) = V_0 \cos \omega t$$


$$Q(t) = V(t)C = V_0 C \cos \omega t$$

$$I(t) = \frac{dQ}{dt} = -\omega V_0 C \sin \omega t$$

$$= \omega V_0 C \cos\left(\omega t + \frac{\pi}{2}\right) \quad \begin{matrix} \uparrow \\ \text{phase} \end{matrix}$$

Large ω , large $I \rightarrow$ capacitor shorts at high ω
 Small ω , small $I \rightarrow$ open circuit for DC

* What's this $\pi/2$?

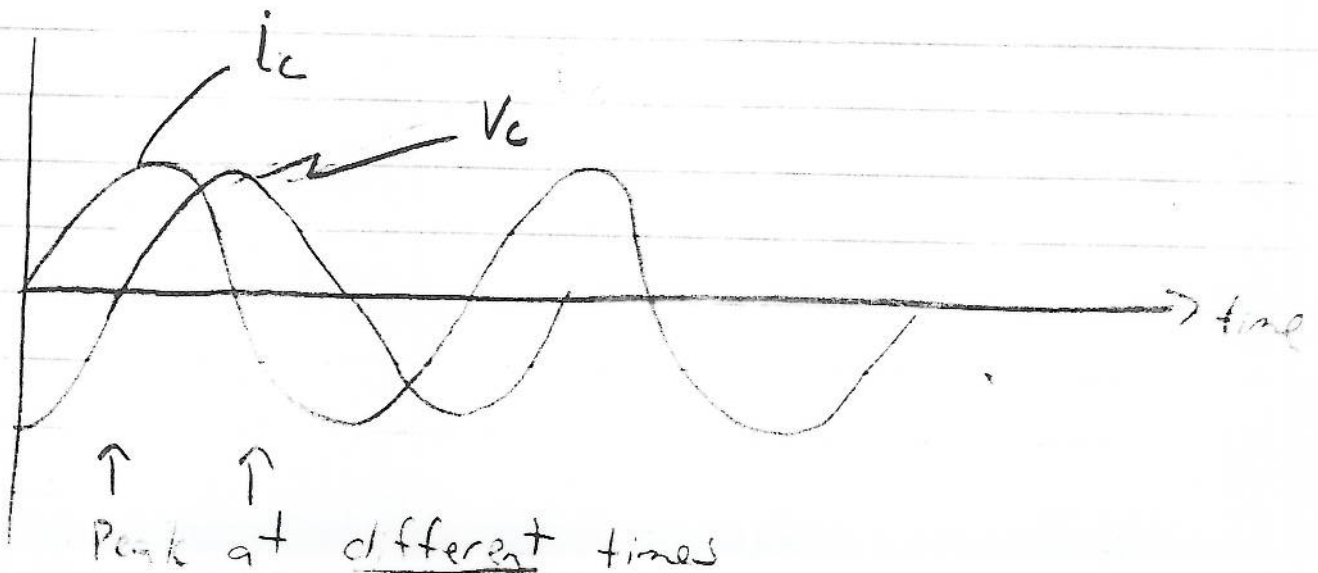

I leads V

$$V(t) = V_0 \cos \omega t = V_0 \operatorname{Re} e^{j\omega t}$$

$$e^{j\omega t} = \cos \omega t + j \sin \omega t$$

$$i = \omega C V_0 \operatorname{Re} e^{j(\omega t + \pi/2)}$$

Want eqn like $V = IR$, $I = V/R$

$$i = \omega C V_0 \operatorname{Re} [e^{j\omega t} e^{j\pi/2}]$$

$$= \operatorname{Re} [j \omega C V_0 e^{j\omega t}]$$

$$i(t) = \frac{V_0 e^{j\omega t}}{\underbrace{1/j\omega C}} \leftarrow \text{like "R"}$$


$$X_C = \frac{1}{j\omega C}$$

Big $\omega \rightarrow$ small X_C

Small $\omega \rightarrow$ big X_C

Phasor diagrams

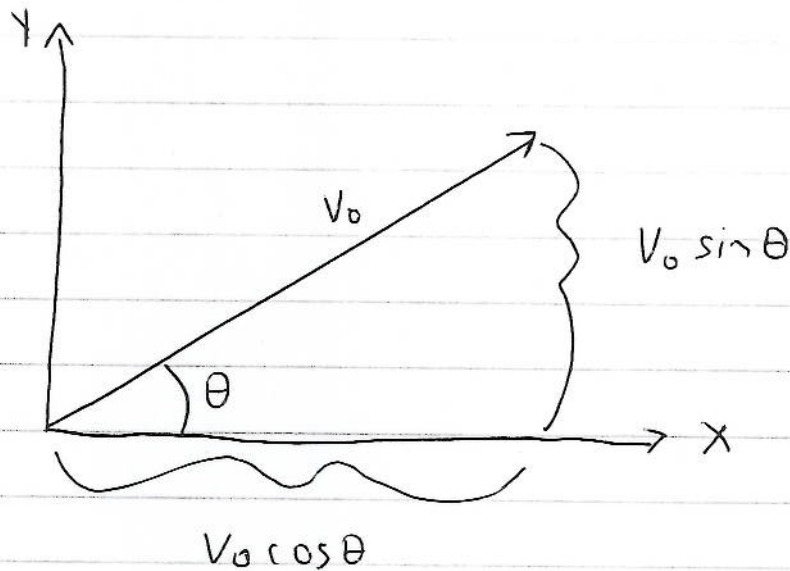Recall $e^{j\theta} = \cos\theta + j\sin\theta$



Rotating vector $\theta = \omega t$

Adding two constants


$$3 + 4 = 7 \quad \text{easy}$$

Adding two waves - add x comps of vectors

$$V(t) = V_1 \cos(\omega t + \phi_1) + V_2 \cos(\omega t + \phi_2)$$

sum depends on time

Complex voltage plane

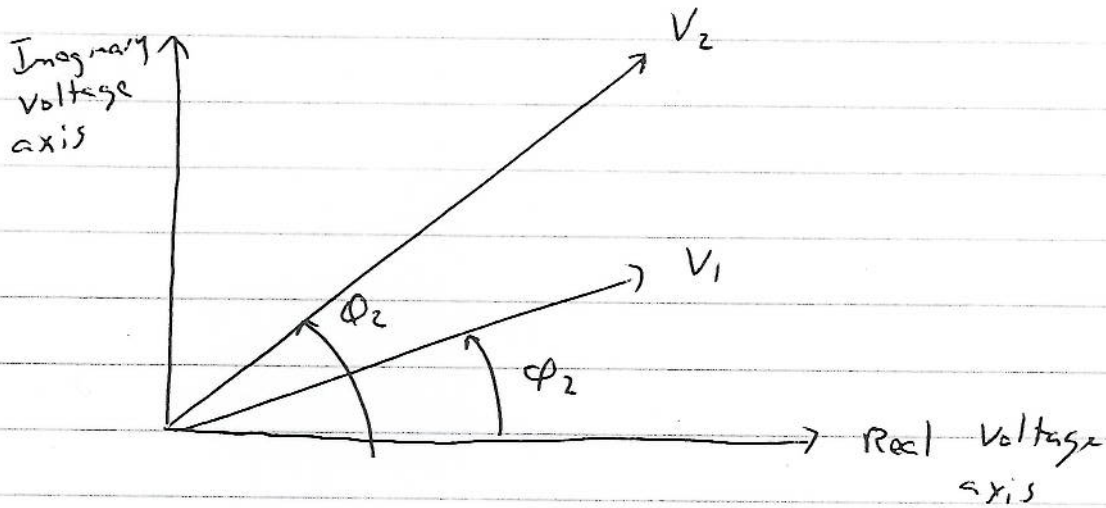


$V(t) \rightarrow$ sum of vectors in 2-d complex plane

Filters (Labs 3 & 4)

High Pass Filter





Low Pass Filter

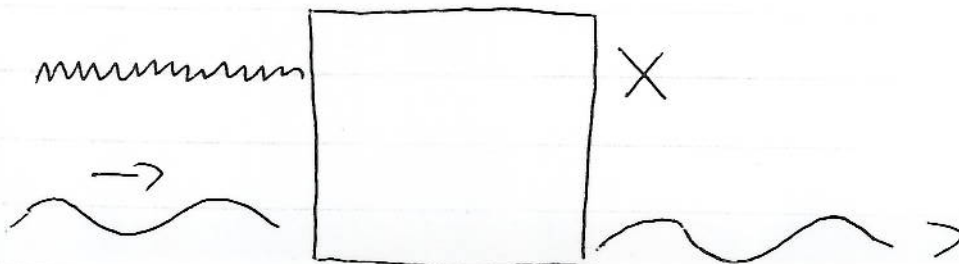


Ex:

51

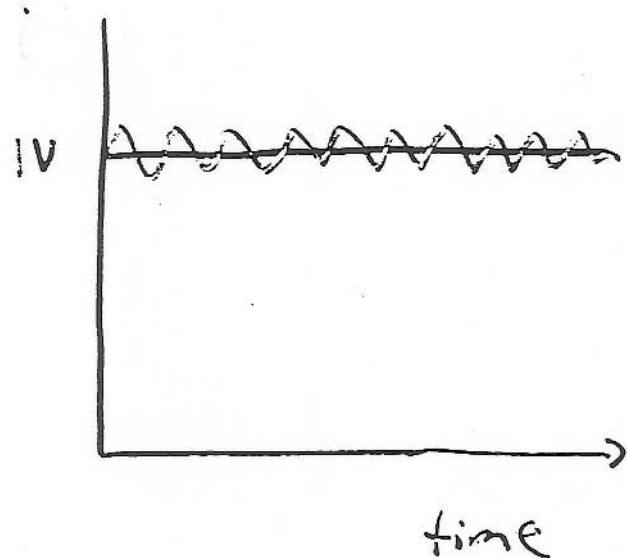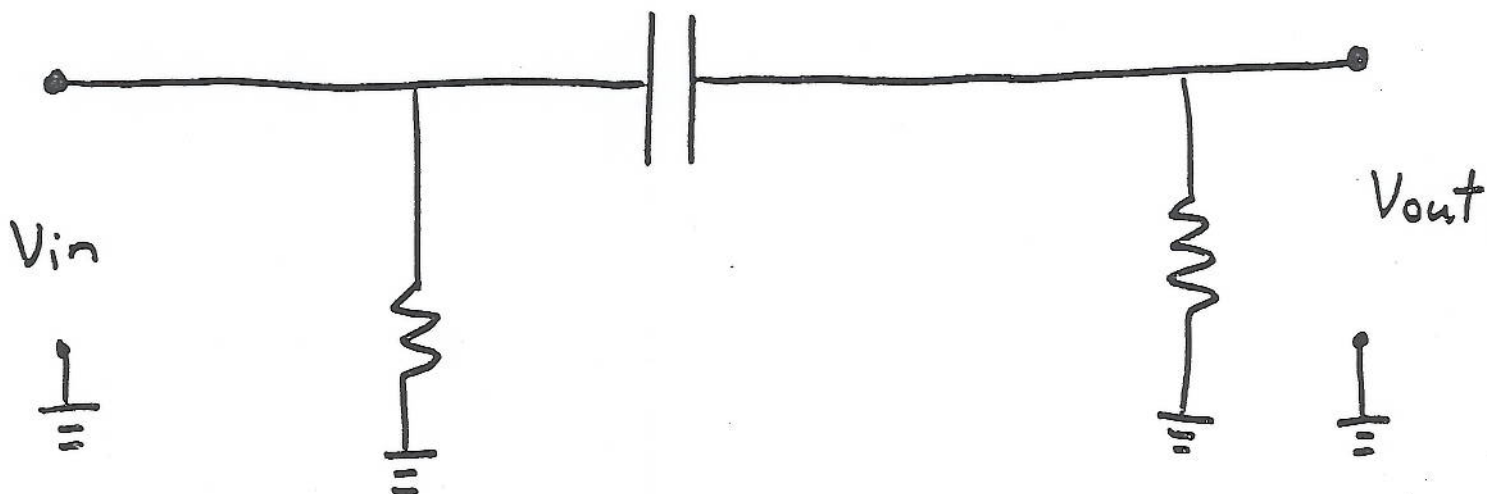

C blocks D.C.


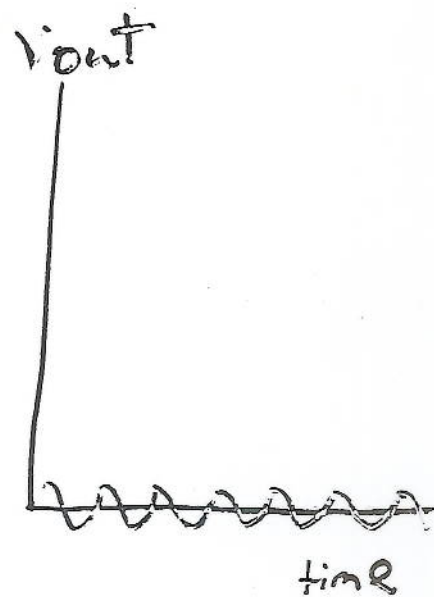


High voltage D.C. level
with signal riding on it.


Output voltage
with just
signal

Ex:

52

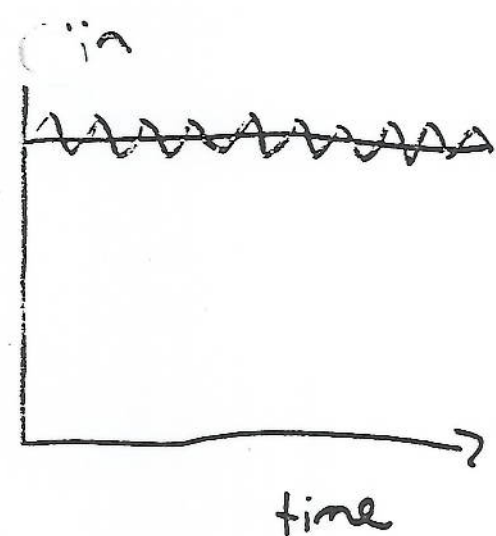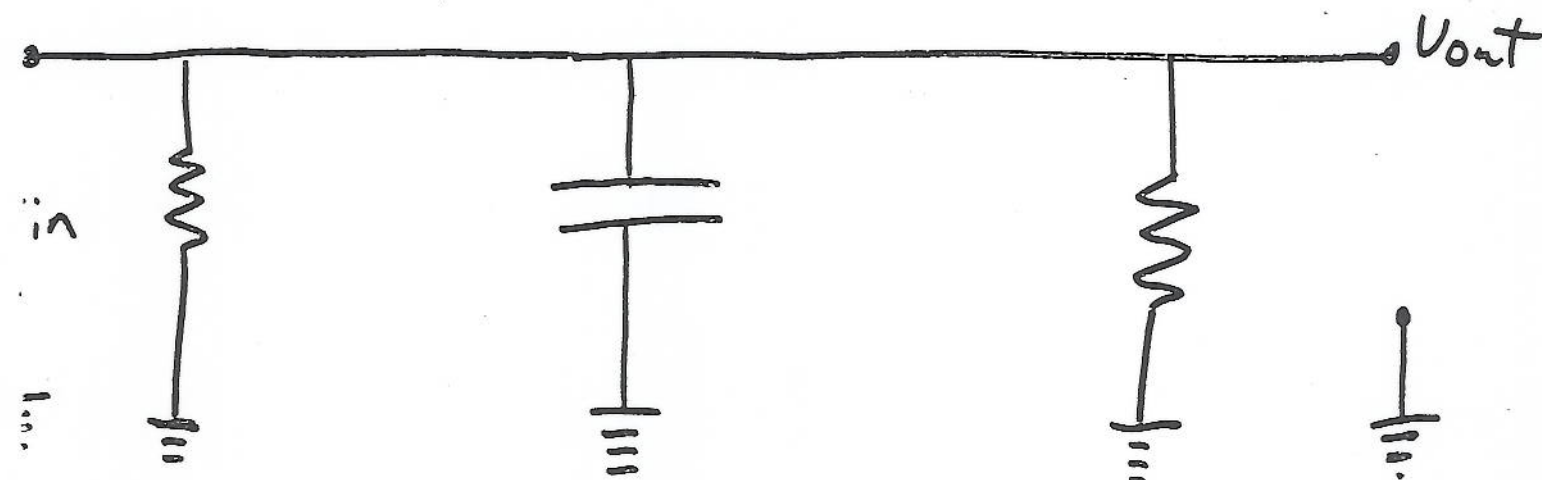


C shorts
AC to
ground

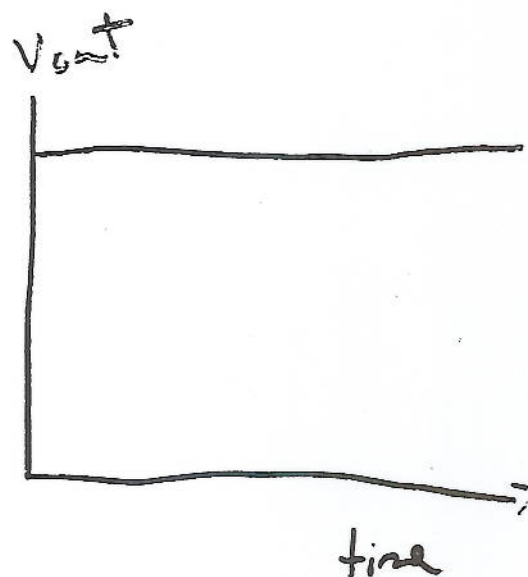

D.C. level with
unwanted noise
on it.

Cleaned up
signal

High Pass filter
Consider

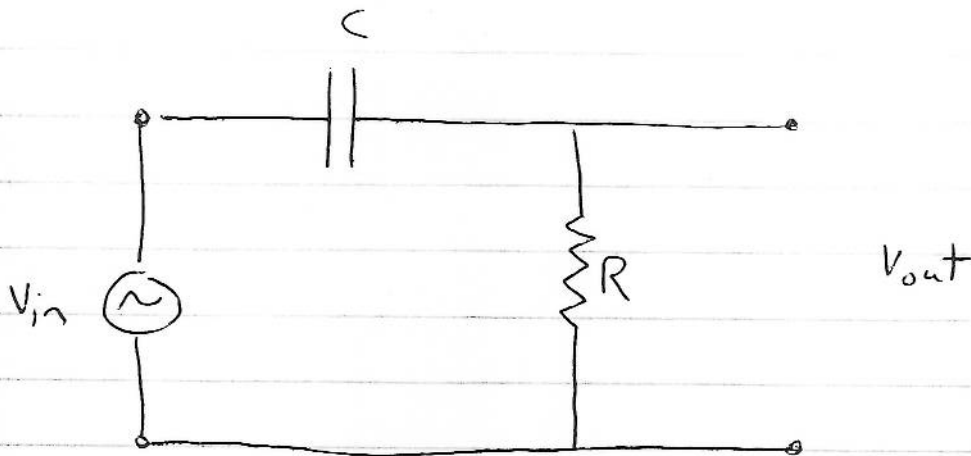


$$\text{gain} \equiv \frac{V_{out}}{V_{in}}$$

$$\text{attenuation} \equiv \frac{V_{in}}{V_{out}}$$

Aside:

If I had

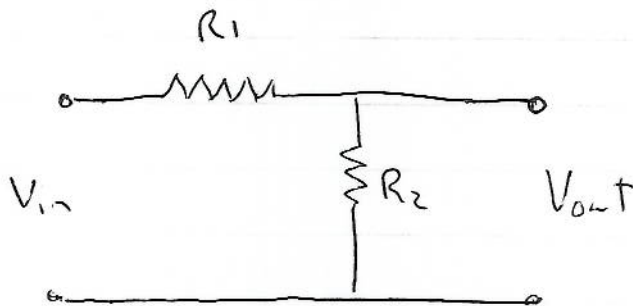

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

Now, same deal


$$V_{out} = \frac{R}{R + X_C} V_{in} = \frac{R}{R + \frac{1}{j\omega C}} V_{in} = \frac{j\omega CR}{1 + j\omega CR} V_{in}$$

90° out of phase
↙

$$\left| \frac{V_{out}}{V_{in}} \right|^2 = \left(\frac{V_{out}}{V_{in}} \right) \left(\frac{V_{out}}{V_{in}} \right)^* = \left(\frac{j\omega RC}{1+j\omega RC} \right) \left(\frac{-j\omega RC}{1-j\omega RC} \right)$$

$$= \frac{\omega^2 C^2 R^2}{1+\omega^2 C^2 R^2}$$
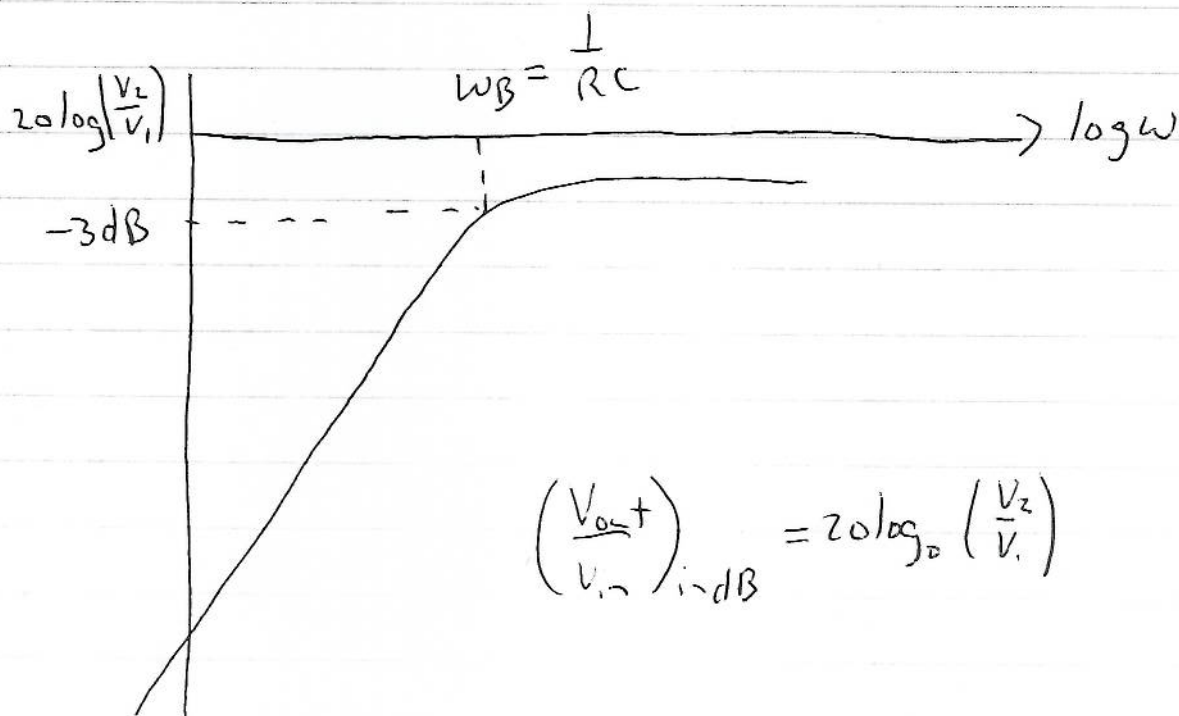
$$\frac{V_{out}}{V_{in}} = \frac{\omega RC}{\sqrt{1+\omega^2 R^2 C^2}}$$




Phasor diagram


Kirchhoff says

$$V_{in} = V_c + V_R$$

ELI ICE

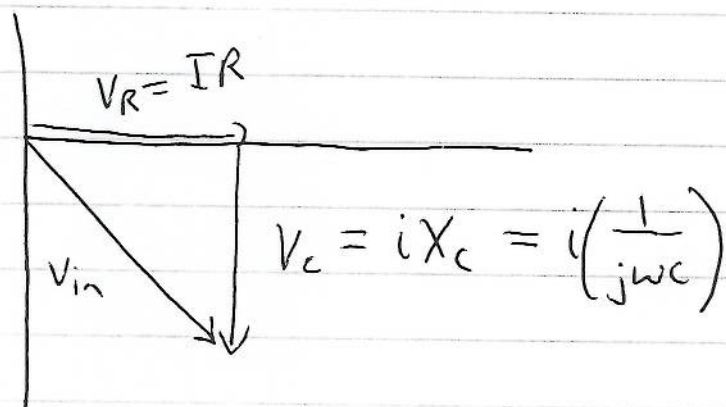

RC Low Pass Filter

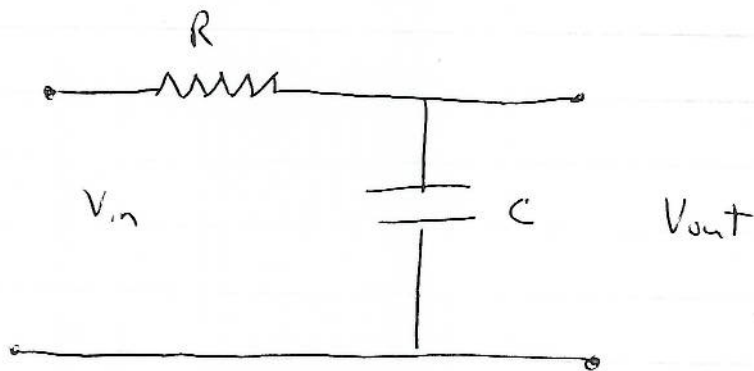


$$V_{out} = \frac{X_c}{X_R + X_c} V_{in} = \frac{\frac{1}{jwc}}{R + \frac{1}{jwc}} V_{in} = \frac{1}{1 + jwCR} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{\sqrt{1 + w^2 R^2 C^2}}$$

Q

56

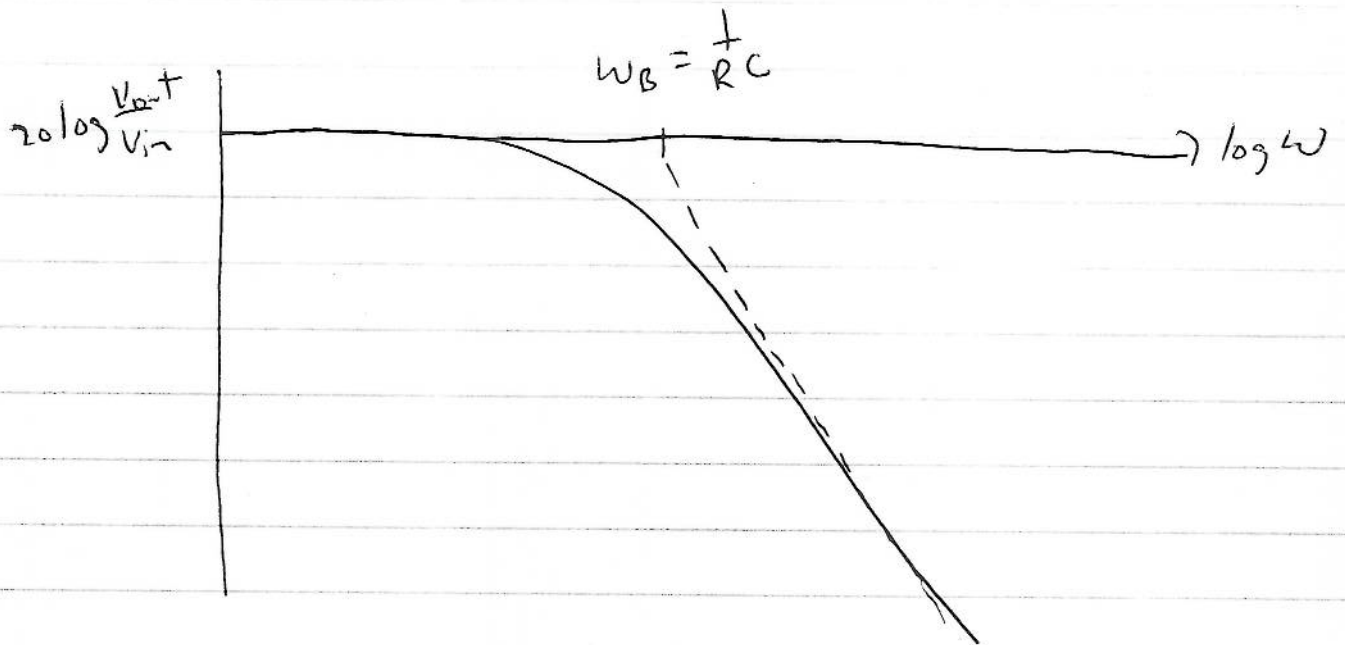

Phasor diagram

